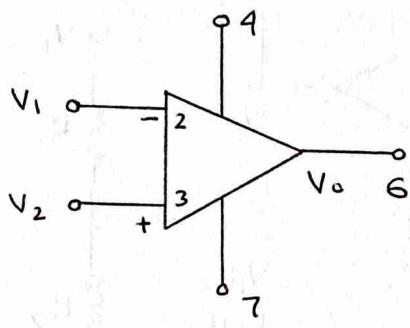


## Solid State Physics, Devices & Electronics

Topic Number	Contents
01	Operational Amplifier
02	Frequency responses of Filters.
03	Number System
04	Logic Gates
05	Karnaugh Map
06	Crystal Structure
07	Semi-Conductors
08	P-N Junction Diode
09	Transistors
10	Zener Diode
~	Previous Year Questions

# Operational Amplifier

31.07.2024



pin 3: Non inverting terminal

pin 2: Inverting terminal


pin 6: Output

pin 4,7: Limiter

$$V_{in} = V_2 - V_1$$

$$A_v = \frac{V_o}{V_{in}} = \frac{V_o}{V_2 - V_1} = \text{Voltage gain}$$

## ① Ideal OP-AMP:

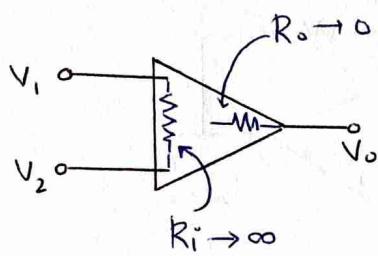

- (a) Input Resistance should be infinite
- (b) For maximum output  $V_o$ ,  $R_o \rightarrow 0$  i.e. output resistance should be zero
- (c)  $R_i \rightarrow \infty$  so that  $V_1, V_2$  not mixed.
- (d) No current flow in the OPAMP


## ② Non-inverting

From the concept of Virtual ground Potential at 0 is  $V_i$

$$\text{Now, } i_1 = \frac{0 - V_i}{R_1}, i_2 = \frac{V_i - V_o}{R_2}$$

As the currents are same
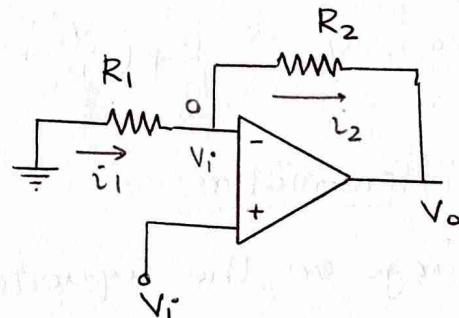
$$-\frac{V_i}{R_1} = \frac{V_i - V_o}{R_2} \Rightarrow V_o = V_i \left(1 + \frac{R_2}{R_1}\right)$$





## ③ Inverting:

As the currents are same,

$$\frac{V_i - 0}{R_1} = \frac{0 - V_o}{R_2}$$
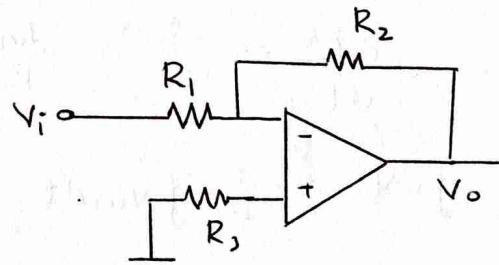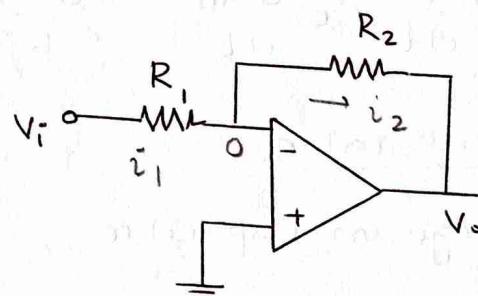
$$\therefore V_o = -\frac{R_2}{R_1} V_i$$




## ④ Differential

From Potential  
divider. Potential  
at a is

$$V_a = \frac{2 \times 6}{2+2} = \frac{12}{4} = 3 \text{ Volt}$$


$$\text{Now, } \frac{3-1}{1} = \frac{V_o - 3}{5}$$
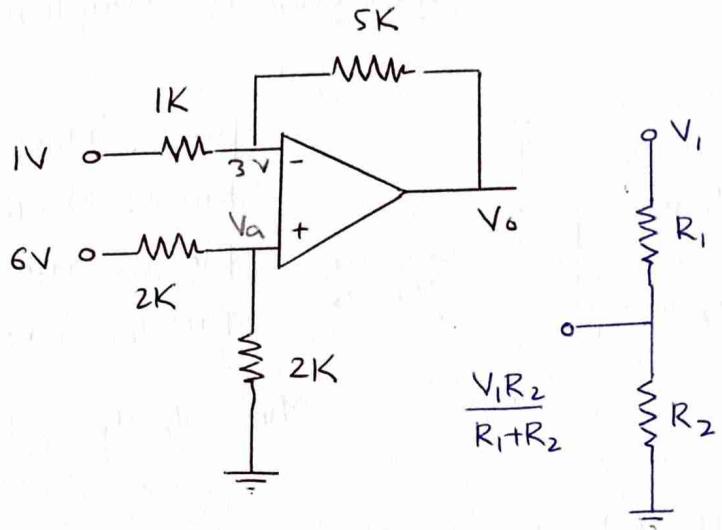
$$10 = V_o - 3 \Rightarrow V_o = 13 \text{ Volt}$$


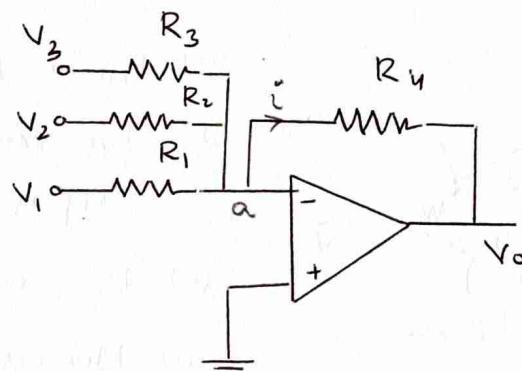
## ⑤ Adder/Summing

From the concept of  
Virtual ground. Potential  
at a.  $V_a = 0$



$$\text{Now } i = \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right) \quad \text{Also } \frac{0 - V_o}{R_4} = i$$


$$\text{So, } V_o = -R_4 \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right)$$

## ⑥ Differentiator

charge on the capacitor

$$q = C(V_{in} - 0) = CV_{in}$$
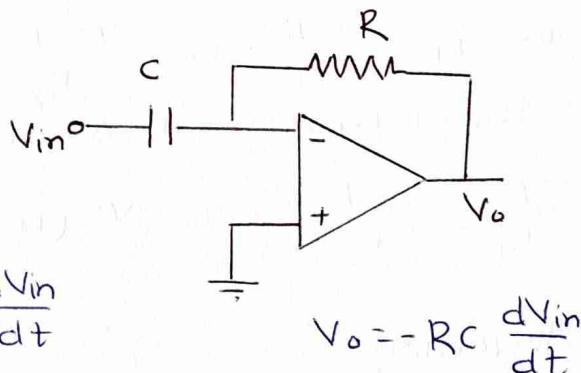
$$i = \frac{dq}{dt} = C \frac{dV_{in}}{dt} \quad \frac{0 - V_o}{R} = C \frac{dV_{in}}{dt}$$




## ⑦ Integrator:

charge on capacitor

$$q = CV = C(0 - V_o)$$

$$\frac{dq}{dt} = -C \frac{dV_o}{dt} \quad i = \frac{V_{in}}{R}$$
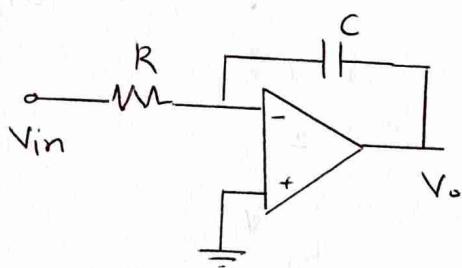
$$\int dV_o = -\frac{1}{RC} \int V_{in} dt$$




$$V_o = -\frac{1}{RC} \int V_{in} dt$$

## ⑧ Exponential / Antilog

Diode Current

$$i = i_0 e^{\frac{qV_{in}}{nKT}} = \frac{V_{in} - V_0}{R}$$
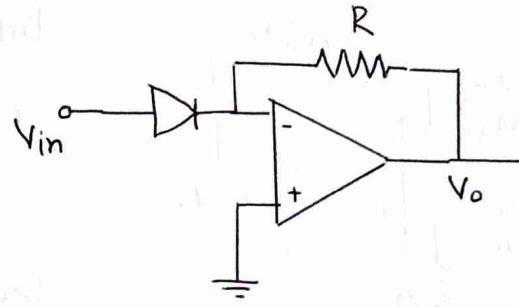
$$V_0 = -i_0 R \exp\left(\frac{qV_{in}}{nKT}\right)$$




## ⑨ Logarithmic

Diode Current

$$i = \frac{V_{in} - V_0}{R} = i_0 \exp\left(-\frac{qV_0}{nKT}\right)$$

$$\frac{V_{in}}{i_0 R} = \exp\left(-\frac{qV_0}{nKT}\right)$$
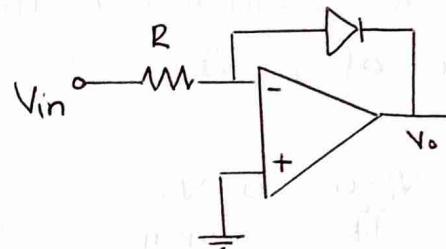
$$V_0 = -\frac{nKT}{q} \ln\left(\frac{V_{in}}{i_0 R}\right)$$




## ⑩

At first we have to observe to voltage at Non inverting terminal is  $V_2$

$$\text{Now } \frac{V_1 - V_2}{R_1} = \frac{V_2 - V_0}{R_3}$$
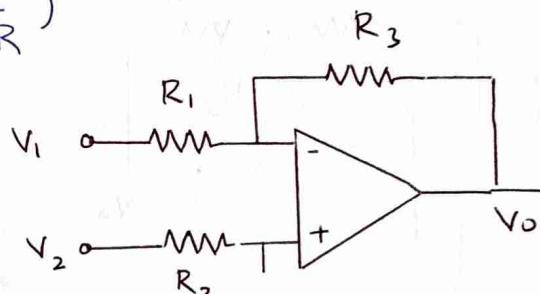
$$V_2 - V_0 = \frac{R_3}{R_1} (V_1 - V_2)$$




$$V_0 = V_2 + \frac{R_3}{R_1} (V_1 - V_2)$$

$$V_0 = \left(1 + \frac{R_3}{R_1}\right) V_2 - \frac{R_3}{R_1} V_1$$

## ⑪

Find the output Voltage

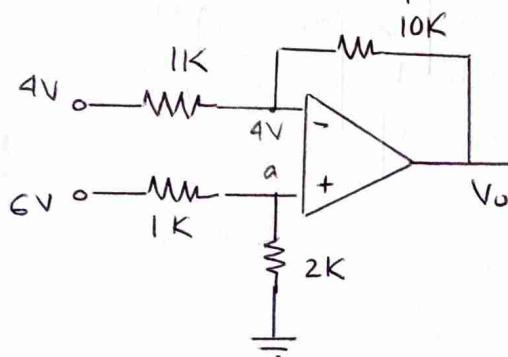


$$\text{Potential at } a, V_a = \frac{6 \times 2}{1+2} = 4 \text{ Volt}$$

$$\frac{4-4}{1} = \frac{4-V_0}{10} \Rightarrow V_0 = 4 \text{ Volt}$$

output voltage is 4 Volt

(12)

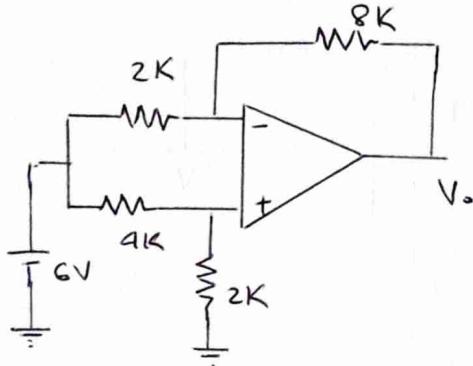

Potential at a.  $V_a = \frac{6 \times 2}{4+2} = 2 \text{ Volt}$

$$\frac{6-2}{2} = \frac{2-V_o}{8} \Rightarrow 16 = 2-V_o \\ \Rightarrow V_o = -14 \text{ Volt}$$


The output Voltage is  $-14 \text{ Volt}$

(13)


If  $V_i = 2 \sin \omega t \text{ mV}$ , the value of  $i_o$  is

$$i = \frac{V_i - 0}{1k} = \frac{0 - V_o}{10k \Omega}$$
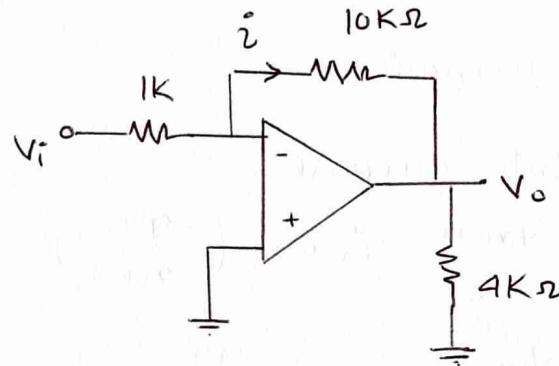
$$i = 2 \sin \omega t \times 10^{-3} \times 10^{-3} = 2 \sin \omega t \mu \text{A}$$



(14)

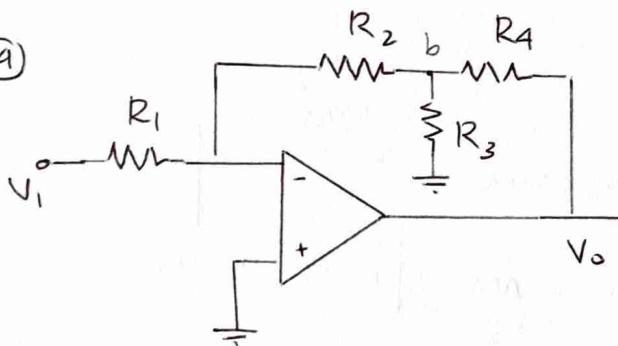

Find the output Voltage  $V_o$ .

let the Potential at b is  $\alpha$

$$\frac{\alpha - 0}{R_2} + \frac{\alpha - 0}{R_3} + \frac{\alpha - V_o}{R_4} = 0$$

$$\alpha \left( \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right) = V_o$$

Also

$$\frac{V_i - 0}{R_1} = \frac{0 - \alpha}{R_2} \Rightarrow \alpha = - \frac{R_2}{R_1} V_i$$

Value of output Voltage is


$$- \frac{R_2}{R_1} V_i \left( \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right) = V_o$$

$$V_o = - \frac{R_2}{R_1} V_i \left( \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right)$$

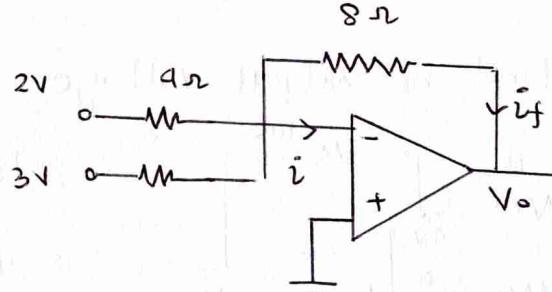(15)

Find the Value of  $i$

Since no current flow in the OPAMP.  $i = 0$



(4)


(16)

Potential at a

$$V_a = \frac{25 \times 3}{3+5} = \frac{75}{8} \text{ Volt}$$

$$\frac{3 - \frac{75}{8}}{15} = \frac{\frac{75}{8} - V_o}{20}$$
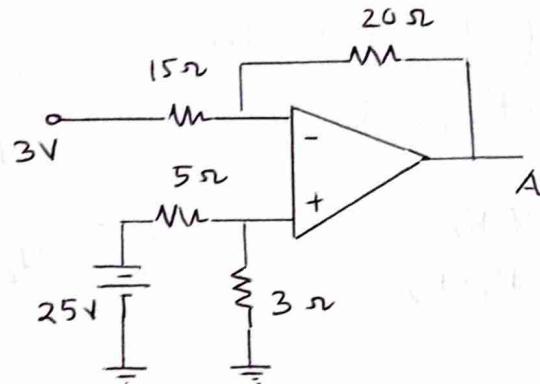
$$-47.06 = 9.375 - V_o \Rightarrow V_o = 9.375 + 47.06 = 56.435 \text{ Volt}$$




(17)

Given that

$$V_1 = 2V$$

$$V_2 = 5V.$$

Find the output  
Voltage  $V_o$

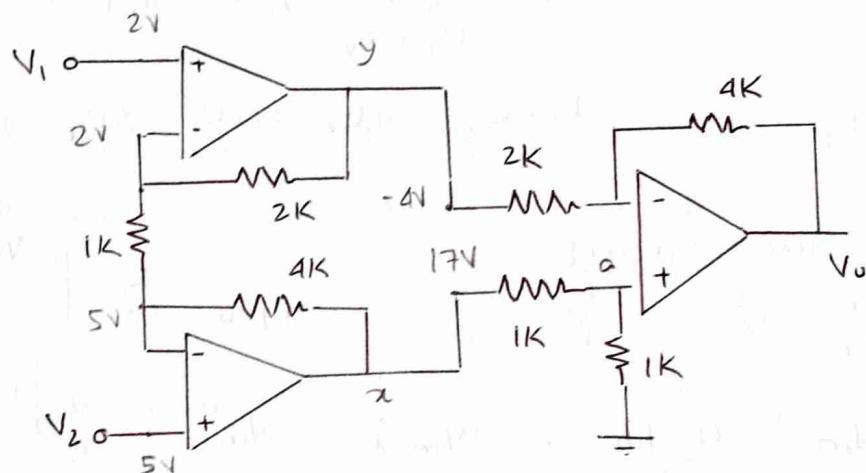

$$\frac{x-5}{4} = \frac{5-2}{1} \Rightarrow x = 17 \text{ Volt} \quad -\frac{y+2}{2} = \frac{5-2}{1} \Rightarrow y = -4 \text{ Volt}$$

$$\text{Potential at } a, V_a = \frac{17 \times 1}{2} = 8.5 \text{ Volt}$$

$$\frac{-4 - 8.5}{2} = \frac{8.5 - V_o}{4} \Rightarrow -V_o + 8.5 = -25 \Rightarrow V_o = 33.5 \text{ Volt}$$


(18)

In the operational amplifier. Voltage at A is

Potential at a

$$V_a = \frac{1 \times 1}{1+1} = 0.5 \text{ Volt}$$

Voltage at A is  
0.5 Volt

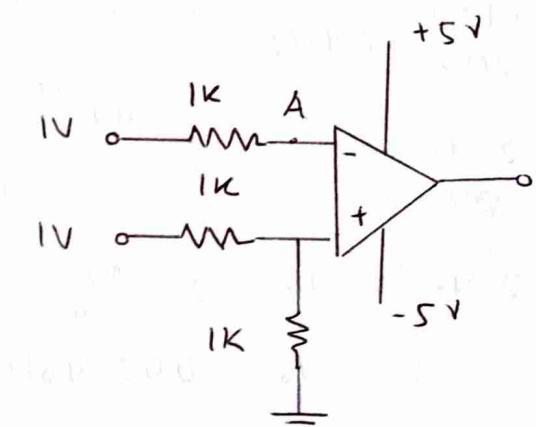

(9)

$$V_o = \left( -V_1 + \frac{V_2}{2} \right) \text{ the}$$

ratio  $R_1/R_2$  is

 $\Rightarrow$ 

$$V_a = \frac{V_2 R_2}{R_1 + R_2}$$

$$\frac{V_1 - V_a}{R} = \frac{V_a - V_o}{R}$$

$$V_1 = 2V_a - V_o \Rightarrow V_o = 2V_a - V_1$$

$$\Rightarrow V_o = \frac{2V_2 R_2}{R_1 + R_2} - V_1 = -V_1 + \frac{V_2}{2}$$

$$\frac{2R_2}{R_1 + R_2} = \frac{1}{2} \Rightarrow R_1 + R_2 = 4R_2 \Rightarrow R_1 = 3R_2 \Rightarrow R_1/R_2 = 3$$

(20)

For the circuit

$$\frac{V_o}{V_{in}} = ?$$


$$V_a = V_{in} \quad \frac{0 - V_{in}}{R} = \underline{\underline{z}} = \frac{V_{in} - z}{R}$$

$$2V_{in} = z$$

$$2V_{in} = \frac{1}{3}(V_{int} + V_o)$$

$$6V_{in} = V_{int} + V_o$$
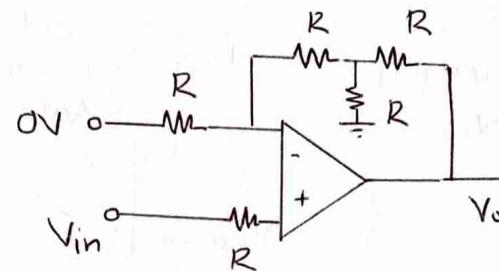
$$5V_{in} = V_o \Rightarrow \frac{V_o}{V_{in}} = 5$$



$$\frac{z - V_{in}}{R} + \frac{z - 0}{R} + \frac{z - V_o}{R} = 0$$

$$z - V_{in} + z + z - V_o = 0$$

$$3z = V_{int} + V_o$$

$$z = \frac{1}{3}(V_{int} + V_o)$$


(21)

$$V_a = \frac{4 \times 100}{200} = 2 \text{ Volt}$$

$$\frac{4 - 2}{100} = \frac{2 - V_o}{99}$$

$$\frac{99}{50} = 2 - V_o \Rightarrow V_o = 2 - \frac{99}{50}$$

$$\Rightarrow V_o = 0.02 \text{ Volt}$$

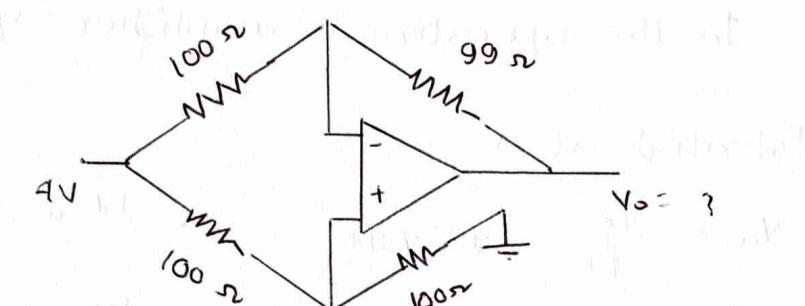


(6)

(22)

$$\text{Given, } V_o = \frac{V_2}{3} - 2V_1$$

The Value of  $R_4$  is
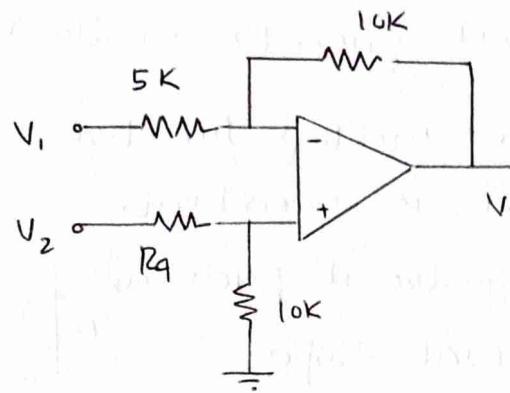
$$\Rightarrow V_a = \frac{V_2 \times 10}{10 + R_4} = \frac{10V_2}{R_4 + 10}$$



$$\frac{V_1 - V_a}{5} = \frac{V_a - V_o}{10}$$

$$\frac{V_2}{3} - 2V_1 = -2V_1 + \frac{3V_2}{R_4 + 10}$$

$$\text{or } 2V_1 - 2V_a = V_a - V_o$$


$$\frac{1}{3} = \frac{30}{R_4 + 10} \Rightarrow R_4 + 10 = 90$$

$$\therefore V_o = -2V_1 + 3V_a$$

$$\Rightarrow R_4 = 80 \Omega$$

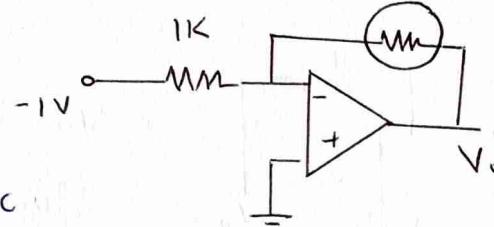- (23) The thermister has a resistance  $3\text{ k}\Omega$  at  $25^\circ\text{C}$ . Its resistance decrease by  $150 \Omega$  per  $^\circ\text{C}$ . upon heating.

The output of the circuit  
at  $30^\circ\text{C}$  will be



Resistance at  $30^\circ\text{C}$  increase  $5\text{ C}$


$$R_f = R_i - \alpha \Delta t = 3000 - (5 \times 150) = 2250 \Omega = 2.25 \text{ k}\Omega$$

$$\frac{-1 - 0}{1} = \frac{0 - V_o}{2.25} \Rightarrow V_o = 2.25 \text{ Volt}$$

- (24) If  $y = \log x$ . The the circuit that can be used to produce an output Voltage  $V_o$  Varying linearly with  $x$  is

$\Rightarrow y = \log x$  so we have to use exponential amplifier



$$x = e^y = V_o$$

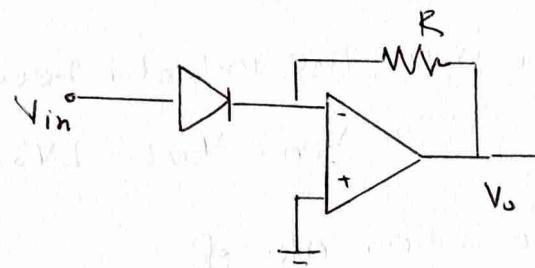



(25) The input given to an ideal OP-AMP integrator circuit is

$\Rightarrow$  This is unistep function and it is constant.

on Integrator it gives a Constant slope.

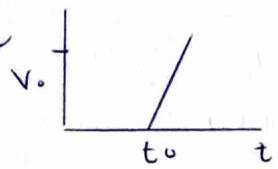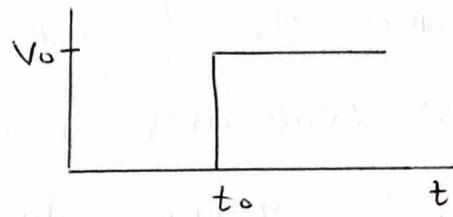


(26)

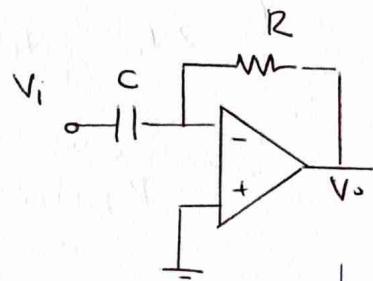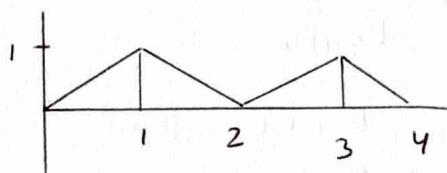

Value of  $RC$  is 1


This is a differentiation
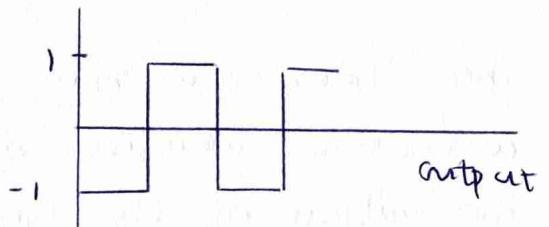
$$V_o = -RC \frac{dV_{in}}{dt} = -\frac{dV_{in}}{dt}$$



output

(27)

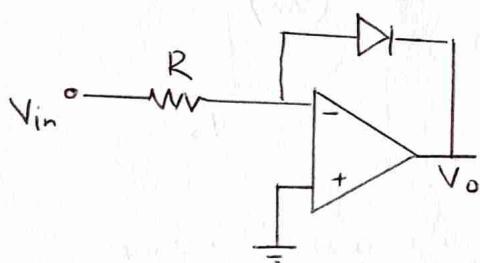


$V_o$  is proportional to

For logarithmic amplifier

$$V_o \propto \ln|V_{in}|$$

(28)

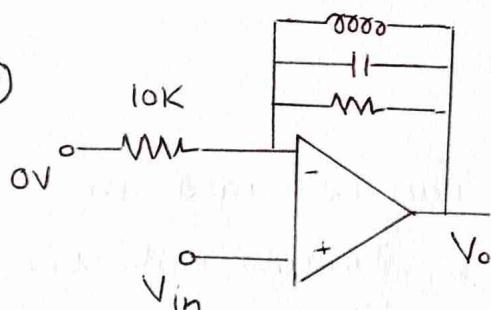

$$L = 1 \text{ mH}$$

$$C = 1 \mu\text{F}$$

$$R = 90\text{K}$$

$$V_{in} = 1 \text{ V DC}$$

For inductor

$$X_L = \omega L$$

$$\text{Capacitor } X_C = \frac{1}{\omega C}$$

$$X_L = 0$$


For Pure DC,  $\omega \rightarrow 0$

AC  $\omega \rightarrow \infty$

As  $X_L$  is 0 the inductor became short circuit

$$\therefore V_{in} = V_{out} = 2 \text{ Volt}$$

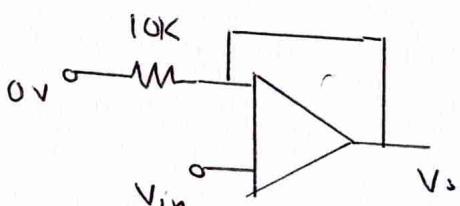There is no role of resistor and capacitor




(29)

(29)

Value of  $I$  will be

$$\frac{x-0}{2} = -1 \Rightarrow x = -2 \text{ Volt}$$

$$i = \frac{0 - (-2)}{2} = 1 \text{ mA}$$

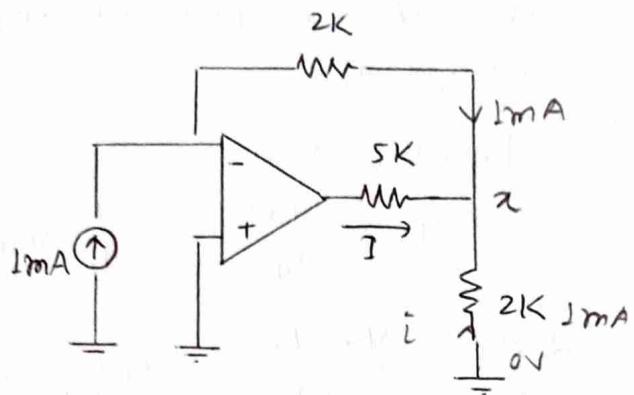Value of  $I$  is  $-2 \text{ mA}$ 

(30)


Value of  $\frac{V_o}{V_i}$  is

$$\frac{V_i - 0}{R} = \frac{0 - x}{4R}$$

$$x = -4V_i$$

$$\text{Potential difference } V_o = V_i - (-4V_i) = 5V_i$$

$$\frac{V_o}{V_i} = 5$$

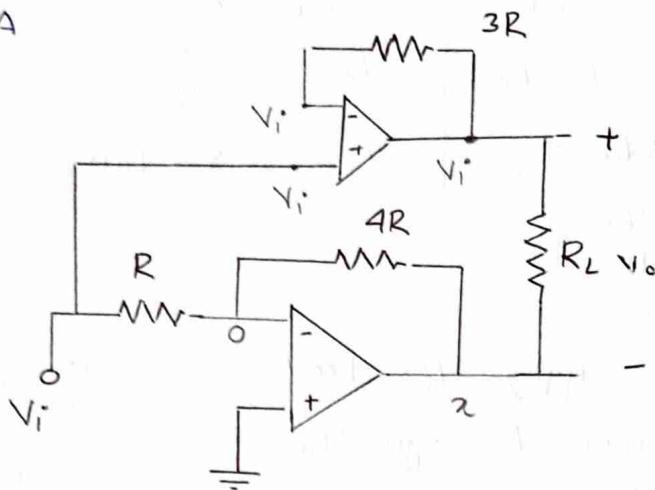

(31)

Value of  $\frac{V_o}{V_1 - V_2}$  is

$$\frac{V_2 - V_1}{R} = \frac{V_1 - y}{R}$$

$$V_2 - V_1 = V_1 - Vy$$


$$Vy = 2V_1 - V_2$$

$$Va = \frac{VyR}{R+R} = \frac{Vy}{2}$$

$$Va - \frac{Vy}{2} = \frac{Vy}{2} - V_o$$

$$V_x - Vy = -V_o$$

$$V_o = Vy - V_x$$

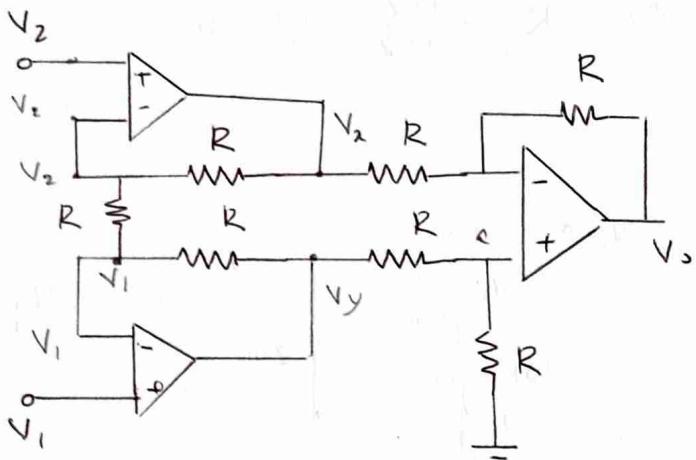

$$\frac{V_x - V_2}{R} = \frac{V_2 - V_1}{R}$$

$$V_x = 2V_2 - V_1$$

$$V_o = 2V_1 - V_2 - 2V_2 + V_1$$

$$V_o = 3V_1 - 3V_2$$

$$\frac{V_o}{V_1 - V_2} = 3$$

(32)

What will be value of output Voltage  $V_o$

$\Rightarrow$  Potential at a.

$$V_a = \frac{10V_o}{10+100} = \frac{V_o}{11} \text{ Volt}$$

$$\frac{2-V_a}{5} = \frac{V_a-V_o}{10}$$

$$4 - 2V_a = V_a - V_o$$


$$V_o = 3V_a - 4$$

$$V_o = \frac{3V_o}{11} - 4$$

$$V_o \left( \frac{3}{11} - 1 \right) = 4$$

$$V_o = -\frac{44}{8}$$

$$V_o = -5.5 \text{ Volt}$$

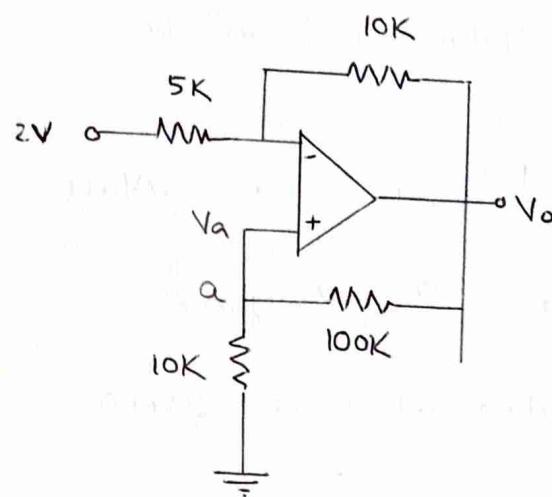

output voltage  
is  $-5.5 \text{ Volt}$

(33)



Input Supply  $V_i = 1 \text{ mV}$ .

The output Voltage  $V_o = ?$

 $\Rightarrow$ 

1K and 2K are in parallel
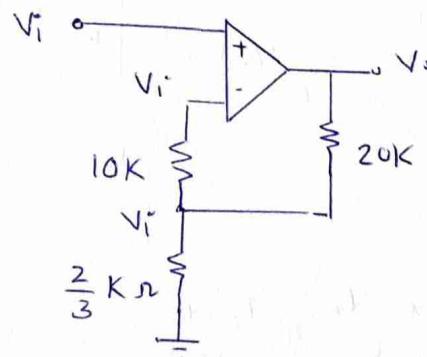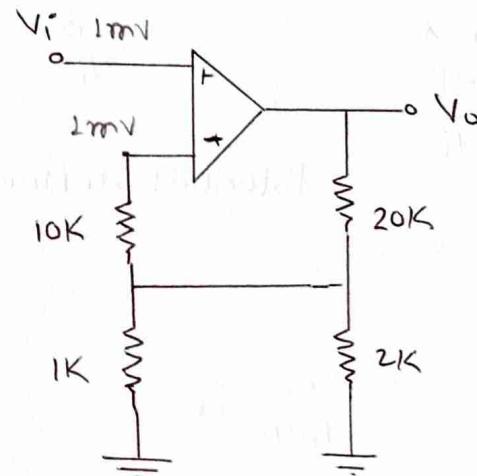
$$\text{So } R = \frac{1 \times 2}{1+2} = \frac{2}{3} \Omega$$



$$V_o = \frac{V_o \times \frac{2}{3}}{20 + \frac{2}{3}} = \frac{2V_o}{62} \approx 1$$

$$V_o = 31 \text{ mVolts}$$


(34)

The output Voltage will be

 $\Rightarrow$ 

$$\frac{1.5 - 0}{22} = \frac{0 - V_o}{100}$$
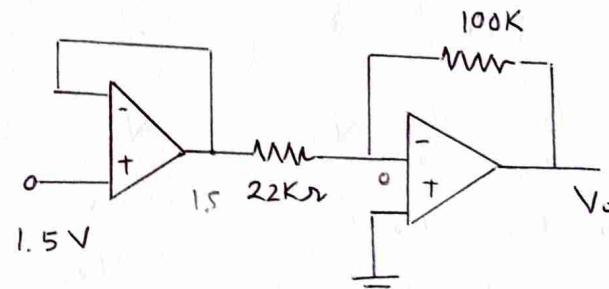
$$V_o = -\frac{1.5 \times 100}{22} = -6.818 \text{ Volt}$$





(10)


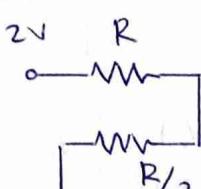
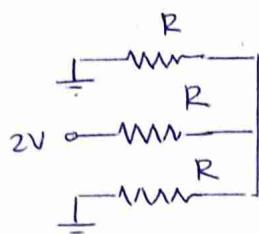
(35)

The output Voltage will be


$\Rightarrow$  From superposition Principle



$$V_1 = \frac{2}{3} V$$

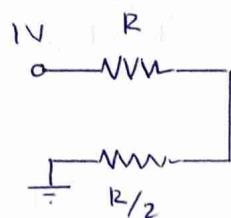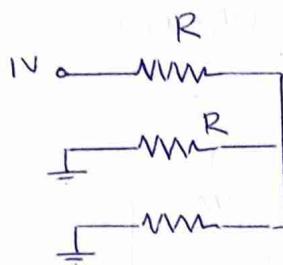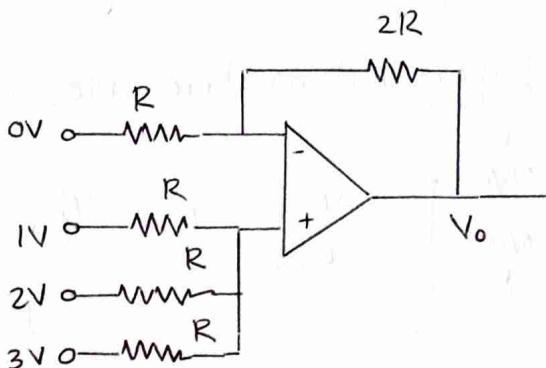
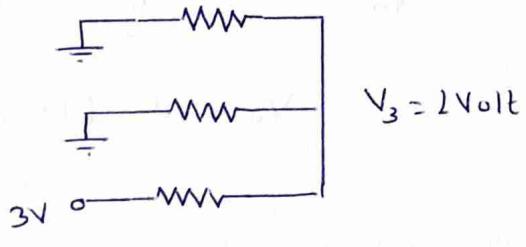
$$V_2 = \frac{1 \times \frac{R}{2}}{R + \frac{R}{2}} = \frac{1}{3} V$$




$$V = V_1 + V_2 + V_3 = \frac{2}{3} + \frac{1}{3} + 1 = 2 \text{ Volt}$$

$$\frac{0-2}{R} = \frac{2-V_o}{2R} \Rightarrow 2-V_o = -4 \Rightarrow V_o = 6 \text{ Volt.}$$

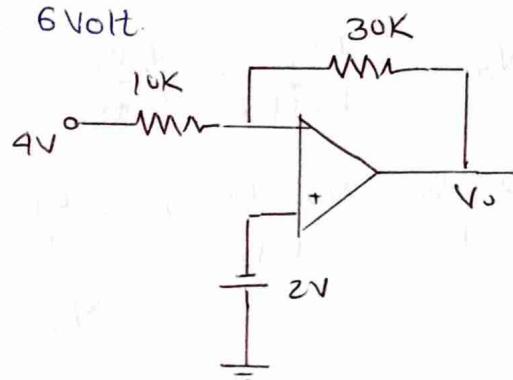(36) Find the output Voltage  $V_o$

$$\Rightarrow \frac{4-(-2)}{10} = -\frac{2-V_o}{30}$$

$$18 = -2-V_o \Rightarrow V_o = -20 \text{ Volt}$$




(37) The output Voltage will be

$$\frac{0-\alpha}{10^7} = 10^{-9} \Rightarrow \alpha = -10^{-2} \text{ Volt}$$

$$\text{Also } \alpha = \frac{V_o \times 1}{1+99}$$

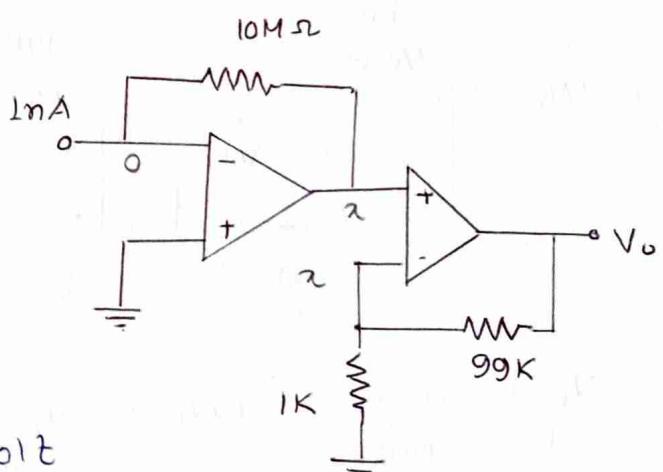
$$\frac{V_o}{100} = -10^{-2} \Rightarrow V_o = 1 \text{ Volt}$$



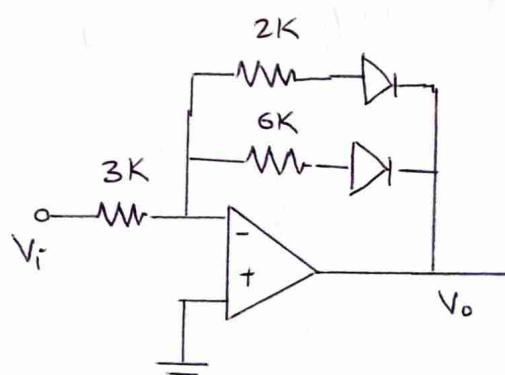(38) If  $V_i = 2V$  then  $V_o = ?$


$$\Rightarrow \frac{V_i-0}{3} = \frac{0-V_o}{6}$$

$$\frac{2}{3} = -\frac{V_o}{6} \Rightarrow V_o = -4 \text{ Volt}$$




③ What will be the output voltage


⇒ By superposition Principle,

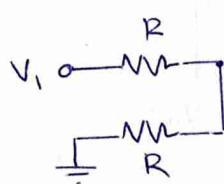
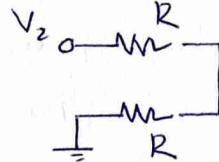
$$\frac{V_1 \times R}{R+R} = \frac{V_1}{2}$$


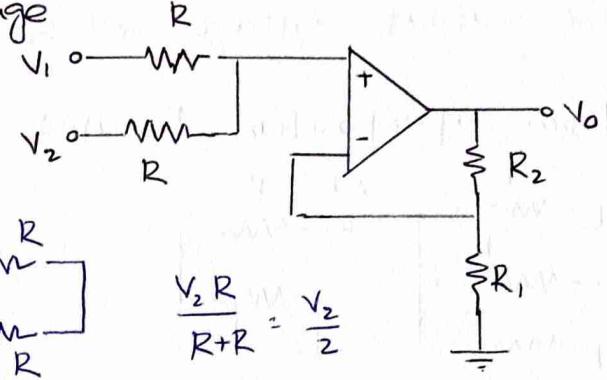
$$\frac{V_2 \times R}{R+R} = \frac{V_2}{2}$$



$$V_a = \frac{V_1}{2} + \frac{V_2}{2} = \frac{1}{2} (V_1 + V_2)$$

Also,


$$\frac{V_o R_1}{R_1 + R_2} = \frac{1}{2} (V_1 + V_2)$$

$$V_o = \frac{1}{2} \left(1 + \frac{R_2}{R_1}\right) (V_1 + V_2)$$

④ What will be the value of  $V_o$

⇒ From Superposition Principle

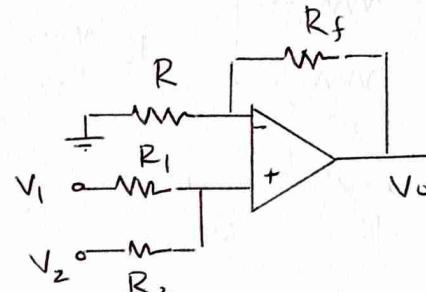
$$V_a = \frac{V_1 R_2}{R_1 + R_2} + \frac{V_2 R_1}{R_1 + R_2} = \frac{V_1 R_2 + V_2 R_1}{R_1 + R_2}$$



$$\frac{0 - V_a}{R} = \frac{V_a - V_o}{R_f} \Rightarrow -\frac{R_f}{R} V_a - V_a = -V_o \Rightarrow V_o = \left(1 + \frac{R_f}{R}\right) V_a$$

$$\Rightarrow V_o = \left(1 + \frac{R_f}{R}\right) \left(\frac{V_1 R_2 + V_2 R_1}{R_1 + R_2}\right)$$

⑤

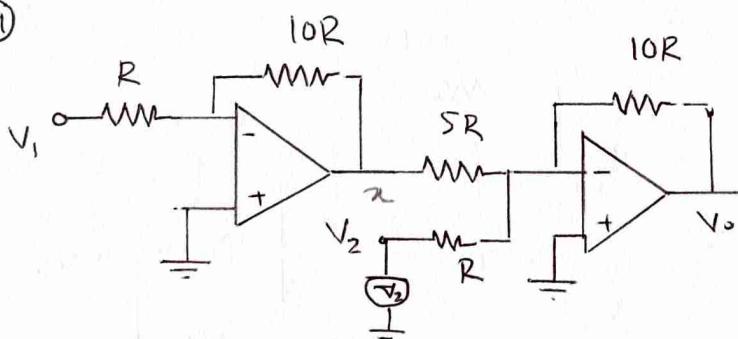

Find the output  
Voltage  $V_o$

$$\Rightarrow \frac{V_1 - 0}{R} = \frac{0 - x}{10R} \quad -\frac{10V_1 - 0}{5R} + \frac{V_2 - 0}{R} = \frac{0 - V_o}{10R}$$

$$x = -10V_1 \quad -2V_1 + V_2 = -\frac{V_o}{10} \Rightarrow V_o = 20V_1 - 10V_2$$


(42) Find the value of  $I_L$

$$\Rightarrow \frac{0-x}{9K} = 0.5 \times 10^{-3}$$

$$x = -4.5 \text{ Volt}$$

$$\text{Now Current } I_L = \frac{0 - (-4.5)}{3.6} \times 10^{-3}$$

$$I_L = 1.25 \text{ mA}$$

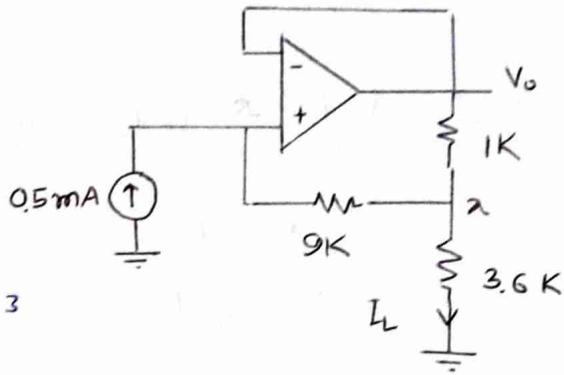

(43) Find the output Voltage  $V_o$

$$\frac{x - V_2}{R_1} + \frac{x - V_2}{R_1} = 0$$


So no

current also  
flows through  
 $R_1$  and  $R_2$

$$x = V_2$$

So  $V_2$  is also equal  
to  $V_o$


$$V_o = V_2$$

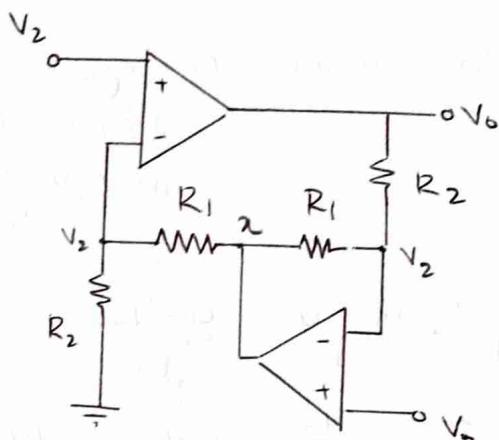

(44)  $V_{o1}$  when S open

$V_{o2}$  when S closed

then  $\frac{V_{o1}}{V_{o2}}$  is

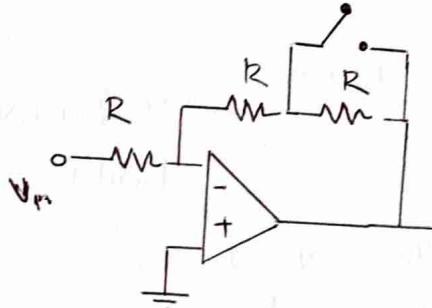

$$\frac{V_{o1}}{V_{o2}} = 2$$


when S is closed

$$\frac{V_{in} - 0}{R} = \frac{0 - V_o}{R} \Rightarrow V_{o2} = -V_{in}$$

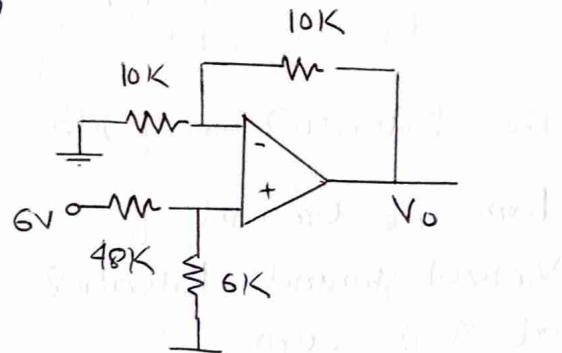(45) output Voltage  $V_o$

$$\Rightarrow V_o = \frac{6 \times 6}{48+6} = \frac{2}{3} V_{in}$$

$$\frac{0 - \frac{2}{3}}{10} = \frac{\frac{2}{3} - V_o}{10} \Rightarrow V_o = \frac{9}{3} \text{ Volt}$$




⑥ Find the output Voltage

$$\frac{O-x}{2} = \frac{x-V_o}{3} \Rightarrow x-V_o = -\frac{3}{2}x$$


$$\Rightarrow \frac{5}{2}x = V_o$$

$$\Rightarrow x = \frac{2}{5}V_o$$
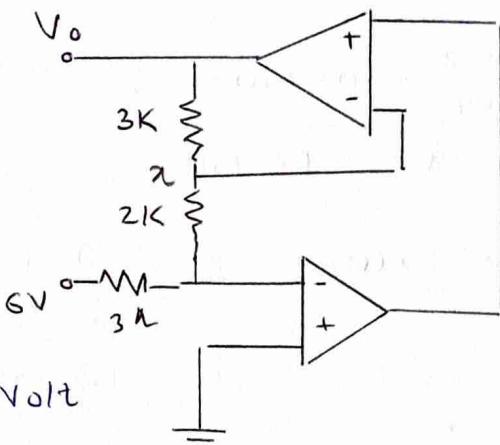
$$\frac{6-O}{3} = \frac{O-x}{2} \Rightarrow x = -4 \quad V_o = -10 \text{ Volt}$$



⑦ The output Voltage is

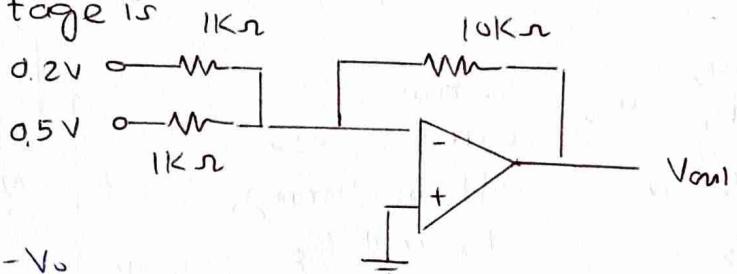

$$\frac{0.2-0}{1} + \frac{0.5-0}{1} = \frac{0-V_o}{10}$$

$$0.7 = -\frac{V_o}{10} \Rightarrow V_o = -7 \text{ Volt}$$

⑧  $R_1 = 120 \Omega$

$R_2 = 1.5 \text{ k}\Omega$

$V_s = 0.6 \text{ V}$


Find  $i$

$$\frac{O-V_s}{R_1} = \frac{V_s-V_o}{R_2}$$

$$V_s - V_o = -\frac{R_2}{R_1} V_s \Rightarrow V_o = \left(1 + \frac{R_2}{R_1}\right) V_s$$


$$\Rightarrow V_o = \left(1 + \frac{1500}{120}\right) \times 0.6 = 8.1 \text{ Volt}$$
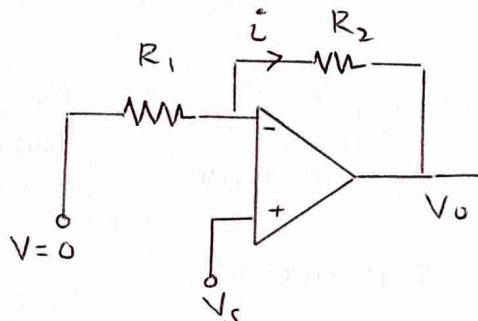
$$i = \frac{V_s - V_o}{R_2} = \frac{0.6 - 8.1}{1.5} = \frac{7.5}{1.5} = 5 \text{ mA}$$



⑨ The Potential at node A is

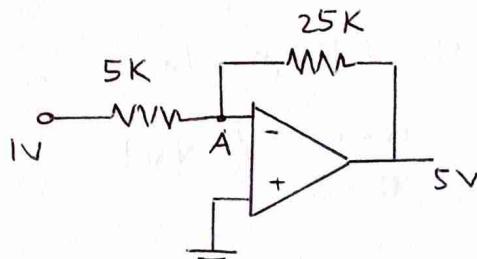From the concept of  
Virtual ground, Potential  
at A is zero.




(50) If  $V_i = 1\text{mV}$  then value of  $V_o$  is

$\Rightarrow$  As no current through  $10K\Omega$

So Potential at 'a' is  $V_i$

$$\text{Now } V_i = \frac{V_o \times \frac{2}{3}}{20 + \frac{2}{3}} = 1$$
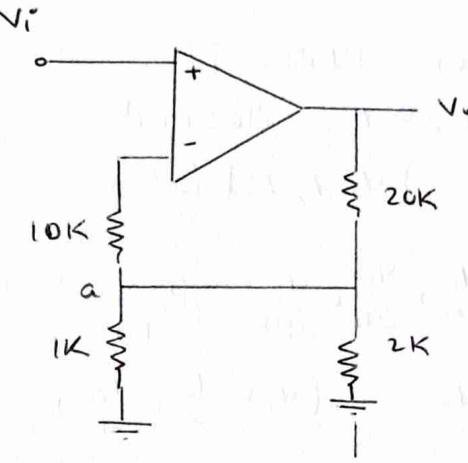
$$\frac{2V_o}{62} = 1 \Rightarrow V_o = 31 \text{ Volt}$$




(51) Find the output Voltage

$\Rightarrow$  As they are grounded Potential

$V_a = 0$  Now

$$\frac{0-0}{R} = \frac{0-V_o}{2R}$$

$$V_o = 0 \text{ Volt}$$

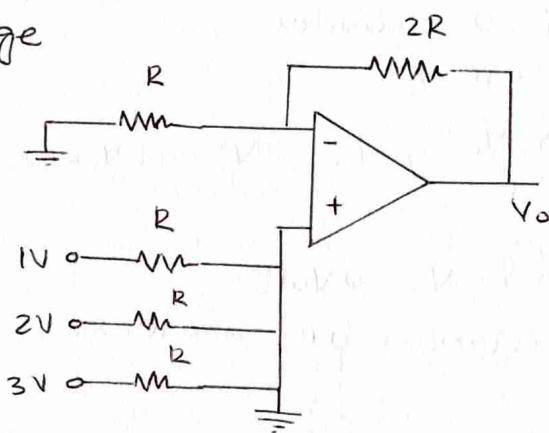

(52) If  $R_1 = 10K\Omega$ ,  $R_2 = 2R_1$ ,

$R_3 = 2R_2$ ,  $R_4 = 2R_3$  then

if  $V_{ref} = 1V$  Then for (0001)  
Vo is equal to

$$\Rightarrow \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} + \frac{V_4}{R_4} = \frac{0-V_o}{R_f} \Rightarrow V_o = -R_f \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} + \frac{V_4}{R_4} \right)$$

$$= -10K \left[ \frac{V_1}{10} + \frac{V_2}{2 \times 10} + \frac{V_3}{4 \times 10} + \frac{V_4}{8 \times 10} \right]$$

$$V_{ref} = 1V$$

$$(0001) \Rightarrow V_4 = 1\text{ Volt}$$

other 0 Volt

$$\Rightarrow V_o = - \left[ V_1 + \frac{V_2}{2} + \frac{V_3}{2^2} + \frac{V_4}{2^3} \right]$$

$$\Rightarrow V_o = - \frac{V_4}{8} = - \frac{1}{8} = -0.125V$$

Case if (101)

$$V_o = - \left( 1 + \frac{1}{2} + 0 + \frac{1}{8} \right) = 1.625$$

if  $V_{ref} = 2\text{ Volt}$


$$(1011) \quad V_1 = 2\text{ Volt} \quad V_3 = 2\text{ Volt}$$

$$V_2 = 0\text{ Volt} \quad V_4 = 2\text{ Volt}$$

(53)  $V_{ref} = 1\text{ Volt}$ . If  
 $|V_o| = 1.25\text{ V}$  is desired  
then  $[V_1, V_2, V_3]$  is

$$\Rightarrow \frac{V_1}{10} + \frac{V_2}{20} + \frac{V_3}{40} = \frac{0 - V_o}{10}$$

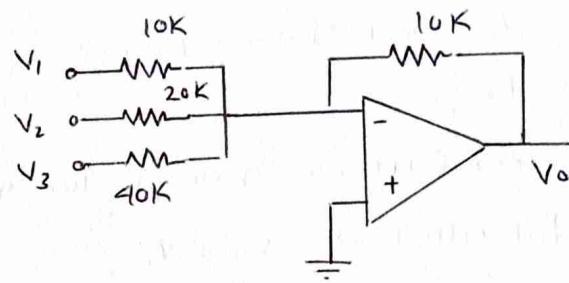or  $V_o = - \left( V_1 + \frac{V_2}{2} + \frac{V_3}{4} \right) = 1.25$




$$\text{So } V_1 = V_3 = 1\text{ Volt}$$

$$V_2 = 0 \text{ So } [101]$$

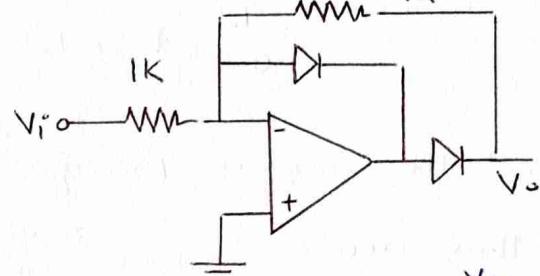
(54) Variation of  $V_o$  and  $V_i$

when  $V_i < 0$  diodes  
are useless

$$\frac{V_o - 0}{1} = \frac{0 - V_i}{1} \Rightarrow V_o = -V_i \quad (V_i < 0)$$




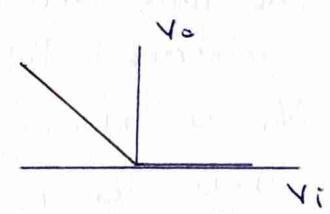when  $V_i > 0$   $V_o = 0\text{ Volt}$   
(Resistances are useless)



(55)  $V_1 = 2.5\text{ V}$   
 $V_2 = 2.25\text{ V}$

Find the output  
Voltage

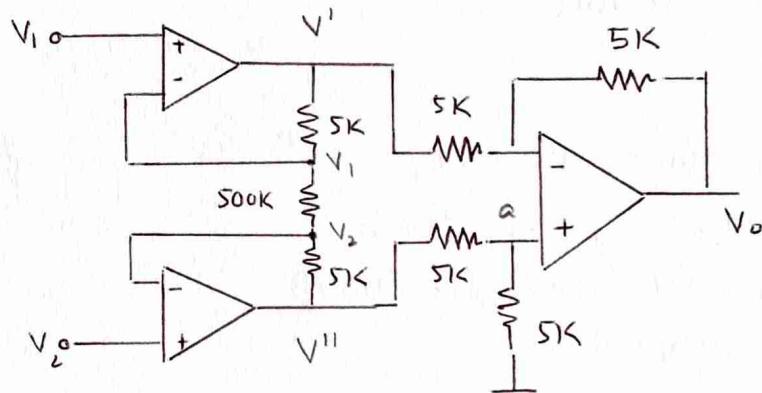

$$\frac{V' - V_1}{5} = \frac{V_1 - V_2}{500}$$

$$\frac{V_1 - V_2}{500} = \frac{V_2 - V''}{5}$$

$$\frac{V' - 2.5}{5} = \frac{2.5 - 2.25}{500}$$

$$\frac{2.5 - 2.25}{500} = \frac{2.25 - V''}{5}$$

$$V' = 2.5025\text{ V}$$

$$V'' = -2.2475\text{ V}$$

$$V_a = -\frac{2.2475 \times 5}{10}$$

$$V_a = 1.12375\text{ Volt}$$

$$\frac{V' - V_a}{5} = \frac{V_a - V''}{5} \Rightarrow 2.5025 - 2 \times (1.12375) = -V''$$

$$\Rightarrow V_o = -0.255\text{ Volt}$$

56 If  $V_o = -V$  the value of  $R_f$  is


Current

$$i = \frac{V}{R} + \frac{2V}{R/2} + \frac{3V}{R/3} + \dots + \frac{nV}{R/n}$$

$$= \frac{V}{R} (1 + 2^2 + 3^2 + \dots + n^2) = \frac{0 \cdot V}{R_f}$$

$$R_f = \frac{R}{(1 + 2^2 + 3^2 + \dots + n^2)}$$

$$R_f = \frac{6R}{n(n+1)(2n+1)}$$

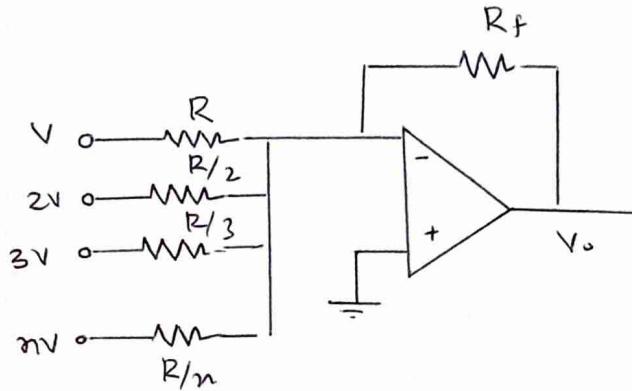

(as  $V_o = -V$ )


57 Find the value of current  $I_L$

$$\frac{V_x - V_i}{R} + \frac{V_x - 0}{R_L} + \frac{V_x - V_o}{R} = 0$$

$$V_x \left( \frac{1}{R} + \frac{1}{R_L} + \frac{1}{R} \right) = \frac{V_o}{R} + \frac{V_i}{R}$$

$$V_x = \frac{\left( \frac{V_o}{R} + \frac{V_i}{R} \right)}{\left( \frac{2}{R} + \frac{1}{R_L} \right)} = \frac{V_o}{2}$$
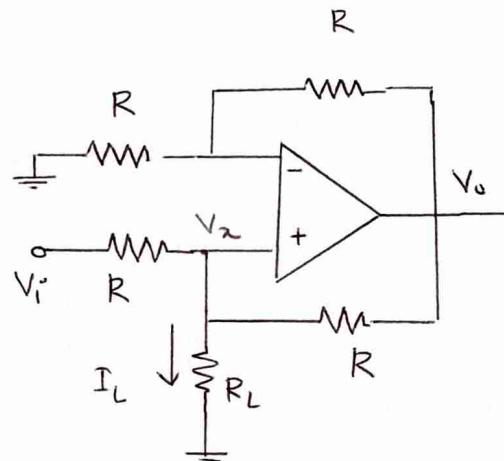
$$\frac{V_o}{R} + \frac{V_i}{R} = \frac{V_o}{R} + \frac{V_o}{2R_L}$$



$$\frac{V_o - V_x}{R} = \frac{V_x - 0}{R} \Rightarrow V_x = \frac{V_o}{2}$$

$$\frac{V_i}{R} = \frac{V_o}{2R_L}$$

$$V_o = \frac{2R_L}{R} V_i$$

$$I_L = \frac{V_x}{R_L} = \frac{V_o}{2R_L} = \frac{V_i}{R}$$

58 Find the value  $\frac{V_o}{I_s}$

$$\frac{x-y}{2} + \frac{x-y}{4} + \frac{x}{10} = 10 \Rightarrow 13x = 15y$$

$$\Rightarrow y = \frac{17}{15}x$$

$$\frac{x-y}{2} - I_s = 0 \Rightarrow x = \frac{15}{17}y$$


$$x-y = 2I_s$$

$$-\frac{2}{17}V_o = 2I_s$$

$$x-V_o = 2I_s$$

$$\frac{V_o}{I_s} = 17$$

$$(\frac{15}{17} - 1)V_o = 2I_s$$

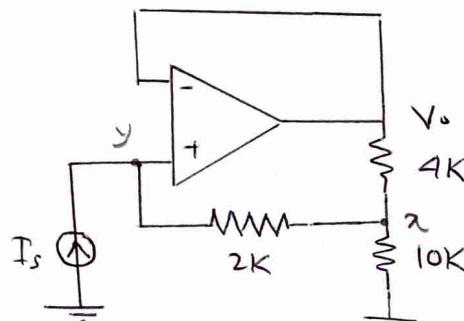

## Frequency Responses of Filters


### ① Capacitor:

Reactance of capacitor

$$X_C = \frac{1}{\omega C} \quad \text{if } \omega \rightarrow \infty, X_C \rightarrow 0$$

$$\omega \rightarrow 0 \quad X_C \rightarrow \text{High (DC)}$$

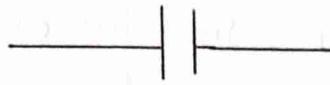In DC, Capacitor Provide high resistance, blocked DC and Passes the AC signal



### ② Inductor:

Reactance of inductor  $X_L = \omega L$

$$\text{For DC } \omega \rightarrow 0$$

$$X_L \rightarrow 0$$


$$\text{For AC } \omega \rightarrow \infty$$

$$X_L \rightarrow \infty$$



Inductor blocks AC signals and Passes DC signals

### ③ Low Pass Filters:

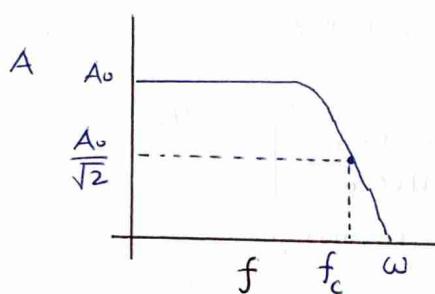

$$\text{Gain, } A = \frac{V_o}{V_i}$$


$f_c$  is cut off frequency / Highest frequency

It Passes Low frequency and blocks high frequency  $\Rightarrow$  Low Pass filters.

$f < f_c \Rightarrow$  Passes the signal

$f > f_c \Rightarrow$  Blocked the signal

### ④ High Pass Filters:

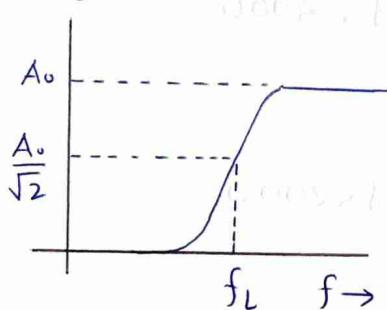

$f < f_L \Rightarrow$  Blocked the signal

$f > f_L \Rightarrow$  Passes the signal


It Passes the high frequency Signals  $\Rightarrow$  High Pass Filters

### ⑤ Band Pass Filters

$0 < f < f_L \Rightarrow$  Blocked

$f_H < f < \infty \Rightarrow$  Blocked

$f_L < f < f_H \Rightarrow$  Passes


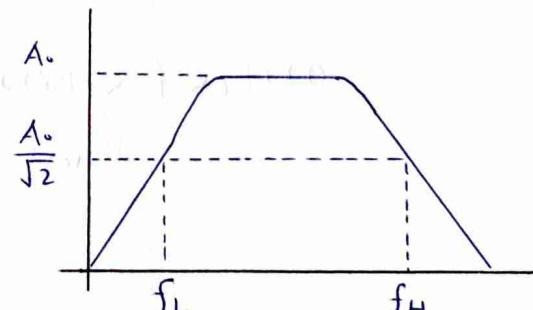


## ⑥ Band Reject Filter

$0 < f < f_H$  Passes

$f_L < f < \infty$  Passes

$f_H < f < f_L$  Signal blocked

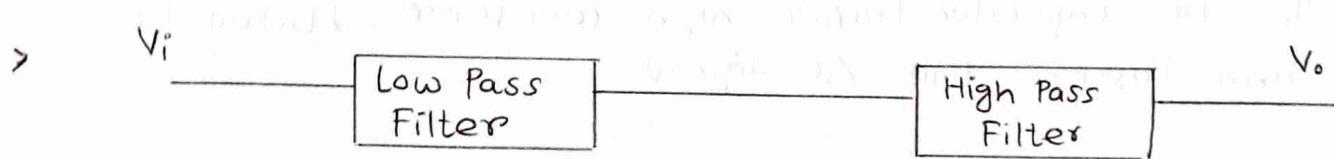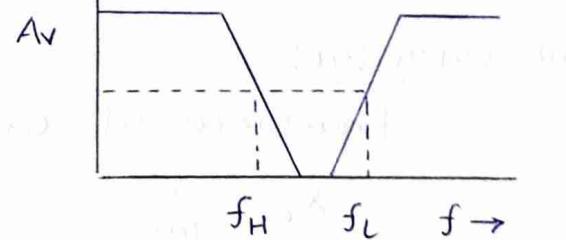

$$f_H = 2000 \text{ Hz}$$

↓

$f < 2000 \text{ Hz}$  allowed


$f > 2000 \text{ Hz}$  Blocked

$$f_L = 4000 \text{ Hz}$$

$f > 4000 \text{ Hz}$  pass


$f < 4000 \text{ Hz}$  Blocked

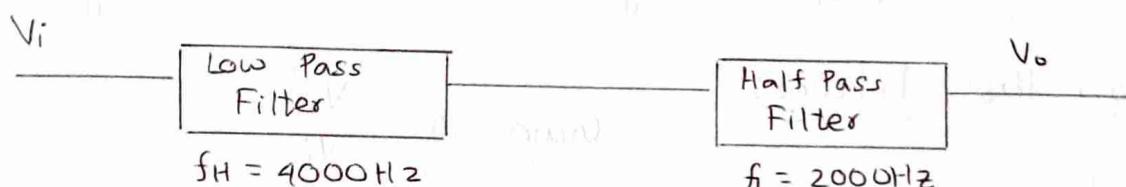∴ No output will Pass  $\Rightarrow$  No Pass Filter



$$f_H = 4000 \text{ Hz}$$


$$f_L = 2000 \text{ Hz}$$

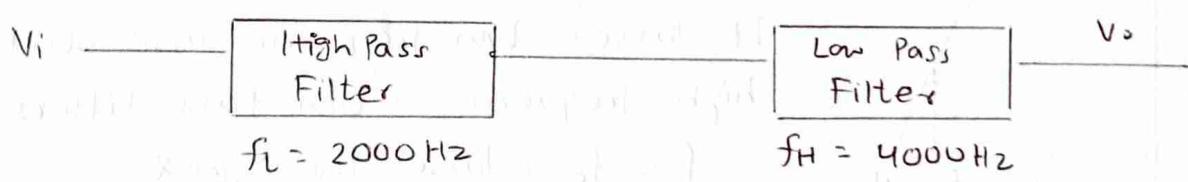

$$f_L = 2000 \text{ Hz}$$

$$f_H = 4000 \text{ Hz}$$

Both are Band Pass Filter.

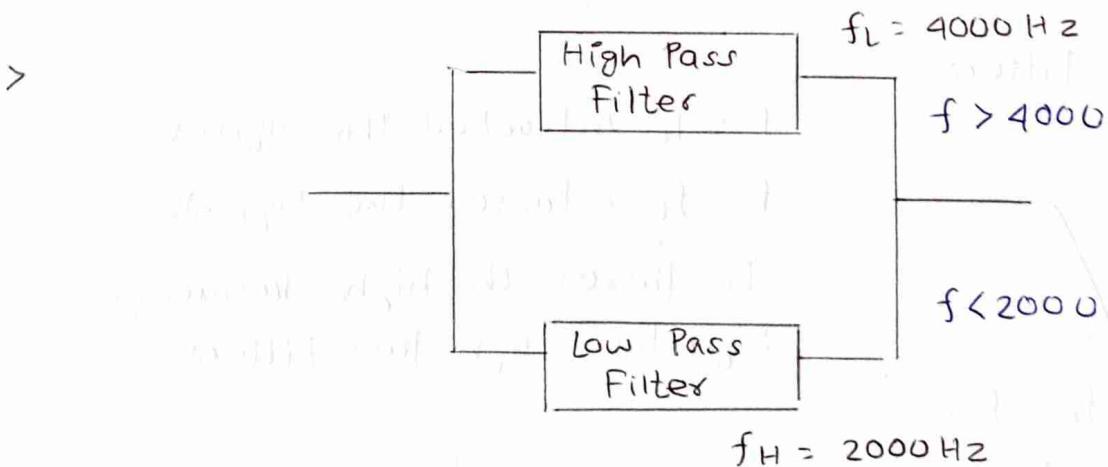

$$f_L = 4000 \text{ Hz}$$


$f > 4000$

$f < 2000$

$$f_H = 2000 \text{ Hz}$$

$2000 \text{ Hz} < f < 4000 \text{ Hz}$  Be rejected

Band Rejecting Filter

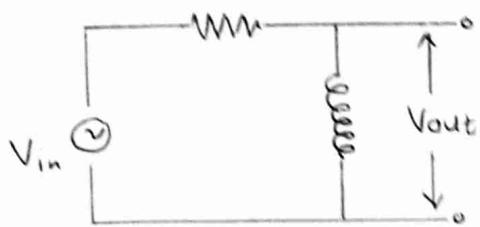

$$V_{in} = i(R + \omega L)$$




$$V_{out} = i\omega L$$

$$A = \frac{i\omega L}{(R + \omega L)i} = \frac{\omega L}{R + \omega L} = \frac{1}{1 + \omega^2 L^2}$$

$$\frac{V_o}{V_{in}} = \frac{R}{R + j\omega L}$$

$$\frac{V_o}{V_{in}} = \frac{R}{\sqrt{R^2 + \omega^2 L^2}}$$
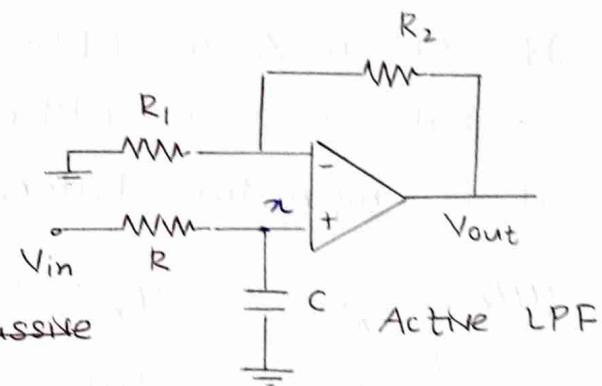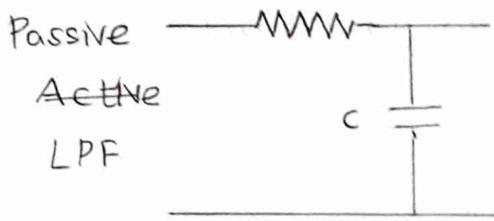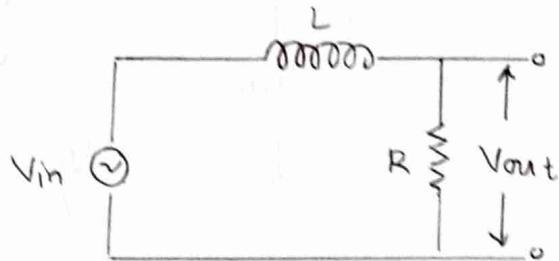
$$A = \frac{1}{\sqrt{1 + \omega^2 L^2}}$$



$$\chi = \frac{V_{in} \cdot \frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{V_{in} \cdot \frac{1}{sC}}{R + \frac{1}{sC}}$$

Here  $s = j\omega$

$$\chi = \frac{V_{in}}{sCR + 1} = \frac{V_{in}}{1 + \omega^2 L^2}$$

$$\frac{V_o - 0}{R_1} = \frac{V_o - \chi}{R_2}$$

$$\frac{V_o}{V_{in}} = \frac{(1 + R_2/R_1)}{(1 + s\tau)}$$

$$V_o = \left(1 + \frac{R_2}{R_1}\right) \frac{V_{in}}{(1 + \omega^2 L^2)}$$

(Low Pass Filter)

HPF:

$$\chi = \frac{V_{in} \cdot R}{R + \frac{1}{j\omega C}} = V_o$$


$$A = \frac{V_o}{V_{in}} = \frac{R + \frac{1}{j\omega C}}{R}$$

$$A = 1 + \frac{1}{\omega CR}$$

$$\omega \rightarrow \infty, A \rightarrow 1$$

$$\omega \rightarrow 0, A \rightarrow \infty$$

only passed  
High frequency

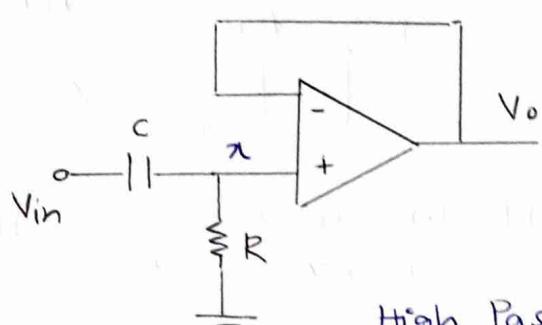


High Pass  
Filters


## ⑦ All Pass Filter:

Allows all frequency

Gain is Constant

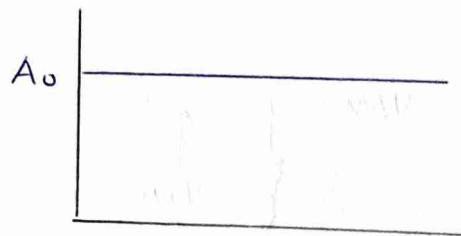

HPF:

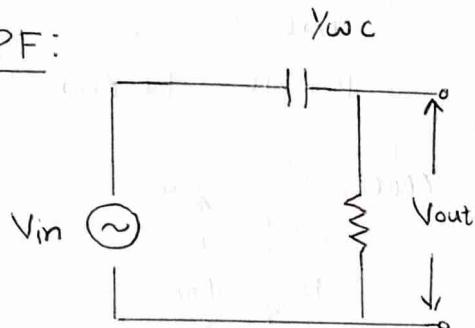

$$V_{out} = iR$$

$$V_{in} = i \left( \frac{1}{\omega_c} + R \right)$$

$$\frac{V_o}{V_i} = \frac{R}{\frac{1}{\omega_c} + R} = \frac{R\omega_c}{1 + R\omega_c}$$

$$\text{Gain, } A = \frac{V_o}{V_i} = \frac{R\omega_c}{1 + R\omega_c} = \frac{2\omega}{2 + 1}$$


$$A = \frac{\omega}{2 + 1}$$

If.  $\omega \rightarrow 0$ ,  $A = 0$  (Blocked Low frequency)

$\omega \rightarrow \infty$ ,  $A = 1$  (Blocked Low, Pass High)

So it is high Pass Filters

LPF

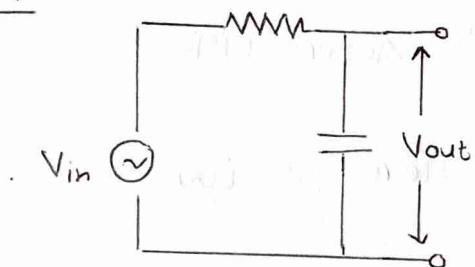


$$V_{in} = i \left( R + \frac{1}{\omega_c} \right)$$

$$V_{out} = i \cdot \frac{1}{\omega_c}$$

$$A = \frac{\frac{1}{\omega_c}}{\frac{RC\omega + 1}{\omega_c}} = \frac{1}{1 + 2\omega}$$

$\omega \rightarrow \infty$ ,  $A \rightarrow 0$  (Blocked High frequency)

Low Pass filters.

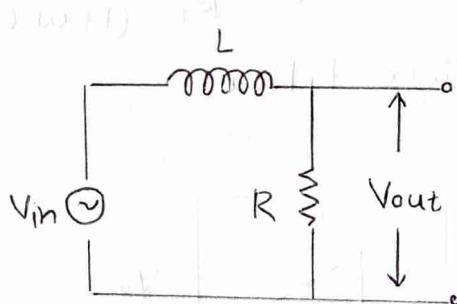

$$V_{in} = i \left( R + \omega L \right)$$

$$V_{out} = iR$$

$$A = \frac{iR}{iR + \omega L} = \frac{1}{1 + \frac{\omega L}{R}} = \frac{1}{1 + \omega^2 R^2}$$

If  $\omega \rightarrow 0$ ,  $A = 1$

$\omega \rightarrow \infty$ ,  $A = 0$

It is a low Pass Filters

## LPF

$$x = \frac{V_{in}R}{R+j\omega L} = V_o$$


$$\frac{V_{in}R}{R+sL} = V_o$$

$$A = \frac{V_o}{V_{in}} = \frac{1}{1+\zeta s}$$

$$s \rightarrow 0 \quad A = 1$$

$$s \rightarrow \infty \quad A = 0$$


Active  
Low Pass  
Filter

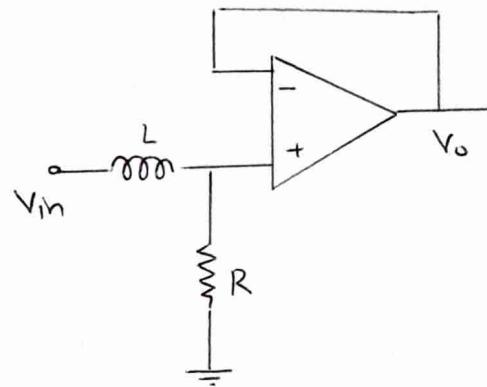
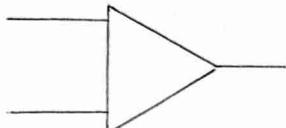
## Slew Rate:

Rate of change of output Voltage with time is called slew rate

output lags with input  
(time  $10^{-6}$  sec)




## Number System

### Binary to decimal & Decimal to Binary

$$(713)_{10} = (1011001001)_2$$

Now

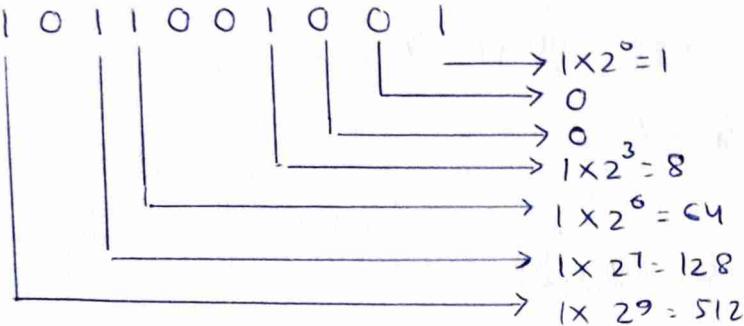

By adding them, we get  $(713)_{10}$

2	713	1
2	356	0
2	178	0
2	89	1
2	44	0
2	22	0
2	11	1
2	5	1
2	2	0
		1

### Octal System

$$(01234567)_8$$

$$(713)_{10} = (1311)_8$$

$$1 \quad 3 \quad 1 \quad 1 \quad 1 \times 8^0 = 1$$

$$1 \times 8^1 = 8$$

By adding  
them  $(713)_{10}$

$$3 \times 8^2 = 192$$

$$1 \times 8^3 = 512$$

8	713	1
8	89	1
8	11	3
		1

### Hexadecimal

$$(0 \ 1 \ 2 \ 3 \ 4 \ 5 \ 6 \ 7 \ 8 \ 9 \ A \ B \ C \ D \ E \ F)_{16}$$

$$(713)_{10} = (2C9)_{16}$$

Binary of  
 $(713)_{10}$

$$(0010 \ 1100 \ 1001)_2$$

16	713	9
16	44	12
		2

① If  $7_n \times 8_n = (38)_n$  then the value of  $n$  is

$$\Rightarrow (7)_n = 7 \times n^0 = 7 \quad (7)_n \times (8)_n = 7 \times 8 = 56$$

$$(8)_n = 8 \times n^0 = 8$$

$$56 = 3n + 8$$

$$38 \rightarrow 8 \times n^0 = 8$$

$$3n = 48$$

$$\rightarrow 3 \times n^1 = 3n$$

$$n = 16$$

② The binary no of  $(2^n - 1)$  is

$$\Rightarrow (0111 \ 1111 \ 1111)_2 \quad 2^0 = 1 = 1 \quad 1 \\ 2^1 = 2 = 1 \quad 1 \\ 2^2 = 4 = 1 \quad 1 \\ 2^3 = 8 = 1 \quad 1$$

③  $(21)_3 = \sqrt{(100)_x}$  the value of  $x$  is

$$\Rightarrow (21)_3 = (2 \times 3^1) + (1 \times 3^0) = 6 + 1 = 7$$

$$49 = (100)_x \Rightarrow x = 7$$

④ Binary equivalent of 9.625

$$\Rightarrow (9)_{10} = (1001)_2 \quad 0.625 \times 2 = 1.250$$

$$0.250 \times 2 = 0.500$$

$$0.500 \times 2 = 1.000$$

$$0.000 \times 2 = 0.$$

$$(9.625)_{10} = (1001.101)_2$$

⑤ The octal equivalent of  $(49.5)_{10}$  is

$$\Rightarrow 0.5 \times 8 = 4.0$$

$$(49.5)_{10} = (61.4)_8$$

$$\begin{array}{r} 8 | 49 | 1 \\ \hline 6 \end{array}$$

⑥ If  $(211)_x = (152)_8$  the value of  $x$  is

$$\begin{array}{l} 211 \\ \swarrow \quad \rightarrow 1 \times x^0 = 1 \\ \swarrow \quad \rightarrow 1 \times x = x \\ \swarrow \quad \rightarrow 2 \times x^2 = 2x^2 \end{array}$$

$$(211)_x = (2x^2 + x + 1)_{10}$$

$$2x^2 + x + 1 = 106$$

$$2x^2 + x - 105 = 0$$

$$\begin{array}{l} 152 \\ \swarrow \quad \rightarrow 2 \times 8^0 = 2 \\ \swarrow \quad \rightarrow 5 \times 8^1 = 40 \\ \swarrow \quad \rightarrow 1 \times 8^2 = 64 \end{array}$$

$$(152)_8 = (106)_{10}$$

$$x = \frac{-1 \pm \sqrt{1+890}}{2 \times 2} = \frac{-1 + \sqrt{890+1}}{2 \times 2} = \frac{28}{4} = 7.$$

⑦ In a particular no system a cubic equation  $x^3 + bx^2 + cx - 190 = 0$  has roots  $x=5$ ,  $x=8$  and  $x=9$  on a base of 10. The base of the number system is

$$\Rightarrow \text{product of roots} = -\frac{d}{a} \quad a \quad x^3 + 24x^2 - 19x - 360 = 0$$

$$\text{sum of roots} = \frac{c}{a} \quad x(x+24) - 15(x+24) = 0$$

$$5 \times 8 \times 9 = (190)_r \quad \text{or } (x+24)(x-15) = 0$$

$$a \quad 360 = x^2 + 9x \quad x = 15 \quad \text{Base of the}$$

$$a \quad x^2 + 9x - 360 = 0 \quad \text{System is 15}$$

⑧ Consider the equation  $(43)_x = (73)_8$ . The no of possible solution is

$$\Rightarrow (43)_x = (4x+3) \quad (73)_8 = 3 + 8y$$

$$8y+3 = 4x+3 \Rightarrow x = 2y \quad (43)_x \Rightarrow x > 4$$

$$x > 4 \quad y < 8 \quad (73)_8 \Rightarrow y < 8$$

2	1	(No)
4	2	(No)
6	3	(Yes)
8	4	(Yes)
10	5	(Yes)
12	6	(Yes)
14	7	(Yes)

Their are 5 possible solutions

⑨ Given  $\sqrt{41} = 5$  is correct in at least one no system  
is the base of the no

$$\Rightarrow (41)_r = (5 \times 5)_r \quad \text{Base of the no system is 6}$$

$$4r+1 = 25$$

$$4r = 24$$

$$r = 6$$

⑩  $(-64)_{10} + (64)_8 = (x)_{10}$  the value of  $x$  is

$$\Rightarrow -64 + (48+4) = x \Rightarrow x = -12$$

⑪ Value of  $\sqrt{(121)_8} = (11)_r$  value of  $r$  is

$$\Rightarrow (121)_8 = (11)_r (11)_8 \text{ so the value does not depend on } r.$$

$$r^2 + 2r + 1 = (r+1)^2 \quad \text{Any value greater than 2}$$

⑫  $(123)_5 = (xy)_8$ .  $x$  and  $y$  are unknown possible  
Value of Solution are

$$\begin{array}{lll} \Rightarrow 25 + 10 + 3 = xy + 8 & 3 & 10 \\ & 2 & 15 \\ xy = 30 & y > x & 1 & 30 \\ & y > 8 & \end{array} \quad \begin{array}{l} \text{Three value} \\ \text{is} \\ \text{possible} \end{array}$$

⑬ The no  $N$  of base  $r$  is represented as  $(N)_r$

$$(10)_{16}^3 = (x)_{10}^2 \text{ The Value of } x \text{ is}$$

$$\Rightarrow (10)_{16}^3 = [1 \times 16^1 + 0 \times 16^0]^3 = 16^3 \quad x^2 = 16^3$$

$$(x)_{10}^2 = [x \times 10^0]^2 = x^2 \quad x = 64$$

⑭  $(125)_R = (203)_5$ . The Value of  $R$  is

$$\Rightarrow (125)_R = R^2 + 2R + 5 \quad (203)_5 = 50 + 0 + 3 = 53$$

$$R^2 + 2R + 5 = 53 \quad R^2 + 8R - 48 = 0$$


$$R^2 + 2R - 48 = 0 \quad R(R+8) - 6(R+8) = 0 \Rightarrow R = 6$$

⑮ Find the Value of  $b$   $\frac{(54)_b}{(4)_b} = (13)_b$

$$\frac{5b+4}{4} = b+3 \Rightarrow 5b+4 = 4b+12 \\ \Rightarrow b = 8$$

# Digital Electronics


Based on digital signal

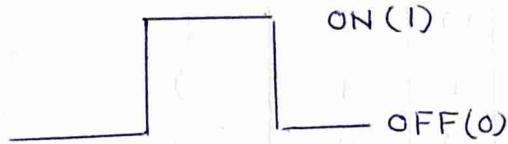

## Logic Gates

### ① NOT Gate:

A	$Y = \bar{A}$	$\bar{Y} = \bar{\bar{A}}$
0	1	0
1	0	1

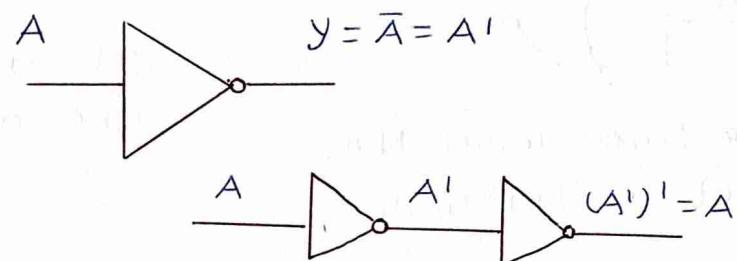


(It has single input)

$$(\bar{\bar{A}}) = A$$


### ② AND Gate:

A	B	$Y = A \cdot B$
0	0	0
0	1	0
1	0	0
1	1	1

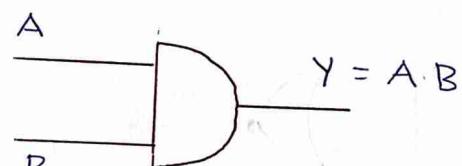


If any of input is low, output will be low.

A	A	$Y = A \cdot A$
0	0	0
1	1	1

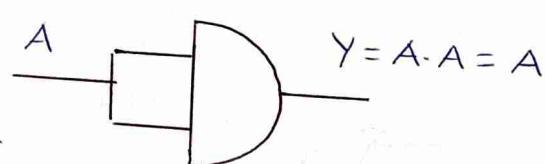


### ③ OR Gate:

A	B	$Y = A + B$
0	0	0
0	1	1
1	0	1
1	1	1

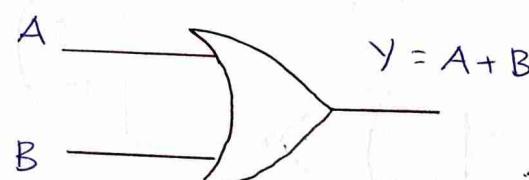


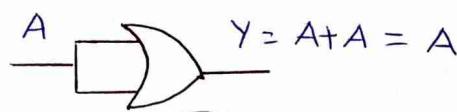If any input is high, the output will be high.





#### ④ NOR Gate:


A	B	$A+B$	$Y = \overline{A+B}$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

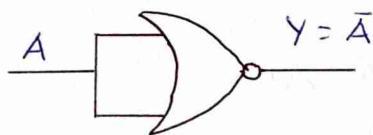


For same input NOR act as NOT Gate.

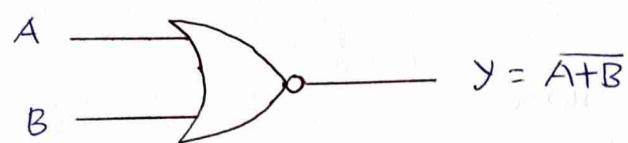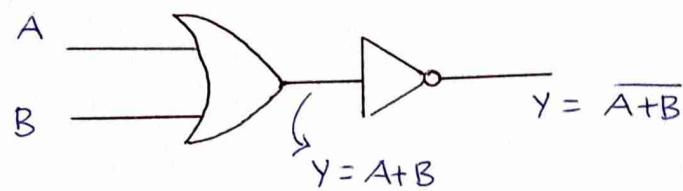

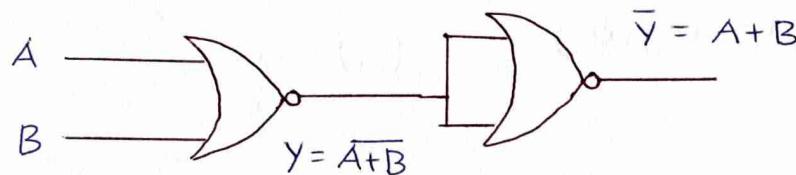
If any of the input is high the output will be low



OR Gate by using NOR Gate

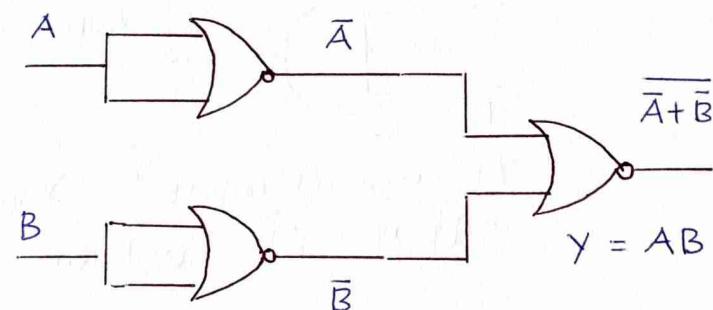



AND Gate by using NOR Gate

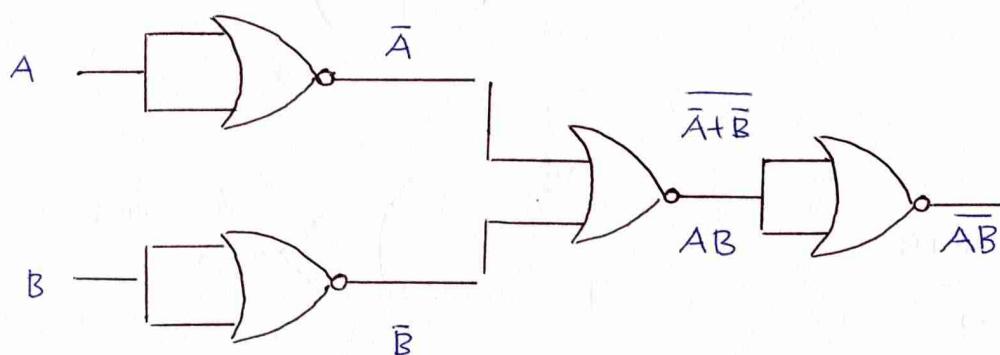

NAND Gate by using NOR Gate



## ⑤ NAND Gate

A	B	AB	$\bar{AB}$
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

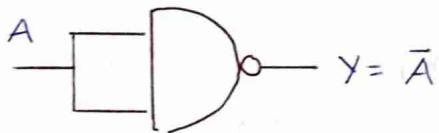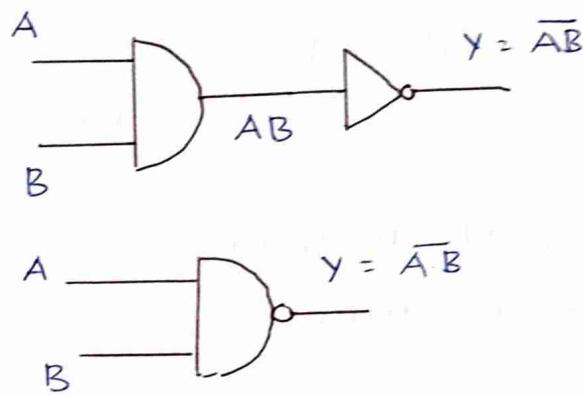

if any of the input is low output will be high

NOT by NAND gate

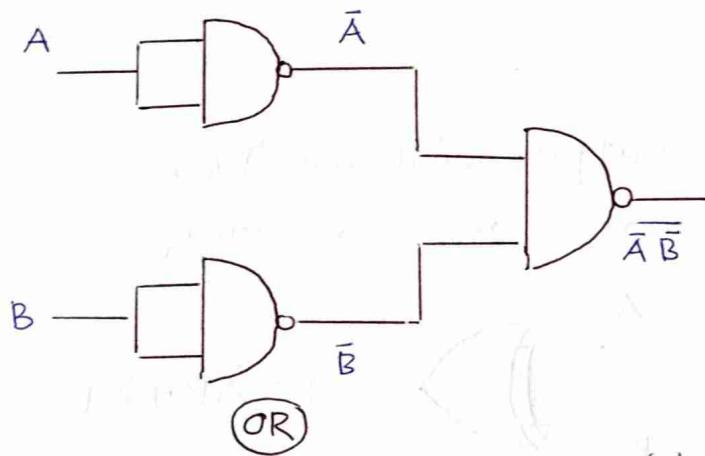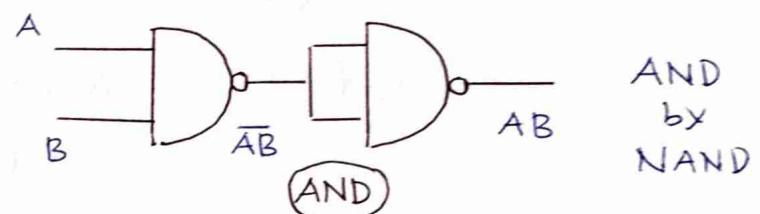


$$A+B = \overline{\overline{A}\overline{B}}$$

$$A \cdot B = \overline{\overline{A}+\overline{B}}$$

(De-Morgan's Law)

(Break the line & change  
the sign)

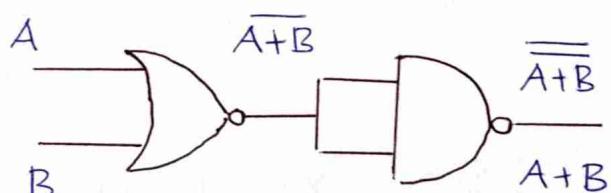


The logic circuit  
is equivalent to OR  
gate

② To design  $A + A\bar{B} + A\bar{B}C$  what should be the minimum number is required

$$\Rightarrow A + A\bar{B} + A\bar{B}C$$

$$= A + A\bar{B}(1+C) = A + A\bar{B} = A(1+\bar{B}) = A$$

so 2 NAND Gate  
is required:

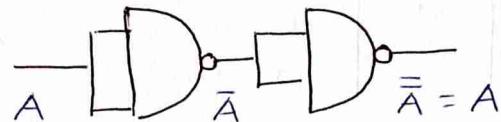

③  $y = \overline{(X \cdot \bar{Y}) + (\bar{X} \cdot Y)}$  is equivalent to

$$\Rightarrow = \overline{(X \cdot \bar{Y})} \cdot \overline{(\bar{X} \cdot Y)}$$


$$\bar{X}\bar{\bar{X}} = 0 \\ Y\bar{Y} = 0$$

$$= (\bar{X}+Y)(X+\bar{Y}) = \bar{X}X + \bar{X}\bar{Y} + XY + Y\bar{Y} \\ = XY + \bar{X}\bar{Y}$$

### ⑥ Ex-OR Gate

If no of 1 are even output will be low  
1 are odd , , , , High


A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

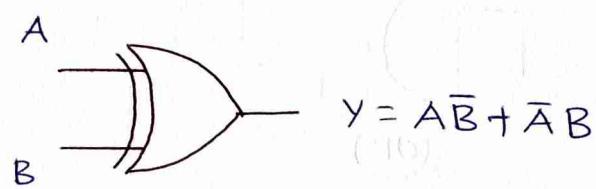

### ⑦ Ex-NOR Gate


A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

$Y = AB + \bar{A}\bar{B}$

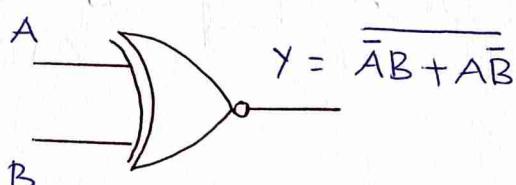

If no of 1 = even: output = 1  
1 = odd: output = 0


⑦ Bubbled AND Gate

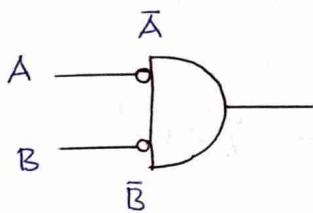

$$Y = \bar{A}\bar{B} = \overline{A+B}$$

(NOR Gate)


⑧ Bubbled OR Gate

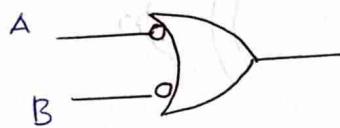

$$Y = \bar{A} + \bar{B} = \overline{AB}$$

(NAND Gate)

Q

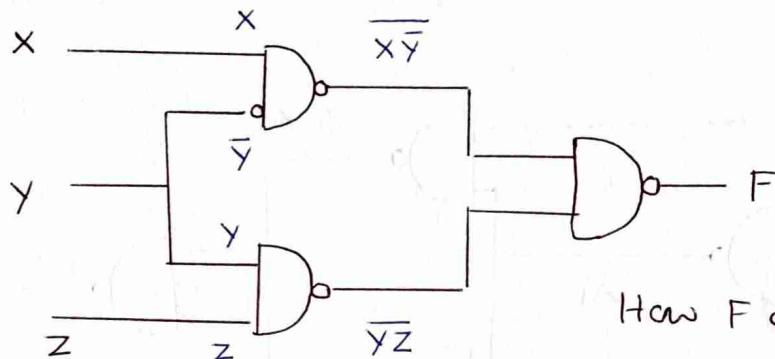

How F depends on  
XYZ

$$F = \overline{\overline{YZ} \cdot \overline{XY}} = \overline{\overline{YZ}} + \overline{\overline{XY}} + YZ + XY$$

(they all dependent)

Q

$$(X \oplus Y) \oplus XY$$

$$= (X\bar{Y} + \bar{X}Y) \oplus XY$$

$$= (X\bar{Y} + \bar{X}Y) \cdot \overline{XY} + (\overline{X\bar{Y} + \bar{X}Y}) XY$$

$$= (X\bar{Y} + \bar{X}Y)(\bar{X} + \bar{Y}) + (\overline{X\bar{Y} + \bar{X}Y}) (\overline{X}Y) XY$$

$$= X\bar{Y} + \bar{X}Y + (\bar{X} + Y)(X + \bar{Y}) XY$$

$$= X\bar{Y} + \bar{X}Y + (\bar{X}\bar{Y} + XY) XY$$

$$= X\bar{Y} + \bar{X}Y + XY$$

$$= X\bar{Y} + Y(X + \bar{X}) = X\bar{Y} + Y = (Y + X)(Y + \bar{Y}) = (X + Y)$$


⊗

$$(A+B)(A+C)$$

$$= A + AC + AB + BC = A(1 + C + B) + BC = A + BC$$


$$\text{so. } (A+B)(A+C) = A + BC$$

(4)

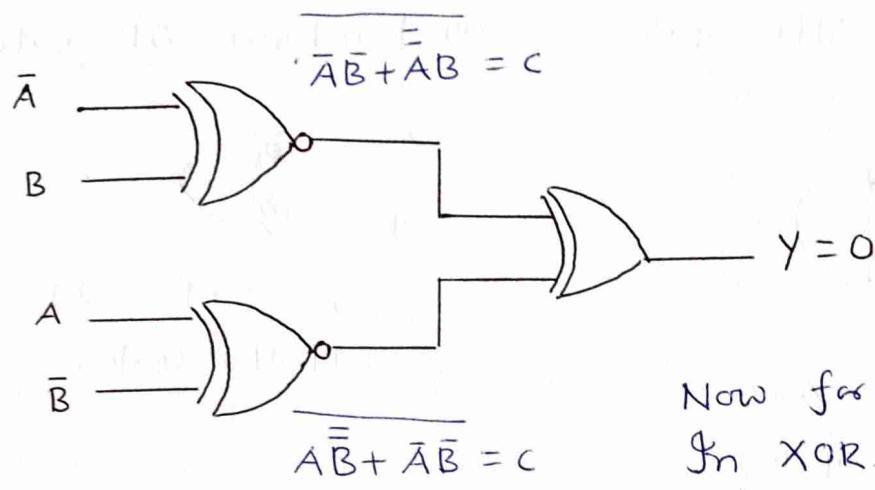

Now for same input  
In XOR output will  
become zero


(5)

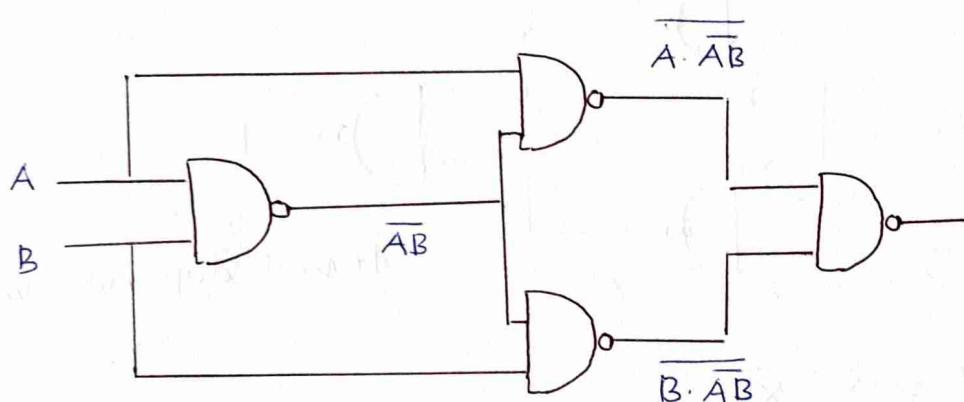

$$\begin{aligned}
 Y &= \overline{\overline{A} \cdot \overline{A}} \cdot \overline{\overline{B} \cdot \overline{B}} = \overline{\overline{A} \cdot \overline{A}} + \overline{\overline{B} \cdot \overline{B}} \\
 &= A \cdot \overline{A} + B \cdot \overline{B} \\
 &= A(\bar{A} + \bar{B}) + B(\bar{A} + \bar{B}) \\
 &= A\bar{B} + \bar{A}B = Y
 \end{aligned}$$

(We can construct  
any gate by NAND/NOR  
so universal gate.)

(6)

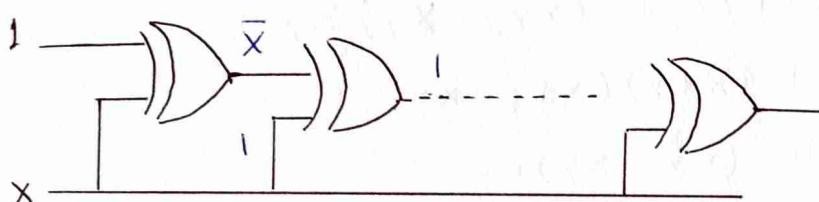

2-bit XOR gate

$$\begin{aligned}
 X\bar{1} + \bar{1}X &= \bar{X} \\
 \bar{X}\bar{X} + XX &= X + \bar{X} = 1
 \end{aligned}$$

Z is even number

In 2nd  $Y = 1$  at 20  $Y = 1$  (also)

## Karnaugh Map

Bar means 0

$$\bar{A} = \bar{B} = \bar{C} = 0$$

### ① 3 Input K Map

A	B	C	Y	
0	0	0	0	0
0	0	1	1	1
0	1	0	1	2
0	1	1	1	3
1	0	0	0	4
1	0	1	1	5
1	1	0	1	6
1	1	1	1	7

	$\bar{B}\bar{C}$	$\bar{B}C$	$BC$	$B\bar{C}$	
$\bar{A}$	0	1	1	1	2
A	4	5	1	7	6

OR

	$\bar{C}$	C
$\bar{A}\bar{B}$	0	1
$\bar{A}B$	1	3
AB	6	7
A $\bar{B}$	4	5

### ② 4 Input K Map

> Remove what changes and take which doesn't change. There A, B changes but C not

> A, C change but B not

$$Y = C + B$$

$$Y = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} + \bar{A}BC + A\bar{B}C + ABC + ABC$$

$$= \bar{B}C + \bar{A}B\bar{C} + \bar{A}B\bar{C} + AB$$

$$= \bar{B}C(1+A) +$$

$$= \bar{B}C + B(A+\bar{A})$$

$$= \bar{B}C + B = (B+\bar{B})(B+C) = B+C$$

$$9) Y = A\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}CD + \bar{A}B\bar{C}D + A\bar{B}\bar{C}D$$

	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
$\bar{A}\bar{B}$		1	1	
$\bar{A}B$		1	1	
AB				
A $\bar{B}$	1	1		

$$Y = \bar{A}D + A\bar{B}\bar{C}$$

we can get the same result by using SOP Method.

Q.  $\bar{A}BC + \bar{A}\bar{B}C + A\bar{B}\bar{C} + A\bar{B}C$  is equivalent to

$$\Rightarrow \begin{array}{c} \bar{B}\bar{C} \quad \bar{B}C \quad BC \quad B\bar{C} \\ \hline \bar{A} & | & | & | \\ A & | & | & | \end{array}$$

$$Y = \bar{A}C + A\bar{C}$$

$$Y = A \oplus C$$

Q.  $AB + ABC + \bar{A}B + A\bar{B}C$  is equivalent to

$$\Rightarrow AB(C + \bar{C}) + ABC + \bar{A}B(C + \bar{C}) + A\bar{B}C$$

$$= ABC + AB\bar{C} + ABC + \bar{A}BC + \bar{A}B\bar{C} + A\bar{B}C$$

$$= ABC + AB\bar{C} + \bar{A}B\bar{C} + A\bar{B}C$$

$$= AC(B + \bar{B}) + B\bar{C}(A + \bar{A})$$

$$= AC + B\bar{C}$$

Q.  $ABC + \bar{A}BC + A\bar{B}C + \bar{A}B\bar{C} + \bar{A}\bar{B}C + \bar{A}\bar{B}\bar{C}$

$$\Rightarrow \begin{array}{c} \bar{B}\bar{C} \quad \bar{B}C \quad BC \quad B\bar{C} \\ \hline \bar{A} & | & | & | & | \\ A & | & | & | & | \end{array}$$

$$Y = \bar{A} + C$$

$$= (\bar{A} + C)(C + \bar{C})$$

$$= \bar{A}\bar{C} + C$$

Q. The Boolean expression  $Y = \overline{PQR} + Q\bar{R} + \bar{P}QR + PQR$   
Simplifies to (JAM 2022)

$$\Rightarrow Y = (\bar{P} + \bar{Q})R + (P + \bar{P})Q\bar{R} + \bar{P}QR + PQR$$

$$Y = \bar{P}R + \bar{Q}R + P\bar{Q}\bar{R} + \bar{P}Q\bar{R} + \bar{P}QR + PQR$$

$$Y = \bar{P}(Q + \bar{Q})R + (P + \bar{P})\bar{Q}R + P\bar{Q}\bar{R} + \bar{P}Q\bar{R} + \bar{P}QR + PQR$$

$$Y = \bar{P}Q\bar{R} + \bar{P}\bar{Q}R + P\bar{Q}R + \bar{P}\bar{Q}\bar{R} + P\bar{Q}\bar{R} + \bar{P}QR + PQR$$


$$\bar{Q}\bar{R} \quad \bar{Q}R \quad QR \quad Q\bar{R}$$

$$Y = Q + R$$

$$\begin{array}{c} \bar{P} \quad | \quad | \quad | \quad | \\ \hline P & | & | & | & | \\ | & | & | & | & | \end{array}$$

Q Simplify  $F = (X+Y)(X+\bar{Y}) + \overline{(X\bar{Y})} + \bar{Y}$
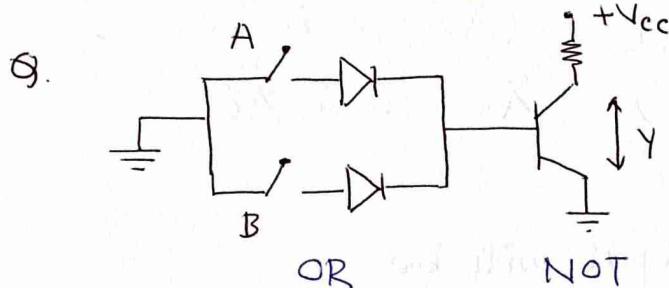
$$\begin{aligned}\Rightarrow F &= X+Y\bar{Y} + (\bar{X}\bar{Y})\bar{\bar{X}} \\ &= X + (X+Y)\bar{X} = X + XX + XY = X + XY \\ &= X(1+Y) = X\end{aligned}$$




Boolean relation at the output stage is

NOR Gate

$$Y = \overline{A+B} = \overline{A} \cdot \overline{B}$$

Q. This gate is equivalent to

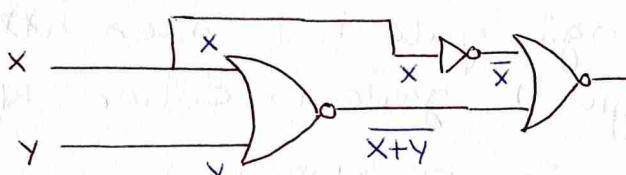

$$Y = \overline{\overline{X} + \overline{X+Y}}$$

$$Y = \overline{\overline{X}} \cdot \overline{\overline{X+Y}} = X(X+Y)$$

$$Y = XX + XY = X(1+Y)$$

$$Y = X \quad \overline{\overline{X}} \quad \text{NOR Gate}$$

Q The dual of  $\bar{A}B + A\bar{B}$  is

$$\Rightarrow \bar{A}B + A\bar{B}$$

DUAL Means

+ replaced by •

• replaced by +

$$= (\bar{A}+B) \cdot (A+\bar{B})$$

$$= A\bar{A} + \bar{A}\bar{B} + AB + B\bar{B} = \bar{A}\bar{B} + AB$$

Q The dual of  $AB + BC + AC$  is

$$\Rightarrow (A+B)(B+C)(A+C)$$

$$(B+AC)(A+C)$$

$$= (AB + AC + BB + BC)(A+C)$$

$$AB + BC + AAC + CAC$$

$$= (AB + AC + BC)(A+C)$$

$$AB + BC + AC + AC$$

$$= \{B(A+C) + AC\}(A+C)$$

$$= AB + BC + AC$$


So it is self dual

Q) check whether

$\bar{A}\bar{B} + \bar{B}\bar{C} + \bar{A}\bar{C}$  is self dual or not

$$\begin{aligned} \Rightarrow & (\bar{A} + \bar{B})(\bar{B} + \bar{C})(\bar{A} + \bar{C}) && \text{yes it is self dual} \\ & = (\bar{B} + \bar{A}\bar{C})(\bar{A} + \bar{C}) \\ & = \bar{B}\bar{A} + \bar{B}\bar{C} + \bar{A}\bar{A}\bar{C} + \bar{A}\bar{C}\bar{C} && (\bar{A}\bar{A} = \bar{A} \text{ & } \bar{C}\bar{C} = \bar{C}) \\ & = \bar{B}\bar{A} + \bar{B}\bar{C} + \bar{C}\bar{A}(\bar{A} + \bar{C}) = \bar{A}\bar{B} + \bar{B}\bar{C} + \bar{A}\bar{C} \end{aligned}$$

Q)

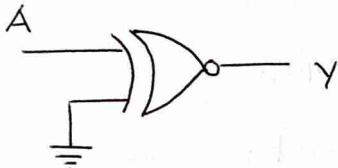

The output will be


$$Y = \overline{A \oplus B} = \overline{\bar{A}\bar{B} + \bar{A}B}$$

$$A = A$$

$$B = 0$$

$$= \overline{\bar{A}0 + \bar{A}0} = \overline{\bar{A}} = \bar{A}$$

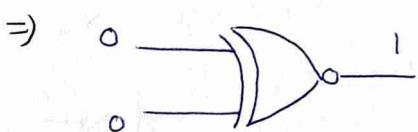Q) The output of a logic gate is 1 when all its inputs are at logic 0. gate is either NOR/EX-NOR



For EX-NOR Gate

$$Y = \overline{\bar{A}\bar{B} + \bar{A}B} = \bar{O} = 1$$


Q)  $Z = P\bar{Q} + P\bar{Q}R + P\bar{Q}RS + P\bar{Q}RST + P\bar{Q}RSTU$  then  $\bar{Z}$  is

$$\Rightarrow Z = P\bar{Q} + P\bar{Q}R + P\bar{Q}RS + P\bar{Q}RST(U+V)$$

$$= P\bar{Q} + P\bar{Q}R + P\bar{Q}RS(U+T)$$

$$= P\bar{Q} + P\bar{Q}R + P\bar{Q}RS$$
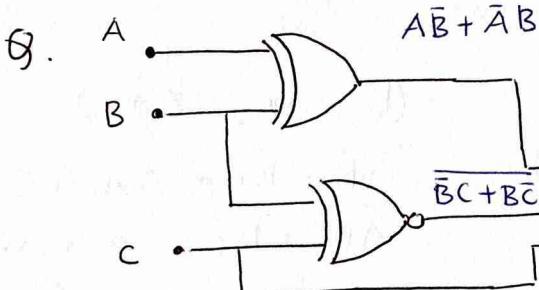
$$= P\bar{Q} + P\bar{Q}R(U+S) = P\bar{Q} + P\bar{Q}R = P\bar{Q}$$




$$A = 1$$

$$B = 0$$

$$C = 1$$
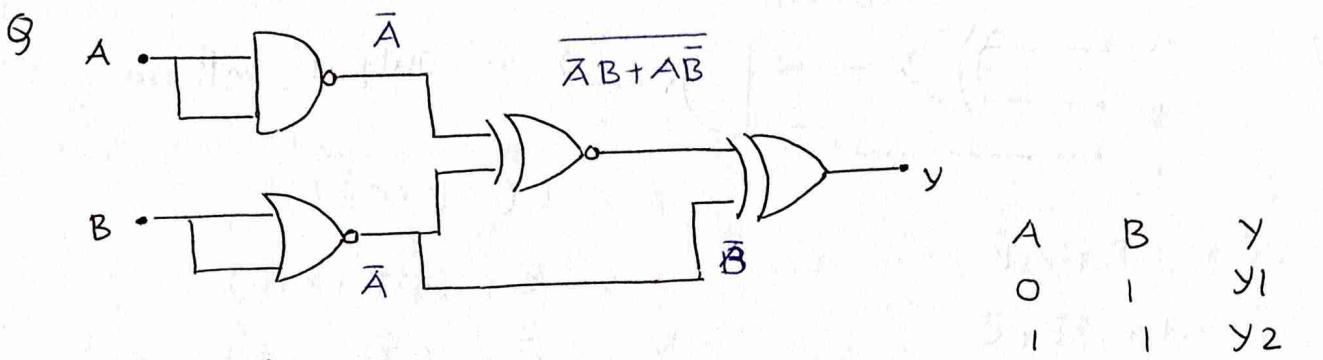
$$Y = (A\bar{B} + \bar{A}B)(\overline{\bar{B}C + BC})C$$



Value of  $y_1$  and  $y_2$  is

$$y_1 = 0$$

$$y_2 = 1$$

Q Simplify  $ABC + \overline{A}BC + A\overline{B}C + \overline{A}B\overline{C} + \overline{A}\overline{B}C + \overline{A}\overline{B}\overline{C}$

=)

	$\overline{B}\overline{C}$	$\overline{B}C$	$BC$	$B\overline{C}$
$\overline{A}$	1	1	1	1
A		1	1	

$$Y = \overline{A} + C$$

$$Y = C + \overline{A}\overline{C}$$

Also  $C + \overline{A}\overline{C} = (C + \overline{C})(C + \overline{A})$

$$C(A + \overline{A}) + \overline{A}\overline{C}$$

$$CA + C\overline{A} + \overline{A}\overline{C}$$

Q Equivalent in SOP for K Map

	$\overline{C}\overline{D}$	$\overline{C}D$	CD	$C\overline{D}$
$\overline{A}\overline{B}$		1	1	
$\overline{A}B$	1			1
AB	1			1
$A\overline{B}$		1	1	

$$Y = \overline{B}D + B\overline{D}$$

$$Y = B \oplus D$$


Q The minimal boolean expression is


	$\overline{B}\overline{C}$	$\overline{B}C$	$BC$	$B\overline{C}$
$\overline{A}$	1			1
A	1			1

$$Y = \overline{C}$$

Q If  $A = B = C = 1$   
then  $Y = ?$

=)  $Y = 1$

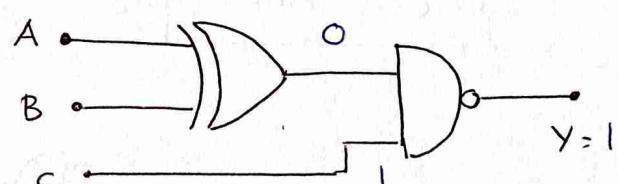

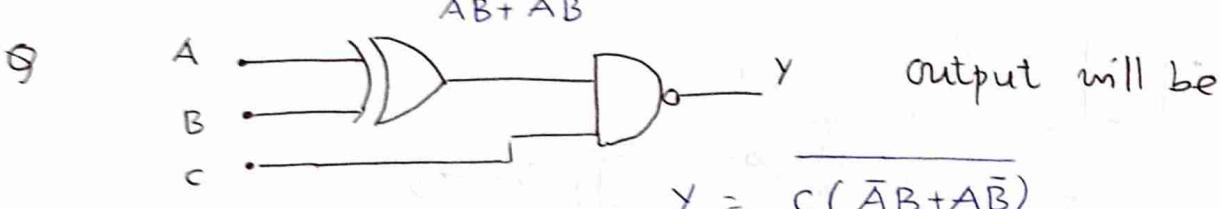

$$Y = \bar{C} + AB + \bar{A}\bar{B}$$

$$Y = \bar{A}\bar{B} + AB + \bar{C}$$

output


$$Y = \overline{C(\bar{A}B + A\bar{B})}$$

$$Y = \bar{C} + (\bar{A}B + A\bar{B})$$

$$Y = \bar{C} + (\bar{A}\bar{B} \cdot A\bar{B})$$

$$Y = \bar{C} + (A + \bar{B})(\bar{A} + B)$$

Q The output will be

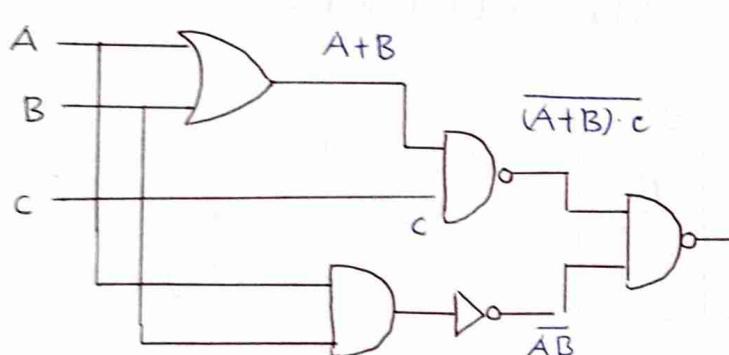


$$Y = \overline{(A+B) \cdot C \cdot \bar{A}\bar{B}}$$

$$Y = \overline{(A+B)C} + AB$$

$$Y = \overline{(A+B)} + \bar{C} + AB$$

$$Y = \bar{A}\bar{B} + \bar{C} + AB$$

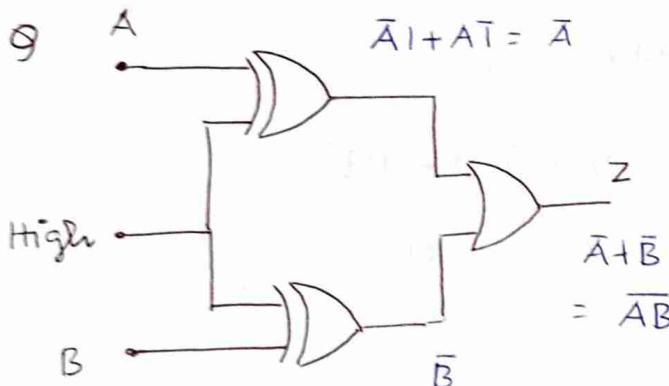


Q  $P + \bar{P}Q$  represents

$$\Rightarrow P + \bar{P}Q$$

$$= (P + \bar{P})(P + Q)$$

$$= P + Q$$

(OR Gate)

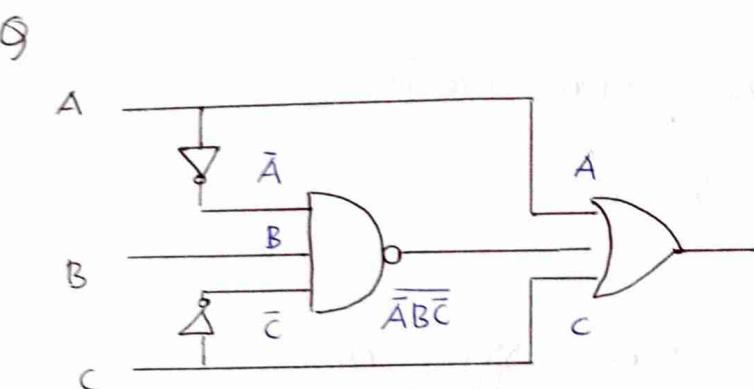


The Circuit is equivalent to

$$Y = A + \bar{A}\bar{B}\bar{C} + C$$

$$= A + (\bar{A} + \bar{B} + \bar{C}) + C$$

$$= A + (A + C + \bar{B}) + C$$

$$= A + \bar{B} + C$$

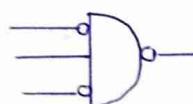

(Equivalent gate)

## Don't Care Condition

Here we take a truth table

A	B	C	Y
0	0	0	0
0	0	1	X0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	X1
1	1	0	0
1	1	1	0

Now from Karnaugh Map

	$\bar{B}\bar{C}$	$\bar{B}C$	$BC$	$B\bar{C}$
$\bar{A}$		X	1	1
A	1	X		

$$Y = A\bar{B} + \bar{A}B$$

We can use X pair with 1 but if 1 engaged then no pair between X and 1

Q Find the Simplified form of  $\sum_d$  means

$$Y = \sum (0, 2, 4, 5, 8, 10) + \sum_d (6, 12, 13) \quad \text{don't care}$$

$$\Rightarrow Y = \bar{C}B + \bar{C}\bar{D} + \bar{B}\bar{D} + \bar{A}\bar{D}$$

Folding of corners also

Gives square. Here All elements of  $\bar{C}\bar{D}$  engaged

$$\text{So } Y = \bar{C}B + \bar{B}\bar{D} + \bar{A}\bar{D}$$

	$\bar{C}\bar{D}$	$\bar{C}D$	$CD$	$C\bar{D}$
$\bar{A}\bar{B}$	0	1	3	2
$\bar{A}B$	4	5	7	X
$AB$	X	X	15	14
$A\bar{B}$	8	9	11	10

Q Expression for 3 input Ex-OR Gate

A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	0	0
1	0	1	1
1	0	0	0
1	1	1	0
1	1	1	1

	$\bar{B}\bar{C}$	$\bar{B}C$	$BC$	$B\bar{C}$
$\bar{A}$		1	0	1
A	1		1	

$$Y = \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC$$

(Check the TT)


① Simplify

	$\bar{C}\bar{D}$	$\bar{C}D$	$C\bar{D}$	$CD$
$\bar{A}\bar{B}$			1	
$\bar{A}B$	X	X	1	X
$A\bar{B}$		1	1	
$AB$	1	1		

$$Y = CD + AD$$

$$Y = D(A+C)$$

② unknown gate should be XOR or NAND

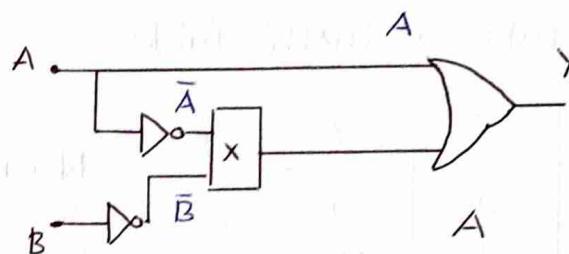

$\bar{A}$	$\bar{B}$	X	A	B	Y
1	1	0	0	0	0
1	0	1	0	1	1
0	1	X	1	0	1
0	0	X	1	1	1

(C) (D)

$\bar{C}$	D
X	X
1	

$$Y = \bar{D} = B$$

③ Find the simplified form

$$f = \sum 5, 7, 8, 10, 13, 15 + \sum_d (0, 1, 2)$$

$$\Rightarrow f = BD + \bar{D}\bar{B}$$

	$\bar{C}\bar{D}$	$\bar{C}D$	$CD$	$C\bar{D}$
$\bar{A}\bar{B}$	X	X		X
$\bar{A}B$		1	1	
$A\bar{B}$	1			1
$AB$				

④ Simplify  $Y = ABC + \bar{A}BC + A\bar{B}C + \bar{A}B\bar{C} + \bar{A}\bar{B}C + \bar{A}\bar{B}\bar{C}$

	$\bar{B}\bar{C}$	$\bar{B}C$	$BC$	$B\bar{C}$
$\bar{A}$	1	1	1	1
A		1	1	

$$Y = \bar{A} + C$$

$$C + \bar{A}\bar{C} = (C + \bar{A})(C + \bar{C}) = \bar{A} + C$$

⑤ A B C Y Find Y.

1  
0  
1  
1  
0

	$\bar{B}\bar{C}$	$\bar{B}C$	$BC$	$B\bar{C}$
$\bar{A}$	1	0	1	1
A	1	1	1	0
	4	5	3	2
	X	X	7	6

$$Y = B + \bar{C}$$


## ① Half Adder

By this adder we can add 2 bit

A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$S = \bar{A}B + A\bar{B} = A \oplus B$$

$$C = AB$$

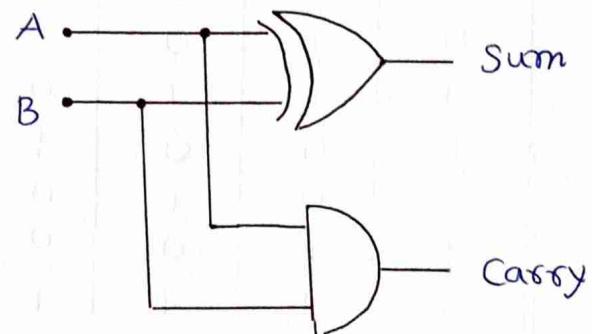

Sum: Ex-OR Gate

Carry: AND Gate

## ② Full Adder

A	B	C	S	C'
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

	$\bar{B}\bar{C}$	$\bar{B}C$	$BC$	$B\bar{C}$
$\bar{A}$		1		1
A	1		1	

$$\begin{aligned}
 S &= A\bar{B}\bar{C} + \bar{A}\bar{B}C + ABC + \bar{A}B\bar{C} \\
 &= \bar{C}(\bar{A}B + A\bar{B}) + C(AB + \bar{A}\bar{B}) \\
 &= \bar{C}(A \oplus B) + C(\bar{A} \oplus \bar{B}) \\
 &= (A \oplus B) \oplus C
 \end{aligned}$$

	$\bar{B}\bar{C}$	$\bar{B}C$	$BC$	$B\bar{C}$
$\bar{A}$			1	
A		1	1	1

$$C' = AC + BC + AB$$

## ③ Half Subtractor


By the electronic device we subtract 2 single bit

A	B	$B_o$	D
0	0	0	0
0	1	0	1
1	0	1	1
1	1	0	0

$$D = A\bar{B} + \bar{A}B$$

$$= A \oplus B$$

$$B_o = \bar{A}B$$

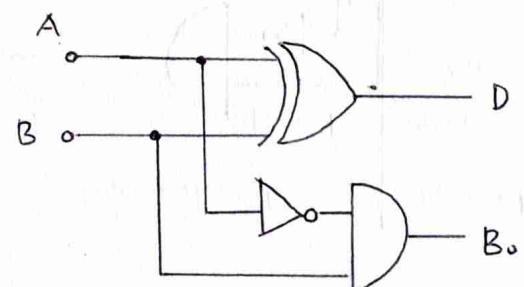

#### ④ Full Subtractor

INPUT			OUTPUT	
A	B	Bin	D	Bout
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

$$D = \bar{A}\bar{B}Bin + \bar{A}B\bar{B}Bin + A\bar{B}\bar{B}Bin + ABBin$$

$$= (\bar{A}\bar{B} + AB)Bin + (\bar{A}B + A\bar{B})\bar{B}Bin$$

$$= (\overline{A \oplus B})Bin + (A \oplus B)\bar{B}Bin$$


$$= (A \oplus B)Bin$$

$$Bout = \bar{A}\bar{B}Bin + \bar{A}B\bar{B}Bin + A\bar{B}Bin + ABBin$$

$$= (\bar{A}\bar{B} + AB)Bin + \bar{A}B(Bin + \bar{B}Bin)$$

$$= (\overline{A \oplus B})Bin + \bar{A}B$$

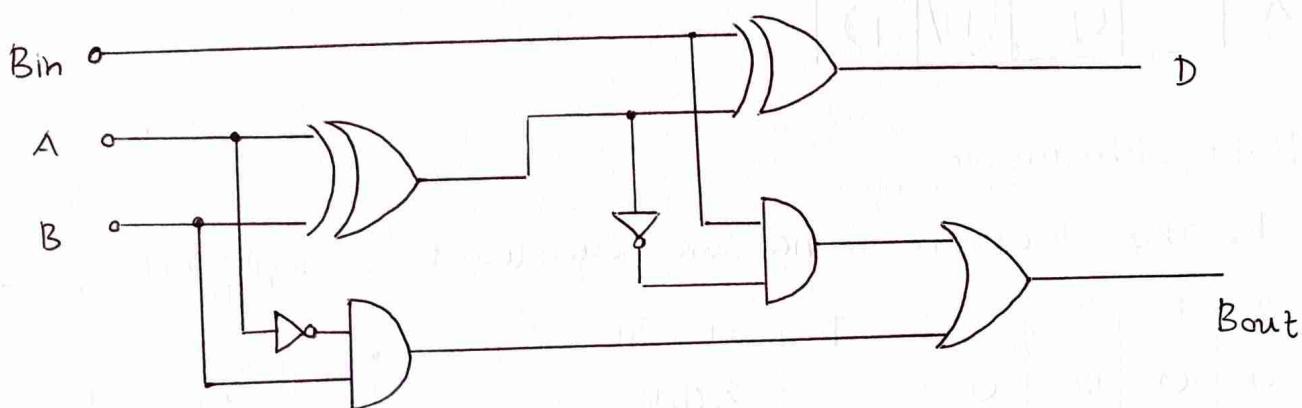The logic circuit can be designed by using two Half Subtractor.



## ① Crystal Structure

These are 3 states of matter —

Solid

Liquid

Gas

Intermol  
ecular  
Force

Strong

Intermediate

Weak

Molecular  
distance

Very  
less

Intermediate

Most

> Some characteristics of Solid:

- They have definite mass, volume and density
- Intermolecular distances are short
- Intermolecular forces are strong
- They are incompressible and rigid have fixed Positions

Solid

Crystalline

Solid

Amorphous

Solid

- Regular shape
- Sharp MP, BP
- Definite heat of fusion
- Anisotropic in nature
- They are True Solids

- Regular shape.
- Range of MP & BP
- They have not it.
- Isotropic in nature
- Pseudo Solids.

> Unit Cell:

Smallest unit that repeats itself to form a Crystal is called unit cell


> Lattice Points: Imaginary Points in Space.

## Types of unit cells:

- ① Primitive unit cell (Atoms are at corners only) Simple Cubic
- ② Non Primitive cell (FCC, BCC, EGC)
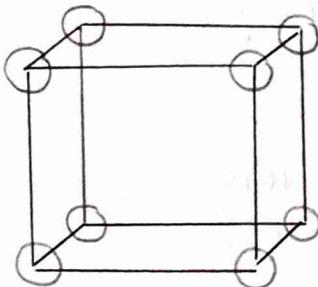
### (a) Simple Cubic unit cell

- > 8 atoms at corners
- > Contribution of each atom in the unit cell is  $\frac{1}{8}$
- > No of atom =  $8 \times \frac{1}{8} = 1$  Neff = 1




- > Co-ordination no is 6
- > Nearest neighbour distance =  $a$  Actually the atom touch each other.
- > Second nearest distance =  $\sqrt{2}a$
- > Volume of unit cell is  $a^3$
- > Volume of atom is  $1 \times \frac{4}{3} \pi r^3$

$$\% \text{ Packing fraction} = \frac{\frac{\text{Volume of atom}}{\text{Volume of unit cell}} \times 100}{a^3} = \frac{1 \times \frac{4}{3} \pi r^3}{a^3} \times 100 = 52.3\%$$

> Void fraction =  $(100 - 52.3) = 47.6\%$
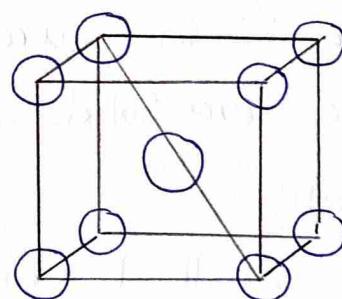
### (b) Body Centred Cubic

- > 8 atoms at corners ( $8 \times \frac{1}{8} = 1$ )
- > 1 atom at centre
- > Neff = 2
- > Nearest Neighbour distance  $\frac{\sqrt{3}}{2}a$
- > Second Nearest is  $a$
- > Coordination no is 8



$$\text{Here } 2\delta = \frac{\sqrt{3}}{2}a$$

$$\delta = \frac{\sqrt{3}}{4}a$$

Packing fraction

$$= \frac{2 \times \frac{4}{3} \pi \delta^3}{a^3}$$

Void fraction = 32%

$$= \frac{8}{3} \times \pi \times \frac{3\sqrt{3}}{64} = 68\%$$

### (c) Face Centred Cubic cell


> At corner  $8 \times \frac{1}{8} = 1$

Face Centre  $6 \times \frac{1}{2} = 3$

> Neff =  $1 + 3 = 4$

> Nearest Neighbour distance  $\frac{a}{\sqrt{2}}$

> Second nearest is  $a$

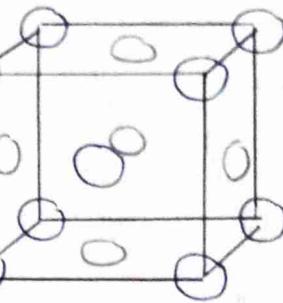

$$2\delta = a/\sqrt{2}$$

> Coordination number CN =  $9 + 4 + 4 = 12$

> Packing fraction =

$$\frac{\text{Neff} \times \frac{4}{3} \pi \delta^3}{a^3} \times 100 = 74\%$$

> Void fraction =  $100 - 74 = 26\%$

## ② closed Packing:

### (a) 1D closed Packing:



### (b) 2D closed Packing

Square closed  
Packing



$$2\delta = a$$


$$Z_{\text{eff}} = \frac{1}{4} \times 4 = 1$$

Coordination No is 4


AAA Type

$$Pf = \frac{\pi R^2}{a^2} = \frac{\pi}{4} \times 100 = 78.5\%$$

## Hexagonal closed Packing

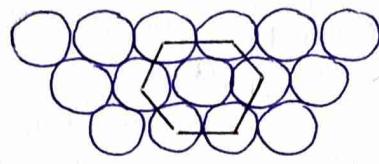

### HCP in 3D

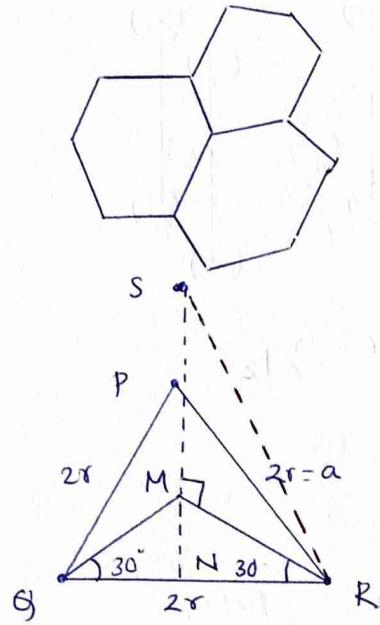

$$\triangle MNR, NR = \frac{a}{2}$$

$$\cos 30^\circ = \frac{\frac{a}{2}}{MR} \Rightarrow MR = \frac{a}{2} \times \frac{2}{\sqrt{3}} = \frac{a}{\sqrt{3}}$$

$$\Rightarrow MR = \frac{a}{\sqrt{3}}$$

Volume of unit cell

Area

Volume of hexagon  $\times$  height

$$= 6 \times \frac{\sqrt{3}}{4} a^2 \times c$$


Packing fraction

=

$$\frac{N \times \text{Volume of atom}}{\text{Volume of unit cell}} =$$

$$\frac{6 \times \frac{4}{3} \pi r^3}{\frac{6\sqrt{3}}{4} \times (2r)^2 + (\sqrt{\frac{2}{3}} \times 4r)}$$


$$= 74\%$$

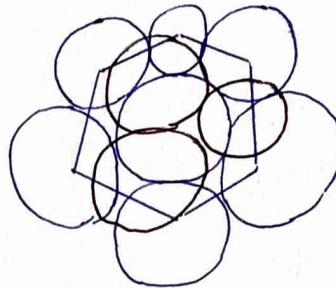

ABAB  
layering

$$N_{eff} = (12 \times \frac{1}{6}) + (\frac{1}{2} \times 2) + 3 = 2 + 1 + 3 = 6$$

Here also,  $a = 2r$

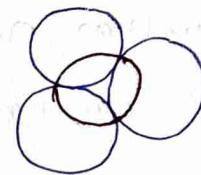

S is centre of Black atom

P, Q, R is for white atoms

M is centre of Void PQR

From  $\triangle SMR$

$$SR = a, MR = a/\sqrt{3}$$

$$SM = \sqrt{(SR)^2 - (MR)^2}$$

$$\frac{c}{2} = \sqrt{a^2 - \frac{a^2}{3}} = \sqrt{\frac{2}{3}} a$$

$$c = \sqrt{\frac{8}{3}} a$$

① An ionic compound has a unit cell consisting of A ions at the corners of a cube and B ions on the centres of the faces of the cube. The empirical formula is

$$\Rightarrow A = 8 \times \frac{1}{8} = 1 \quad \text{Empirical formula}$$

$$B = 6 \times \frac{1}{2} = 3 \quad \text{is } AB_3$$

② A diatomic molecule  $X_2$  has a bcc structure with a cell edge of 300 pm. The density of the molecule is 6.17 g/cm<sup>3</sup>. The number of molecule in 200 g of  $X_2$  is

$$\Rightarrow \rho = \frac{w N_{eff}}{a^3 N_A} \Rightarrow 6.17 \times 10^3 = \frac{w \times 2 \times 10^{-3}}{(300 \times 10^{-12})^3 N_A} \Rightarrow w = 50$$

In 50 g  $\rightarrow N_A$   
200 g  $\rightarrow 4N_A$

③ At 373K Copper has FCC unit cell structure with cell edge of  $a \text{ \AA}$ . The approximate density of Cu is

$$\Rightarrow \rho = \frac{w N_{eff}}{a^3 N_A} = \frac{4 \times 63.5}{(a \times 10^{-8})^3 N_A} = \frac{422}{a^3}$$

④ Nearest neighbour distance in Na crystal is 1.83  $\text{\AA}$ . Density of electrons in Na crystal

$\Rightarrow$  Na is BCC

Nearest neighbour distance

$$-\frac{\sqrt{3}}{2}a = 1.83 \times 10^{-10} \Rightarrow a = 2.11 \times 10^{-10} \text{ m}$$

$$\text{Density of atom} = \frac{\text{No of atom}}{\text{Volume}} = \frac{2}{(2.11 \times 10^{-10})^3} = 2.12 \times 10^{29} \text{ /m}^3$$

⑤ Consider 2 types of space lattice. SC & FCC. Ratio of nearest neighbour distance

$$\Rightarrow 1 : \frac{1}{\sqrt{2}}$$

## Miller Indices

- ① Take intercepts  $(3a \ 2b \ 6c)$
- ② Remove constant  $(3 \ 2 \ 6)$
- ③ Reciprocate  $(\frac{1}{3} \ \frac{1}{2} \ \frac{1}{6})$
- ④ LCM Multiplied  $(\frac{1}{3} \times 6 \ \frac{1}{2} \times 6 \ \frac{1}{6} \times 6)$

Miller indices of  $(3a \ 2b \ 6c)$  is  $[2 \ 3 \ 1]$

> If intercepts are  $(a \ \infty \ \infty)$   
the Miller indices  $(1 \ 0 \ 0)$


## Law of Rational Indices

$$\text{If } OA = a \quad OA' = na \\ OB = b \quad OB' = mb \\ OC = c \quad OC' = kc$$

The features of Miller indices -


- ① Represent direction of a plane
- ② It won't be infinite ever
- ③ Only integral Value.
- ④ Plane is never considered to be Passing through origin
- ⑤ Reciprocal of intercepts
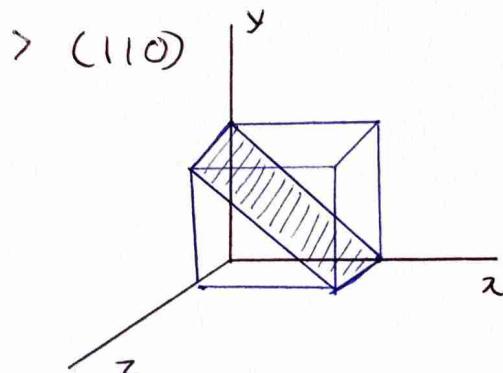
> For  $(2a, 3b, 5c) \Rightarrow 2 \ 3 \ 5 \Rightarrow \frac{1}{2} \ \frac{1}{3} \ \frac{1}{5} \Rightarrow (15 \ 10 \ 6)$



>  $(200)$


$$(\frac{1}{2} \infty \infty)$$

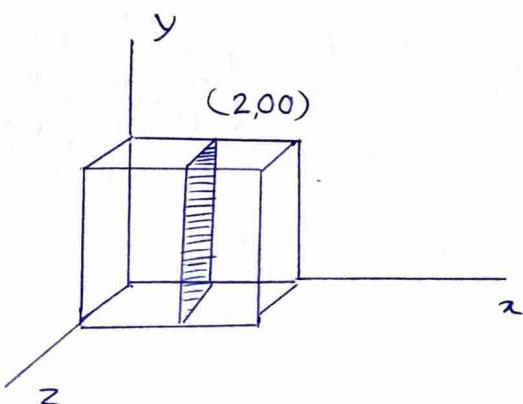

MI of 230

$$(\frac{1}{2}, \frac{1}{3}, \infty)$$

$$(\frac{a}{2}, \frac{b}{3}, \infty)$$

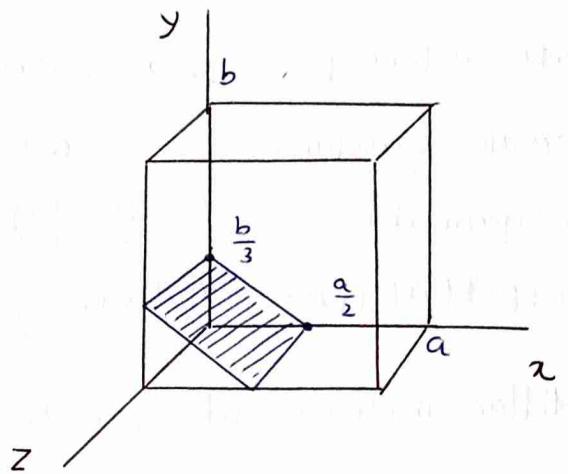

### Distance between Interplaner Space:

If Miller indices are  $(h k l)$  then


$$\frac{1}{h}, \frac{1}{k}, \frac{1}{l} \Rightarrow (\frac{a}{h}, \frac{b}{k}, \frac{c}{l})$$

From  $\triangle PAO$

$$\cos \alpha = \frac{OP}{OA} = \frac{d}{(a/h)}$$

$$\cos \beta = \frac{d}{(b/k)}$$

$$\cos \gamma = \frac{d}{(c/l)}$$

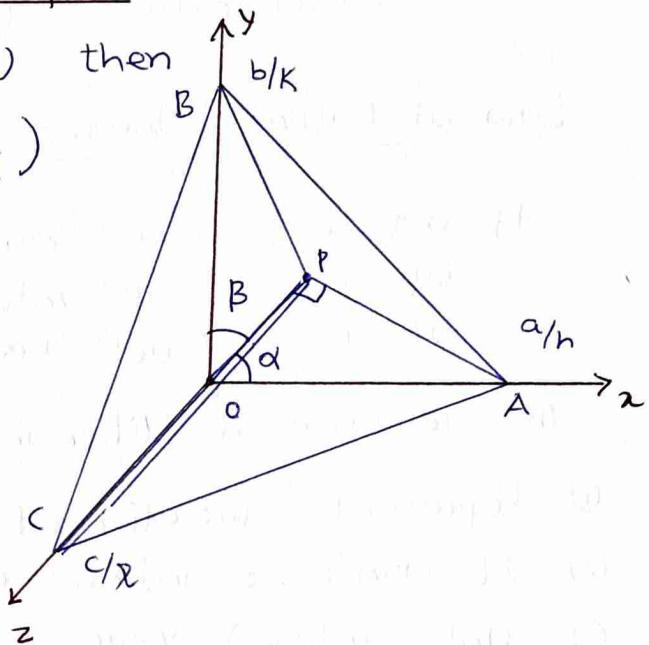

From the Law of direction Cosine we have

$$\cos^2 \alpha + \cos^2 \beta + \cos^2 \gamma = 1$$

$$\left(\frac{d}{a/h}\right)^2 + \left(\frac{d}{b/k}\right)^2 + \left(\frac{d}{c/l}\right)^2 = 1$$

$$d = \sqrt{\frac{1}{\frac{h^2}{a^2} + \frac{k^2}{b^2} + \frac{l^2}{c^2}}}$$

So distance between interplaner plane

$$d = \frac{1}{\sqrt{\frac{h^2}{a^2} + \frac{k^2}{b^2} + \frac{l^2}{c^2}}}$$



> For cubic:  $a=b=c$

$$d_{hkl} = \frac{a}{\sqrt{h^2 + k^2 + l^2}}$$

### X-ray Diffraction/ Bragg's Law

Constructive interference will be form if the Path difference.  $\Delta = n\lambda$

$$\Delta = QR + RS = n\lambda$$

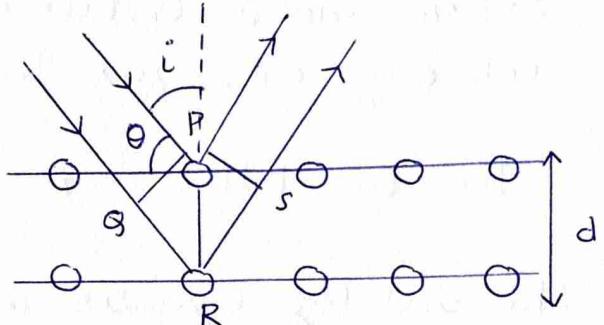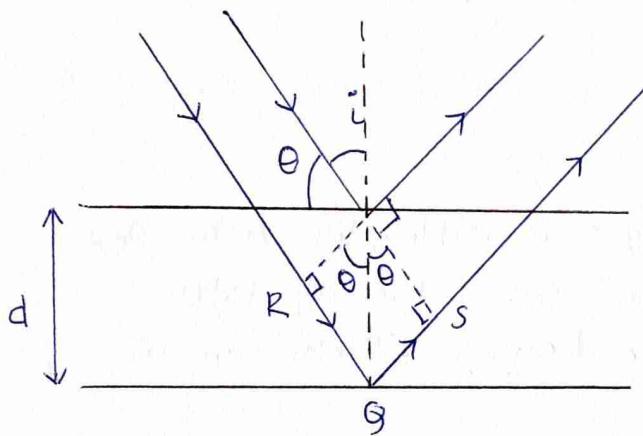

$\theta$  is glancing angle

$i$  is incident angle

$$\theta + i = \pi/2$$

Path difference.  $\Delta x = RQ + QS$

$$RQ = ds \sin \theta$$

$$QS = ds \sin \theta$$

$$2ds \sin \theta = n\lambda \rightarrow \text{Bragg's Law}$$

$$n\lambda = 2d_{hkl} \sin \theta$$

For Cubic Crystal,  $d_{hkl} = \frac{a}{\sqrt{h^2 + k^2 + l^2}}$

$$n\lambda = \frac{2a}{\sqrt{h^2 + k^2 + l^2}} \sin \theta$$

$n$  is the order of diffraction

$d$  is interference spacing

(If order is not mention. take  $n=1$ )

① Bragg's angles for the first and second order reflection by a crystal are  $\theta_1$  and  $\theta_2$  respectively.  $\frac{\sin\theta_1}{\sin\theta_2}$  is

$$\Rightarrow 2d \sin\theta = n\lambda \Rightarrow \sin\theta \propto n$$

$$\Rightarrow \frac{\sin\theta_1}{\sin\theta_2} = \frac{1}{2}$$

② Sodium metal crystallizes in a BCC lattice with a unit cell edge of  $3.29\text{\AA}$ . The radius of sodium atom

$$\Rightarrow \text{For BCC lattice } r = \frac{\sqrt{3}}{4}a = \frac{\sqrt{3}}{4} \times 3.29 = 1.42\text{\AA}$$

③ Na and Mg crystallize in BCC and FCC type crystal. Then the number of atoms of Na and Mg present -

$$\Rightarrow \text{For BCC, } N_{eff} = 2$$

$$\text{FCC } N_{eff} = 4$$

④ An X-ray beam of wavelength  $1.54\text{\AA}$  is diffracted from the (100) planes of a solid with a cubic lattice of lattice constant  $3.08\text{\AA}$ . The first order Bragg diffraction angle

$$\Rightarrow 2d \sin\theta = n\lambda \quad \lambda = \frac{2 \times 3.08 \sin\theta}{\sqrt{1+1+0}}$$

$$n\lambda = \frac{2a \sin\theta}{\sqrt{h^2+k^2+l^2}} \quad 2 \times 3.08 \sin\theta = 1.54 \Rightarrow \theta = \sin^{-1}\left(\frac{1}{4}\right)$$

⑤  $0.71\text{\AA}$  wavelength of X-ray is diffracted in a simple cubic crystal having  $a = 2.814\text{\AA}$  for plane (110) then

$$\Rightarrow 2d \sin\theta = n\lambda \quad \frac{2 \times 2.814 \times \sin\theta}{\sqrt{1+1+0}} = 0.71$$

$$\frac{2a \sin\theta}{\sqrt{h^2+k^2+l^2}} = n\lambda \quad \sin\theta = \frac{\sqrt{2} \times 0.71}{2.814}$$

$$\theta = \sin^{-1}(0.357)$$

Simple Cubic: Reflection through every plane is possible  
like (100) (010) (210) (200) ...

BCC: Reflection is possible if  $h+k+\lambda = \text{Even}$   
(100) X (110) ✓ (111) X (210) X

FCC: They should be unmixed  
(0 is Consider as even)  
(100) X (201) X (h, k, λ) should be  
(101) X (200) ✓ unmixed.

⑥ Consider a monoatomic FCC solid with lattice constant  $\sqrt{3} \text{ Å}$ . Which of the following is correct ( $\lambda = 1 \text{ Å}$ )

$$\Rightarrow \frac{2a \sin \theta}{\sqrt{h^2 + k^2 + \lambda^2}} = n\lambda \Rightarrow \frac{2\sqrt{3} \sin \theta}{\sqrt{1+1+1}} = 1 \quad (111)$$

$$\Rightarrow \sin \theta = \frac{1}{2} \Rightarrow \theta = \frac{\pi}{6}$$

$$\text{Interplaner distance } d = \frac{a}{\sqrt{h^2 + k^2 + \lambda^2}} = \frac{\sqrt{3}}{\sqrt{3}} = 1 \text{ Å}$$

⑦ For a single cubic lattice  $d_{100} : d_{110} : d_{111} =$

$$\Rightarrow \frac{a}{\sqrt{1+0+0}} : \frac{a}{\sqrt{1+1+0}} : \frac{a}{\sqrt{1+1+1}}$$

$$a : \frac{a}{\sqrt{2}} : \frac{a}{\sqrt{3}} \Rightarrow \sqrt{6} : \sqrt{3} : \sqrt{2}$$

⑧ In a powder diffraction pattern recorded from a FCC sample using X-ray. The first peak appears at  $30^\circ$ . The second peak will appear at angle

$\Rightarrow$  For FCC. first peak at  $(11\bar{1})$   
Second peak at  $(200)$


$$\frac{2a \sin \theta_1}{\sqrt{h^2 + k^2 + l^2}} = n\lambda \Rightarrow \frac{\sin 30}{\sqrt{2+1}} = \lambda \Rightarrow \lambda = \frac{2a}{2\sqrt{3}} \Rightarrow \lambda = \frac{a}{\sqrt{3}}$$

$$\lambda = 2 \cdot \frac{a}{\sqrt{4}} \times \sin \theta = \frac{a}{\sqrt{3}} \Rightarrow \theta = \sin^{-1}\left(\frac{1}{\sqrt{3}}\right)$$

⑨ The maximum radius of the interstitial sphere that can just fit into the void between the body centred atom of BCC structure is

$$\Rightarrow 4R = \sqrt{3}a$$

$$R = \frac{\sqrt{3}}{4}a$$

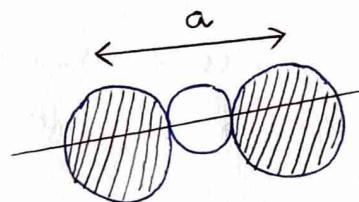

$$2R + 2r = a$$

$$\Rightarrow r = \frac{a - 2R}{2} = \frac{a}{2} - 2 \cdot \frac{\sqrt{3}}{4}a = \frac{a}{2} - \frac{\sqrt{3}a}{4}$$

$$r = \frac{a}{2} \left(1 - \frac{\sqrt{3}}{2}\right)$$

⑩ The cube FCC  $(200)$  has a lattice constant  $2.814 \text{ \AA}$ ,  $\lambda = 0.710 \text{ \AA}$ . The glancing angle corresponding to second order reflection

$$\Rightarrow \frac{2a \sin \theta}{\sqrt{h^2 + k^2 + l^2}} = n\lambda \quad 2.814 \sin \theta = 2 \times 0.710$$

$$\frac{2 \times 2.814 \times \sin \theta}{2} = 2\lambda \quad \sin \theta = \frac{1}{2}$$

$$\theta = 30^\circ$$

(11) The Miller indices of a plane passing through the three points having (001), (1,0,0) & (0.5, 0.5, 0.25) are

$\Rightarrow$  Equation of plane

$\Rightarrow$

$$\begin{vmatrix} x & y & z-1 \\ 1 & 0 & -1 \\ 0.5 & 0.5 & -0.75 \end{vmatrix} = \frac{x(x_1-x_2)}{x_1-x_3} + \frac{y(y_1-y_2)}{y_1-y_3} + \frac{z(z_1-z_2)}{z_1-z_3} = \frac{x(0+0.5)}{x(0+0.5)} + \frac{y(-0.5+0.75)}{y(-0.5+0.75)} + \frac{z(-1)(0.5)}{z(-1)(0.5)} = \frac{x}{2} + \frac{y}{4} + \frac{z}{2} = \frac{1}{2} \Rightarrow 2x + y + 2z = 2$$

Intercepts

$$1 \quad 2 \quad 1$$

$$\frac{1}{1} \quad \frac{1}{2} \quad \frac{1}{1}$$

Miller indices are (212)

$$2 \quad 1 \quad 2$$

$$\frac{x}{1} + \frac{y}{2} + \frac{z}{1} = 1$$

(12) X-ray of wavelength  $\lambda=a$  is reflected from the (111) plane of a simple cubic lattice. If the lattice constant is  $a$ , Braggs angle will be


$$\Rightarrow \frac{2a \sin \theta}{\sqrt{h^2+k^2+l^2}} = n\lambda \Rightarrow \frac{2a \sin \theta}{\sqrt{3}} = a \Rightarrow \theta = \sin^{-1}\left(\frac{\sqrt{3}}{2}\right) = \frac{\pi}{3}$$

(13) Consider X-ray diffraction from a crystal with a FCC. The lattice plane for no diffraction peak is

$\Rightarrow (212) \Rightarrow$  Mixture of odd & even  $\Rightarrow$  No diffraction peak

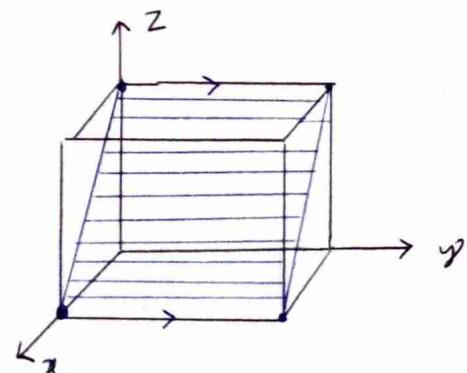(14) Crystallographic plane represent (101) miller indices

$$a = \frac{1}{1} = 1, b = \frac{1}{0} = \infty, c = \frac{1}{1} = 1$$



From Bragg's Law,  $n\lambda = \frac{2a \sin\theta}{\sqrt{h^2+k^2+l^2}}$

Right hand side  
is constant

$$\frac{\lambda}{2a} = \frac{\sin\theta}{\sqrt{h^2+k^2+l^2}} \quad [\text{for } n=1]$$

$$\frac{\lambda}{4a} = \frac{\sin^2\theta}{(h^2+k^2+l^2)} = \text{constant}$$

- ⑪ In an XRD experiment following set of reflections expressed as  $2\theta (\circ)$  38.40, 44.50, 64.85, 77.90, 81.85, 98.40, 111.20. The crystal structure is

=)

$2\theta$	$\theta$	$\sin^2\theta$	$h^2+k^2+l^2$	$\frac{\sin^2\theta}{h^2+k^2+l^2}$
38.40	19.2	0.108153271	$1^2+0^2+0^2=1$	0.108153271
44.50	22.25	0.1433747	$1^2+1^2+0^2=2$	0.054076635
38.50	19.2	0.1081532	$1^2+1^2+0^2=2$	0.054076635
44.50	22.25	0.1433747	$2^2+0^2+0^2=4$	0.0358436
38.40	19.2	0.10815327	$1^2+1^2+1^2=3$	0.03605109
44.50	22.50	0.1433747	$2^2+0^2+0^2=4$	0.03661652
64.85	32.425	0.287505	$2^2+2^2+0^2=8$	0.035938

} Values are different so no simple cubic

} Values are not same so not BCC


} Values are same so structure is FCC

## Voids:


### ① Triangular voids:

This Vacancy is triangular void →

(In 2dim)

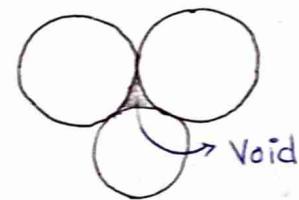

Coordination no is 3

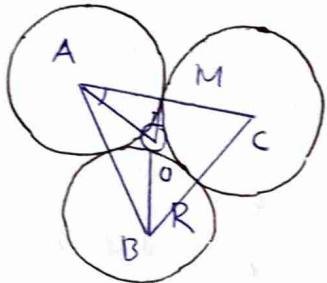

Ratio of cation and anion is 0.154.

$$\frac{AM}{AO} = \cos 30$$

$$\frac{R}{R+r} = \frac{\sqrt{3}}{2}$$

$$2R = \sqrt{3}R + \sqrt{3}r$$

$$(2 - \sqrt{3})R = \sqrt{3}r$$

$$\frac{r}{R} = \frac{(2 - \sqrt{3})}{\sqrt{3}} = 0.154$$

Radius of inner atom is  $r$


$$AM = R$$

$$AO = R+r$$

$$\frac{r_+}{r_-} = 0.154$$
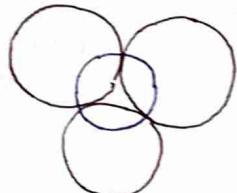
### ② Tetrahedral Voids:

Coordination no of tetrahedral Void is 4.




$$\sin 54.75 = \frac{R}{R+r}$$

$$0.816R + 0.816r = R$$

$$0.816r = 0.184R$$

$$\frac{r}{R} = 0.225$$

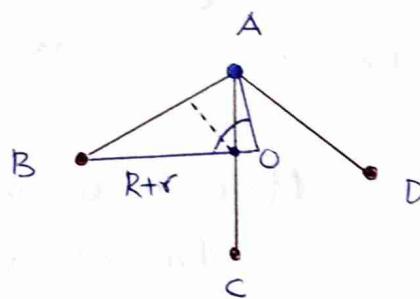

$$AB = 2R$$

$$AO = R+r$$

### ③ Cubic Void


$$\sqrt{3}a = 2(R+r)$$

$$\text{and } a = 2R$$

$$2\sqrt{3}R = 2(R+r)$$

$$\sqrt{3}R = R+r$$
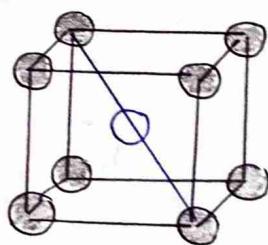
$$(\sqrt{3}-1)R = r \Rightarrow \frac{r}{R} = \frac{r_+}{r_-} = 0.732$$




#### ④ Octahedral Void


$$AC = 2R$$

$$BC = 2R$$

$$AO = R + r$$

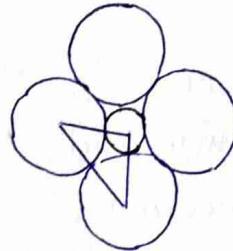

$$AB = 2(R + r)$$

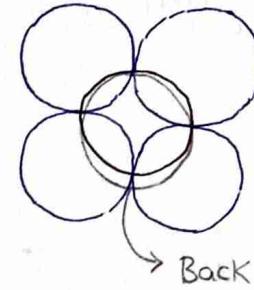


$$AC^2 = AO^2 + OC^2 \Rightarrow 4R^2 = 2(R^2 + r^2 + 2Rr)$$

$$(2R)^2 = 2(R+r)^2 \Rightarrow \frac{r}{R} = \sqrt{2} - 1$$

$$\frac{r_+}{r_-} = 0.414$$

Void	$r_+/r_-$
Cubic	0.732 - 1
Octahedral	0.414 - 0.732
Tetrahedral	0.225 - 0.414
Triangular	0.155 - 0.225


#### Caesium chloride (CsCl)

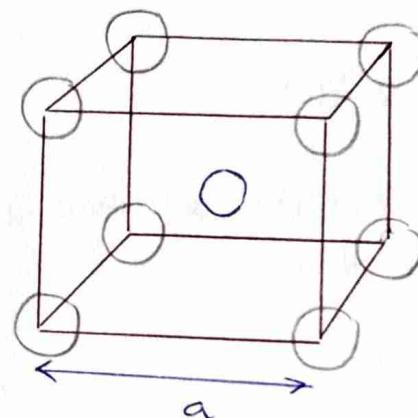

$$r_{\text{Cl}} + r_{\text{Cs}} = \frac{\sqrt{3}}{2} a$$

Simple Cubic  
Not BCC

Tetrahedral

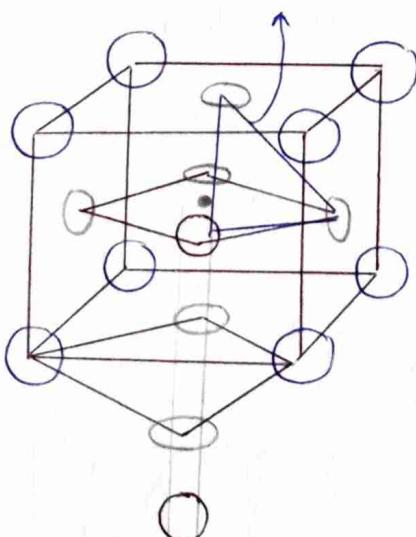

Make an octahedral void and be same for all sides

One edge is shared by 4 edge

At Edge octahedral void formed and contribution is  $\frac{1}{4}$



Body diagonal makes tetrahedral (8)

## Sodium chloride (NaCl)

Octahedral Voids are Occupied by  $\text{Na}^+$

$$2(r_{\text{Cl}^-} + r_{\text{Na}^+}) = a$$
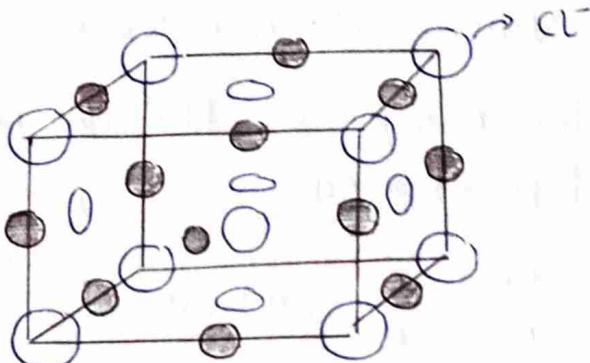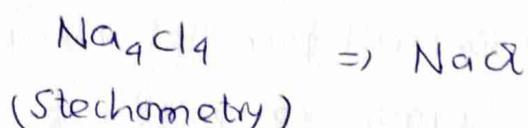
$$r_{\text{Na}^+} + r_{\text{Cl}^-} = \frac{a}{2}$$



No of  $\text{Cl}^-$  atom =

$$\text{Na}^+ \text{ atom } (12 \times \frac{1}{4}) + 1 = 4$$

(NaCl makes FCC structure)

- ⑫ The radius of a Calcium ion is 94pm and of the oxide ion is 146pm. The Possible structure is

$$\Rightarrow \frac{r_+}{r_-} = \frac{94}{146} = 0.643 \quad 0.414 < 0.643 < 0.732$$

Structure is Octahedral

- ⑬ CsI crystallise in BCC lattice. If  $a$  is edge length

$$\Rightarrow r_{\text{Cs}} + r_{\text{I}} = \frac{\sqrt{3}}{2} a$$

- ⑭ CsBr has BCC type structure with edge length 4.3 Å. The shortest inter ionic distance between Cs and Br



$$\Rightarrow \text{Inter ionic distance } r_{\text{Cs}} + r_{\text{Br}} = \frac{\sqrt{3}}{2} a = \frac{\sqrt{3} \times 4.3}{2} = 3.72 \text{ Å}$$

- ⑮ In a Solid AB having NaCl structure. A atoms occupy the corners of unit cell. If all the FCC atoms along one of the axes are removed then the resultant stoichiometry of the solid is

$\Rightarrow$  Removed atom,

$$a = (8 \times \frac{1}{8}) + (4 \times \frac{1}{2}) = 3 \Rightarrow A$$

$$4 \Rightarrow B$$

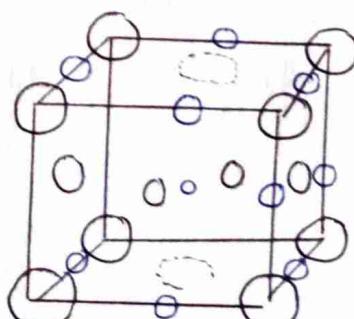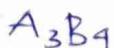

⑯ Tetrahedral void in a crystal implies that

⇒ Void is surrounded by four spheres

⑰ The radius of Na<sup>+</sup> ion is 95 pm and that of Cl<sup>-</sup> is 181 pm.  
type of void

$$\Rightarrow \frac{r_+}{r_-} = \frac{95}{181} = 0.524$$

$$0.414 < 0.524 < 0.732$$

### Direction Indices

[100] represent all parallel indices  
to it (100), (200), (300)

### Family of Planes

{100}

(100) (T00)  
(010) (0T0)  
(001) (00T)

### Family of direction Indices

<100> → Family of direction

[100] [T00] [001] [010] [0T0] [00T]

### Diamond cubic:

FCC lattice → Principal diagonal has 1 atom

1 → FCC

1 → Half of THV

Nearest neighbour


$$\text{distance} = \frac{\sqrt{3}}{4} a = 2r$$

$$r_2 = \frac{\sqrt{3}}{8} a$$

(Structure of  
Diamond)

$$N_{\text{eff}} = 8$$
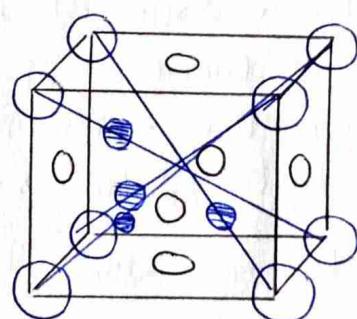
$$P_f = \frac{8 \times \frac{4}{3} \pi r^3}{a^3} = 34\%$$



## Density of Planes


No of atom per unit area

$$(4 \times \frac{1}{4}) = 1$$

$$\text{Area} = a^2$$

No of atom per unit area =  $\frac{1}{a^2}$
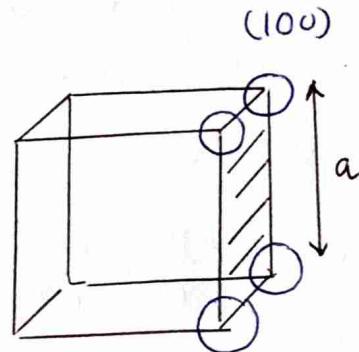
$$\% \text{ pf} = \frac{\text{area of atom}}{\text{area of Sphere}} = \frac{\pi r^2}{a^2} = \frac{\pi r^2}{4r^2} = \frac{\pi}{4} = 0.785$$




## (110) plane FCC

No of atom

$$(4 \times \frac{1}{4}) + (2 \times \frac{1}{2}) = 2$$
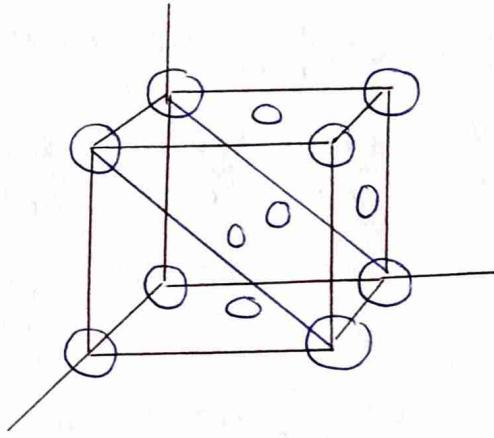
$$\text{per unit area} = \frac{2}{\sqrt{2}a^2} = \frac{\sqrt{2}}{a^2}$$




$$\% \text{ pf} = \frac{2\pi r^2}{\sqrt{2}a^2} = \sqrt{2}\pi \frac{1}{8} = \frac{\sqrt{2}}{8}\pi = 0.555$$

## (111) Plane BCC

Atom per unit area

$$= \frac{\frac{1}{6} \times 3}{\frac{\sqrt{3}}{4} a^2} = \frac{0.5 \times 4}{\sqrt{3} a^2}$$

$$= \frac{2}{\sqrt{3} a^2}$$

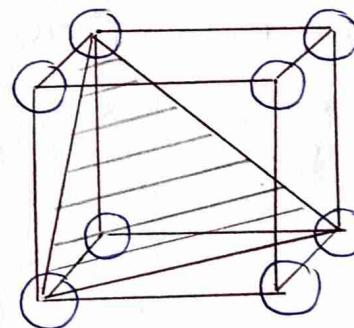

$$\delta = \frac{\sqrt{3}}{4} a$$

$$\% \text{ packing} = \frac{\frac{1}{2} \times \pi r^2}{\frac{\sqrt{3}}{4} \times (\sqrt{2}a)^2} = \frac{1}{2} \times \frac{4}{\sqrt{3}} \times \frac{\pi}{2} \times \frac{r^2}{a^2} = \frac{\pi}{\sqrt{3}} \times \frac{3}{16}$$

- ⑯ The solid phase of an element follows van der Waals bonding with inter-atomic potential  $V(r) = -\frac{P}{r^6} + \frac{Q}{r^{12}}$ . Bond length is

$$\Rightarrow V(r) = -\frac{P}{r^6} + \frac{Q}{r^{12}} \Rightarrow \frac{\partial V}{\partial r} = \frac{6P}{r^7} - \frac{12Q}{r^{13}} = 0$$

$$\frac{6P}{r^7} = \frac{12Q}{r^{13}} \Rightarrow P = \frac{2Q}{r^6} \Rightarrow r = \left(\frac{Q}{P}\right)^{-\frac{1}{6}}$$

- ⑰ The potential of a diatomic molecule as a function of  $r$
- $$V(r) = -\frac{a}{r^6} + \frac{b}{r^{12}}$$
- The value of potential at eqbm

$$\Rightarrow \frac{\partial V}{\partial r} = \frac{6a}{r^7} - \frac{12b}{r^{13}} = 0 \Rightarrow \frac{6a}{r^7} = \frac{12b}{r^{13}} \Rightarrow 6a = \frac{12b}{r^6}$$

$$\Rightarrow r^6 = \frac{2b}{a} \Rightarrow r = \left(\frac{2b}{a}\right)^{\frac{1}{6}}$$

$$V(r) = -\frac{a^2}{2b} + b \frac{a^2}{4b^2} = -\frac{a^2}{2b} + \frac{a^2}{4b} = -\frac{a^2}{4b}$$

- ⑲  $\alpha$ -Co has hcp structure with lattice spacing of  $2.51\text{\AA}$  and height  $4.07\text{\AA}$  and  $\beta$ -Co is FCC with cube sides  $3.55\text{\AA}$ . The ratio of densities

$$\Rightarrow \rho = \frac{Z \text{Neff}}{a^3 N_A} \quad \rho_1 = \frac{6 \times A}{N_A \times 6 \times \frac{\sqrt{3}}{4} a^2 c} \quad \rho_2 = \frac{4A}{N_A a^3}$$

$$\frac{\rho_1}{\rho_2} = \frac{6 \times 4 \times (3.55)^3}{6 \times \frac{\sqrt{3}}{4} \times (2.51)^2 \times 4.07 \times 4} = 1.007$$

- ⑳ If relative density of Tungsten is  $18.8 \text{ gm/cm}^3$  and its atomic weight is 184, assuming that at room temp. there are two free  $e^-$  per atom. density of free  $e^-$

$$\Rightarrow \rho = \frac{\text{Neff} \times 184 \times 10^{-3}}{a^3 \times N_A} \quad \text{Tungsten is BCC so Neff} = 2$$

$$a^3 = 3.25 \times 10^{-29} \quad 1 \text{ atom has } 2e^-$$

$$18.8 \times 10^3 = \frac{2 \times 184 \times 10^3}{a^3 \times N_A} \quad e^- \text{ density} = \frac{4}{a^3} = \frac{4}{3.25} \times 10^{-6}$$

$$= 1.23 \times 10^{23} / \text{cm}^3$$

From Bragg's law,

$$n\lambda = 2d \sin\theta \Rightarrow \lambda = 2d \sin\theta$$

$$\frac{1}{d} = (2 \sin\theta) \frac{1}{\lambda} \Rightarrow \frac{2\pi}{d} = (2 \sin\theta) \left(\frac{2\pi}{\lambda}\right)$$

( $\frac{1}{d} = \sigma$  is Reciprocal Lattice)


It is a theoretical concept

$$\frac{1}{\text{Volume}} = \frac{1}{\text{area}} \times \frac{1}{\text{height}}$$

$$\frac{\text{area}}{\text{Volume}} = \frac{1}{\text{height}}$$


$$\frac{(\vec{b} \times \vec{c})}{\vec{a} \cdot (\vec{b} \times \vec{c})} = \frac{1}{d_{hkl}}$$
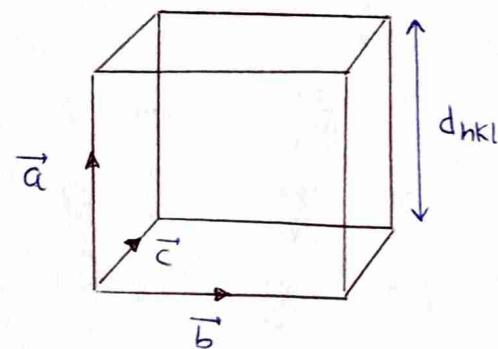
$$2\pi \left[ \frac{\vec{b} \times \vec{c}}{\vec{a} \cdot (\vec{b} \times \vec{c})} \right] = \sigma_{hkl}$$


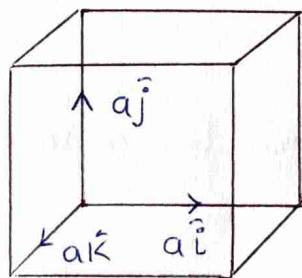
### Primitive unit cell

$$2\pi \left[ \frac{\vec{c} \times \vec{a}}{\vec{a} \cdot (\vec{b} \times \vec{c})} \right] = \vec{b}^*$$



$$\begin{cases} \vec{a} = a\hat{i} \\ \vec{b} = b\hat{j} \\ \vec{c} = c\hat{k} \end{cases} \quad \begin{matrix} \text{Primitive} \\ \text{Vectors} \end{matrix}$$

$$2\pi \left[ \frac{\vec{a} \times \vec{b}}{\vec{a} \cdot (\vec{b} \times \vec{c})} \right] = \vec{c}^*$$

$$2\pi \left[ \frac{\vec{b} \times \vec{c}}{\vec{a} \cdot (\vec{b} \times \vec{c})} \right] = \vec{a}^*$$



Reciprocal of Simple Cubic is also Simple Cubic  
Volume =  $(\frac{2\pi}{a})^3$

$$\vec{a}^* = \frac{2\pi}{a} \hat{i}$$

$$\vec{b}^* = \frac{2\pi}{a} \hat{j}$$

$$\vec{c}^* = \frac{2\pi}{a} \hat{k}$$

## Face centred cubic

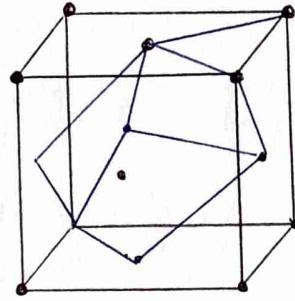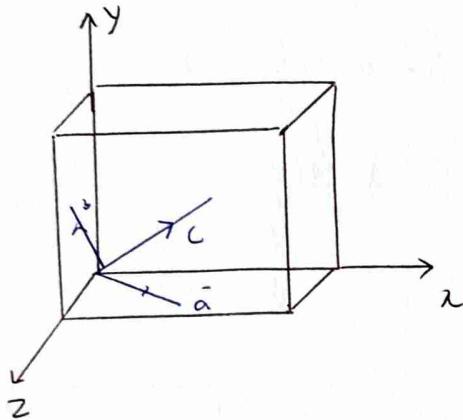

$$\vec{a} = \frac{a}{2} \hat{i} + \frac{a}{2} \hat{k}$$

$$\vec{b} = \frac{a}{2} \hat{j} + \frac{a}{2} \hat{k}$$

$$\vec{c} = \frac{a}{2} \hat{i} + \frac{a}{2} \hat{j}$$

$$\vec{a}^* = \frac{2\pi}{a} (\hat{i} - \hat{j} + \hat{k})$$

$$\vec{b}^* = \frac{2\pi}{a} (-\hat{i} + \hat{j} + \hat{k})$$

$$\vec{c}^* = \frac{2\pi}{a} (\hat{i} + \hat{j} - \hat{k})$$

Reciprocal of BCC  $\rightarrow$  FCC  
FCC  $\rightarrow$  BCC

$$\vec{a} \cdot \vec{a}^* = 2\pi$$

$$\vec{a} \cdot \vec{b}^* = 0$$

$$\vec{b} \cdot \vec{b}^* = 2\pi$$

$$\vec{a}_i \cdot \vec{a}_j = 2\pi \delta_{ij}$$

- (22) The relation of the reciprocal basis vector  $\vec{A}$  to direct basis  $\vec{a}$  is given by

$$\Rightarrow \vec{A} \cdot \vec{a} = 2\pi$$

- (23) Given that the edge of diamond is  $0.356\text{ nm}$ . The number of atoms per meter cube is

$$\text{No of atom} = \frac{8}{(0.356 \times 10^{-9})^3} = \frac{8}{4.5 \times 10^{-29}} = 1.77 \times 10^{29} \text{ m}^{-3}$$

- (24) FCC is reciprocal of BCC lattice

Insulators

Conductivity is Low

Resistivity is High

Conductors

Conductivity is High


Resistivity is Low.

> Need of Semiconductors

- Value of Current (charge) can be controlled.
- Conductivity can be controlled.
- Unidirectional Current flow is possible.
- In diode unidirectional flow happens

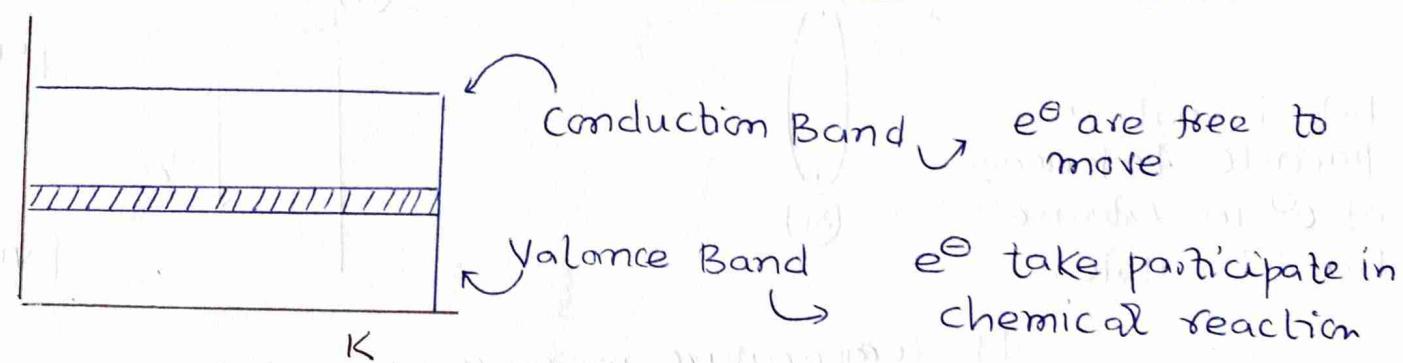Examples


- Elemental Semiconductors: Si, Ge
- Compound Semiconductors: InP, GaAs



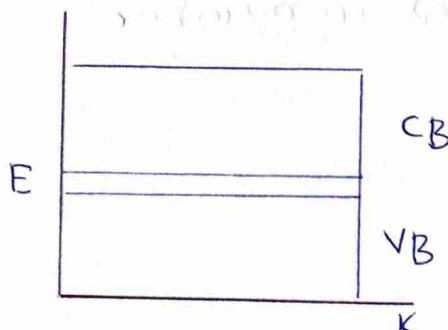
(a) Energy of Valence Band.  $-\infty$  to  $E_V$

Conduc<sup>n</sup> Band  $E_C$  to  $\infty$


> Gap between the two bands is Energy Band Gap  $E_g$



Conductors

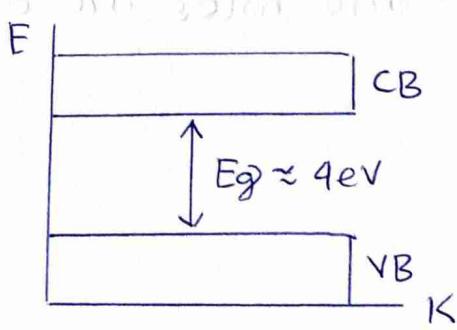

Insulators (67)

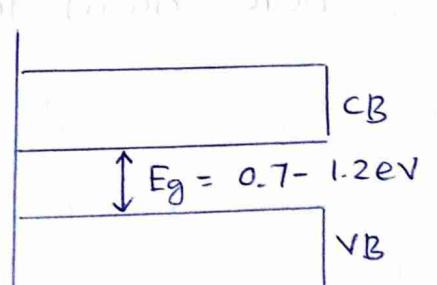

Semiconductors

## Semiconductors

Intrinsic SC  
(Pure Semiconductor)

Extrinsic SC  
(Doping)

p-type

N-type


09.10.2024

### Intrinsic Semiconductor:


At T=0K

VB is completely filled

CB is completely empty

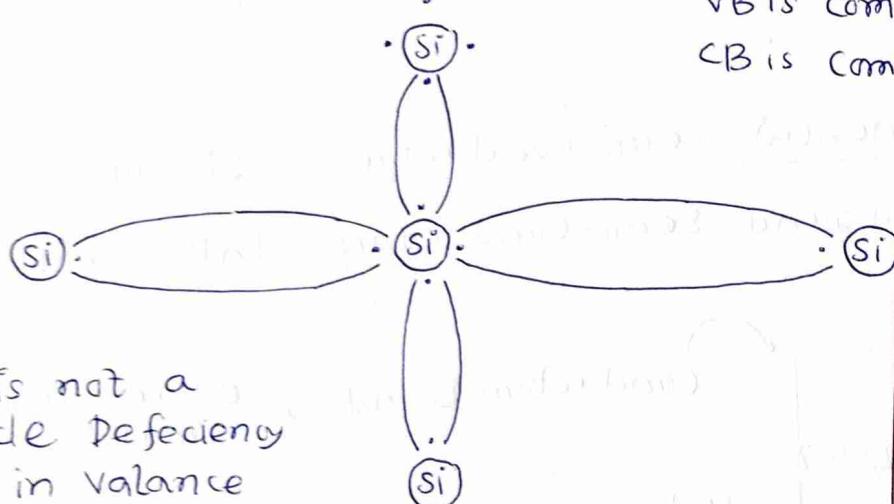

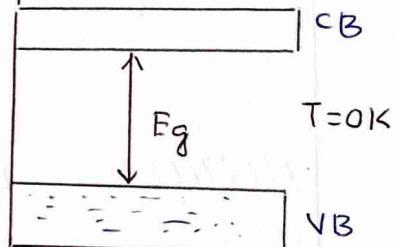Hole is not a particle. Deficiency of  $e^-$  in Valance band is Hole.



If temperature increase. Some holes created in Valance band some hole goes to Conduction band. At 0K Semiconductor behave like insulator and at high temperature it behave like conductors.

- > Direction of movement of  $e^-$  is just opposite to the Hole.
- > Here no of free  $e^-$  and holes are equal in number

## Extrinsic Semiconductors.

### (a) N-type SC:


> The extra  $e^-$  of P is out of bond at even OK

> Here two types  $e^-$  -


(a) Thermally generated

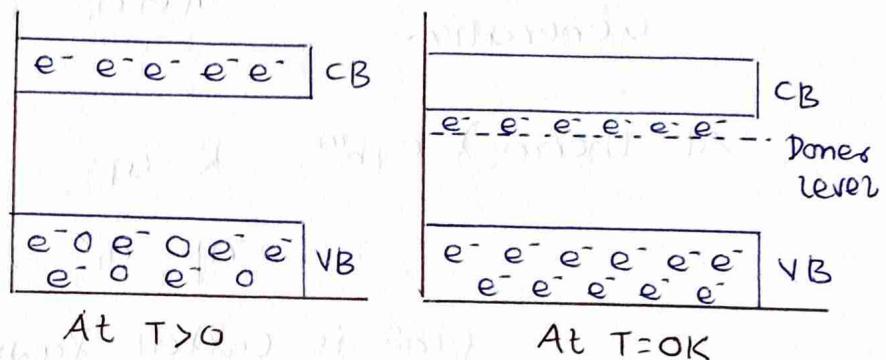(b) Adding impurity.


> Holes are just thermally generated hole.



### (b) p-type SC:

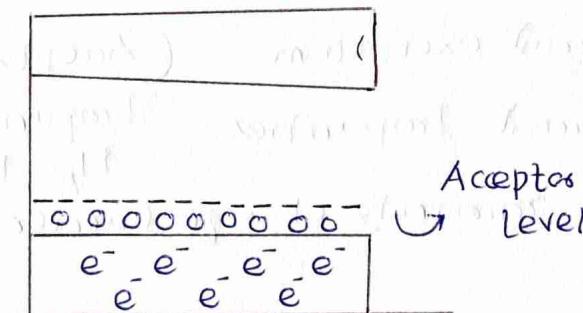

At  $T = 0$

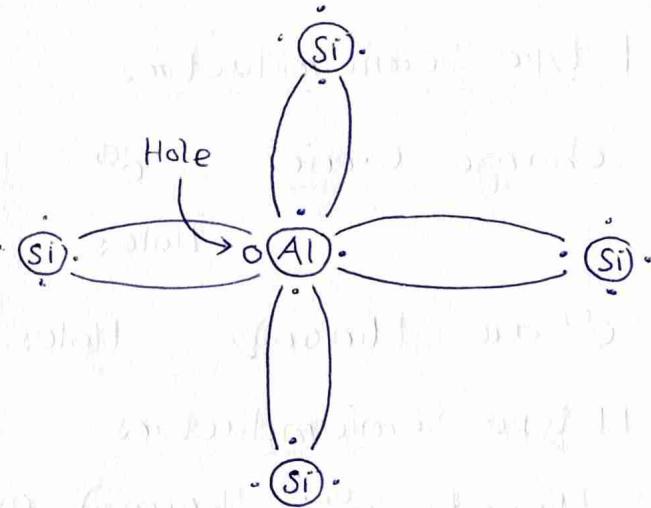

At  $T = 0K$ , only Holes are present

$T \uparrow$ . Thermally generated Holes & electrons

Majority  $\Rightarrow$  Hole

Minority  $\Rightarrow$  Electron

(p-type)

Majority  $\Rightarrow$  Electron

Minority  $\Rightarrow$  Hole

(n-type)

> For Intrinsic Semiconductor

If T increase  $e^-$  became free and hole created.

This is the generation of  $e^-$ -Hole Pair

> electron comes to Hole  $\Rightarrow$  Recombination

Rate of  
Recombination

$R \propto n$  ( $e^-$  density)

$\propto p$  (Hole density)

$$\text{So } R \propto np$$

Rate of  
Generation

$G \propto n^2$  (Intrinsic Carrier Concentration)

$$\text{At thermal eqm } R = G$$

$$np = n^2 \Rightarrow n_i = \sqrt{np}$$

(This is called Laws of mass action)

> P-type Semiconductors

charge carriers:  $e^-$ : Thermal excitation (Acceptors)  
Holes: Thermal, Impurities (Impurities)

$e^-$  are Minority, Holes are minority charge carrier Neg

> N-type Semiconductors:

Majority  $e^-$ : Thermal excitation, Impurities

Minority Holes: Thermal excitation

(Donor Impurities)  $N_D \rightarrow$  Positive

> N-type and P-type has no net charge (Neutral)

> From the principle of Electrical Neutrality we have

$$n + N_A = p + N_D$$

> For N-type semiconductor,  $N_A = 0$

$$n + N_A = p + N_D \Rightarrow n = p + N_D \Rightarrow N_D = n - p$$

But here  $n \gg p$ ,  $N_D = n$

From the Laws of mass action

$$np = n_i^2 \Rightarrow p = \frac{n_i^2}{N_D}$$

> Similarly for P-type semiconductor,  $n = \frac{n_i^2}{N_A}$

### Electron Concentration in Conduction Band:

Density of state,  $g(p) dp = \left( \frac{4\pi p^2 dp}{h^3} \right) \sqrt{2mE}$

Energy,  $p = \sqrt{2mE}$

$$2pdP = 2mdE \quad g(E) dE = \frac{4\pi}{h^3} \sqrt{2mE} \frac{mdE}{\sqrt{2mE}}$$

$$dp = \frac{mdE}{\sqrt{2mE}}$$

$$g(E) dE = \frac{4\pi}{h^3} \sqrt{2mE} mdE \times 2$$

$$f(E) = \frac{1}{e^{\frac{E-E_f}{kT}} + 1} \quad N = \int f(E) g(E) dE$$

$$N = V \int_{E_c}^{\infty} \frac{8\sqrt{2}\pi m^{3/2} E^{1/2} dE}{h^3} \frac{1}{e^{\frac{E-E_f}{kT}} + 1}$$

$$= \frac{8\sqrt{2}\pi m^{3/2} V}{h^3} \int_{E_c}^{\infty} \frac{E^{1/2} dE}{e^{\frac{E-E_f}{kT}} + 1}$$

$$n = \frac{NE}{V} = \frac{8}{h^3} \sqrt{2m^{3/2}} \pi \int_{E_c}^{\infty} \frac{E^{3/2} dE}{e^{\frac{E-E_f}{kT}} + 1} \quad \frac{E-E_f}{k_B T} \gg 1$$

$$\text{or } n = \gamma \int_{E_c}^{\infty} E^{3/2} e^{-\frac{(E-E_f)}{kT}} dE$$

$$\text{or } n = \gamma \int_{E_c}^{\infty} E^{3/2} e^{-\frac{(E-E_c+E_f-E_f)}{kT}} dE$$

$$\text{or } n = \gamma \int_{E_c}^{\infty} E^{3/2} e^{-\frac{(E_c-E_f)}{kT}} e^{-\frac{(E-E_c)}{kT}} dE$$

$$\text{or } n = \gamma \cdot e^{-\frac{(E_c-E_f)}{kT}} \int_{E_c}^{\infty} E^{3/2} e^{-\frac{(E-E_c)}{kT}} dE$$

$$\text{or } n = \gamma \cdot e^{-\frac{(E_c-E_f)}{k_B T}} \int_{E_c}^{\infty} (E-E_c)^{3/2} e^{-\frac{(E-E_c)}{k_B T}} dE$$

$$\text{or } n = \gamma \cdot e^{-\frac{(E_c-E_f)}{kT}} \int_{0}^{\infty} (K_B T)^{3/2} x^{3/2} e^{-x} \cdot K_B T dx \quad \text{put } x = \frac{E-E_c}{K_B T}$$

$$\text{or } n = \gamma \cdot e^{-\frac{(E_c-E_f)}{kT}} \int_0^{\infty} (K_B T)^{3/2} e^{-x} x^{3/2} dx$$

$$\text{or } n = \gamma \cdot e^{-\frac{(E_c-E_f)}{kT}} \cdot (K_B T)^{3/2} \int_0^{\infty} e^{-x} x^{3/2} dx$$

$$\text{or } n = \frac{8\sqrt{2} \lambda m^{3/2}}{h^3} \cdot \frac{1}{2} \sqrt{\pi} (K_B T)^{3/2} e^{-\frac{(E_c-E_f)}{kT}}$$

$$\text{or } n = 2 \left[ \frac{2\pi m K_B T}{h^3} \right]^{3/2} e^{-\frac{(E_c-E_f)}{kT}}$$

$$\text{or } n = N_c e^{-\frac{(E_c-E_f)}{kT}}$$

## Electronic Concentration

$$n = 2 \left( \frac{2\pi m_e^* K_B T}{h^2} \right)^{3/2} e^{-\frac{(E_c - E_F)}{K_T}}$$

$$m^* = \frac{\hbar^2}{(\frac{d^2 E}{d k_u})}$$

$$p = 2 \left( \frac{2\pi m_h^* K_B T}{h^2} \right)^{3/2} e^{-\frac{(E_F - E_v)}{K_T}}$$

## Intrinsic Semiconductor

Here we have,  $n = p$

$$2 \left( \frac{2\pi m_e^* K_B T}{h^2} \right)^{3/2} e^{-\frac{(E_c - E_F)}{K_T}} = 2 \left( \frac{2\pi m_h^* K_B T}{h^2} \right)^{3/2} e^{-\frac{(E_F - E_v)}{K_T}}$$

$$e^{-\frac{(E_c - E_F - E_v + E_F)}{K_B T}} = \left( \frac{m_h^*}{m_e^*} \right)^{3/2}$$

$$E_F = \frac{E_c + E_v}{2} + \frac{3}{4} K_B T \ln \left( \frac{m_h^*}{m_e^*} \right)$$

At  $T=0K$

$$E_F = \frac{E_c + E_v}{2}$$

$$m_h^* > m_e^*$$

> From the law of mass action we have

$$n_i^2 = n_p = N_c e^{-\frac{(E_c - E_F)}{K_T}} N_v e^{-\frac{(E_F - E_v)}{K_T}}$$

$$= N_c N_v e^{-\frac{(E_c - E_v)}{K_T}}$$

$$n_i^2 = N_c N_v e^{-\frac{E_g}{K_T}}$$

$$n_i = \sqrt{N_c N_v} e^{-\frac{E_g}{2K_B T}}$$

①  $I = I_0 \left(1 - \frac{V}{V_0}\right)^2$  The Parameter  $V_0$  and  $\sqrt{I_0}$  can be graphically determined by

$$\Rightarrow I = I_0 \left(1 - \frac{V}{V_0}\right)^2$$

$$\Leftrightarrow \sqrt{I} = \sqrt{I_0} \left(1 - \frac{V}{V_0}\right)$$

$$\Leftrightarrow \frac{\sqrt{I}}{\sqrt{I_0}} = 1 - \frac{V}{V_0}$$

$$\Leftrightarrow \frac{V}{V_0} = 1 - \frac{\sqrt{I}}{\sqrt{I_0}}$$

$$\begin{aligned} & V = V_0 - \frac{V_0}{\sqrt{I_0}} \sqrt{I} & y = V \\ & y = c + mx & x = \sqrt{I} \\ & \text{Slope, } m = -\frac{V_0}{\sqrt{I_0}} & \\ & \text{Intercept, } c = V_0 & \end{aligned}$$


② I-V characteristic of a device  $I = I_s \left[ \exp\left(\frac{av}{T}\right) - 1 \right]$

The graph between  $\log I$  and  $\frac{av}{T}$  will be

$$\Rightarrow I = I_s e^{\frac{av}{T}}$$

$$\log I = \log I_s + \frac{av}{T}$$

Ohm's Law in Vector Form

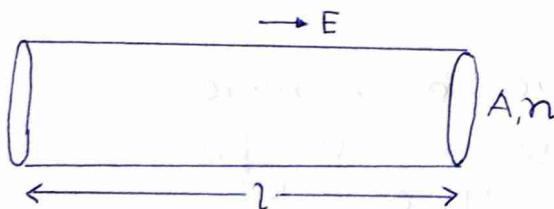

$$\begin{aligned} ma &= eE \\ a &= \frac{eE}{m} \end{aligned}$$

$$V_d = u + at = \frac{eEZ}{m}$$

$$i = \frac{(nA\lambda)e}{t}$$

$$i = \frac{(nA\lambda)eV_d}{\lambda}$$

$$i = neAV_d$$

$$\frac{i}{A} = neV_d$$

$$J = ne \cdot \frac{eEZ}{m}$$

$$J = \left(\frac{ne^2}{m}\right) E$$

$$\vec{J} = \sigma \vec{E}$$

Conductivity

$$\sigma = \frac{ne^2}{m}$$

$$\rho = \frac{m}{ne^2}$$

$$\text{Mobility } \mu = \frac{V_d}{E} = \frac{eEZ}{mE} = \frac{eZ}{m} \Rightarrow \mu \propto \frac{1}{m^*}$$

$$\text{So } \mu_e \gg \mu_h \quad \sigma = \frac{ne^2}{m} \quad \sigma = ne\left(\frac{eZ}{m}\right)$$

Now in case of semiconductor

$$\sigma = ne\mu$$

$$J = J_e + J_p = (n_e \mu_e e + n_p \mu_p e) E = \sigma E$$

$$\boxed{\sigma = (n_e \mu_e + n_p \mu_p)}$$

If we remove  $e^-$  from donor impurity, we get  $N_d^+$

$$\text{So } N_d^+ = N_d [1 - f(E_d)] \quad E_d \Rightarrow \text{Energy of donor level}$$

$$\text{or } N_d^+ = N_d \left[ 1 - \frac{1}{1 + e^{-\frac{(E_f - E_d)}{KT}}} \right] \quad f(E) = \frac{1}{1 + e^{\frac{E - E_f}{KT}}}$$

$$\text{or } N_d^+ = N_d \left[ \frac{1 - e^{-\frac{(E_f - E_d)}{KT}}}{1 + e^{-\frac{(E_f - E_d)}{KT}}} \right] \quad f(E_d) = \frac{1}{1 + e^{\frac{E_d - E_f}{KT}}}$$

$$\text{or } N_d^+ = N_d \left[ \frac{e^{-\frac{(E_f - E_d)/KT}}}{1 + e^{-\frac{(E_f - E_d)/KT}}} \right]$$

$$\text{or } N_d^+ = N_d e^{-\frac{(E_f - E_d)}{K_B T}}$$

$$2E_f - (E_c + E_d) = K_B T \ln \left( \frac{N_d}{N_c} \right)$$

$$E_f = \frac{E_c + E_d}{2} + \frac{K_B T \ln \left( \frac{N_d}{N_c} \right)}{2}$$

For n-type semiconductor


$$n = N_d^+$$

$$N_c e^{-\frac{(E_c - E_f)}{K_B T}} = N_d e^{-\frac{(E_f - E_d)}{K_B T}}$$

$$e^{(-E_c + E_f + E_d - E_f)/K_B T} = \frac{N_d}{N_c}$$

$$\text{At } T=0 \quad E_f = \frac{E_c + E_d}{2}$$

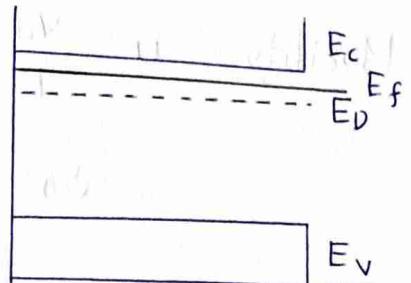So For n-type Semiconductor  
Ef shifted to upward



(For n-type sc)

So basically

$$E_f = \frac{E_c + E_d}{2} + \frac{k_B T}{2} \ln \left( \frac{N_a}{N_c} \right)$$

$$N_c = 2 \left( \frac{2\pi m k_B T}{h^2} \right)^{3/2}$$

If T increase, Nc also decrease, fermi level will be shifted to downward. (For n-type Semiconductor)

> p-type:

$$p = n + N_a^-$$

$$p = N_a^- \quad (N_a^- \gg n)$$

$$N_a^- = N_a f(E_a)$$

$$N_a^- = N_a \left[ \frac{1}{1 + e^{-(E_a - E_f)/kT}} \right]$$

$$N_a^- = N_a e^{-(E_a - E_f)/kT}$$

$$p = N_v e^{-(E_f - E_v)/kT}$$

For p type semic

$$N_a^- = p$$


$$\frac{N_a}{N_v} = e^{-(E_a - E_f - E_v + E_f)/kT}$$

$$-\chi_n \left( \frac{N_a}{N_v} \right) = -(E_a - 2E_f + E_v)/kT$$

$$-kT \chi_n \left( \frac{N_a}{N_v} \right) = 2E_f - (E_a + E_v)$$

$$2E_f = (E_a + E_v) + kT \ln \left( \frac{N_a}{N_v} \right)$$
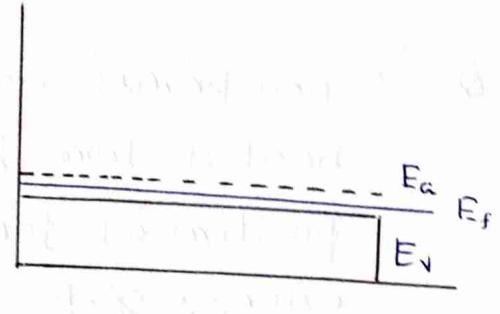
$$E_f = \frac{E_a + E_v}{2} + \frac{kT}{2} \ln \left( \frac{N_a}{N_v} \right)$$



Q. The resistivity of an intrinsic semiconductor is  $4.5\ \Omega$  at  $20^\circ\text{C}$  and  $2\ \Omega$  at  $32^\circ\text{C}$ . Find  $E_g$

$$\sigma = \frac{1}{\rho} = e n_i u_i$$

$$\frac{S_1}{S_2} = \frac{n_2}{n_1} \Rightarrow \frac{4.5}{2} = \frac{n_2}{n_1} \Rightarrow \frac{n_2}{n_1} = 2.25$$

$$e^{-\frac{E_g}{2kT_1} + \frac{E_g}{2kT_2}} = 2.25$$

$$e^{\frac{E_g}{2k} \left( \frac{1}{T_2} - \frac{1}{T_1} \right)} = 2.25$$

$$\frac{E_g}{2k} \left( \frac{1}{305} - \frac{1}{293} \right) = \ln(2.25)$$

$$-E_g \times (4.86 \times 10^{10}) = 0.8109 \Rightarrow E_g = 1\text{eV}$$

Q. The Concentration of electrons  $n$  and holes  $p$ , for an intrinsic Semiconductor at a temp  $T$  can be expressed as  $n = p = AT^{3/2} \exp(-\frac{E_g}{2k_B T})$ . If the mobility of both types of carrier is proportional to  $T^{-3/2}$  then the log of conductivity is a linear function of  $T^{-1}$  with slope

$$\Rightarrow \chi_n \sigma = \chi_n K' - \frac{E_g}{2k_B T}$$


$$\text{Slope is } -\frac{E_g}{2k_B}$$

$$\sigma = K' e^{-E_g/2kT}$$

- Q. A phosphorus doped silicon (doping density =  $10^{17}/\text{cm}^3$ ) is heated from  $100^\circ\text{C}$  to  $200^\circ\text{C}$  then  
 $\Rightarrow$  position of fermi level moves towards middle of energy gap
- Q. For an intrinsic semiconductor, at finite temperature the Position of fermi level  
 $\Rightarrow$  depends on both  $m_e^*$  and  $m_h^*$
- Q. If  $K_B = 8.625 \times 10^{-5} \text{ eV/K}$

The band gap of the semicond
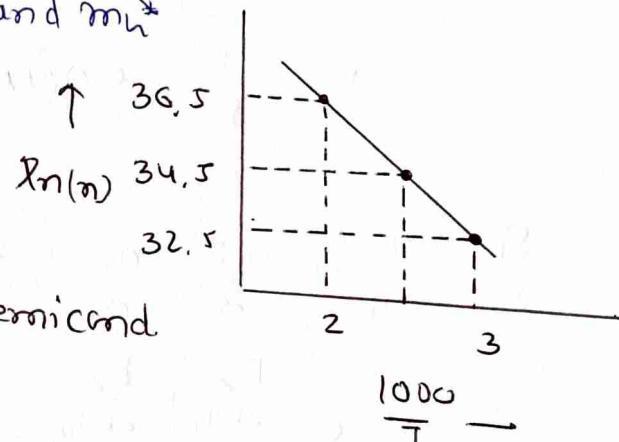
$$\Rightarrow n_i = c e^{-\frac{E_g}{2K_B T}}$$



$$E_F(n_i) = E_{FC} - \frac{E_g}{2K_B T} \times \frac{1000}{1000}$$

$$m = \frac{-E_g}{2 \times 1000 \times K_B T}$$

$$\text{Slope} = \frac{36.5 - 32.5}{2 - 3} = -4$$

$$E_g = 8000 K_B T = 0.69 \text{ eV}$$

- Q. In a Crystalline Solid, the energy band structure for an  $e^-$  is

$$E = \frac{\hbar^2 K (2K-3)}{2m}$$

The effective mass of the  $e^-$  in the crystal is

$$\Rightarrow m_e^* = \frac{\hbar^2}{\left(\frac{d^2 E}{d K^2}\right)} = \frac{m}{2}$$

$$E = \frac{\hbar^2 (2K^2 - 3K)}{2m}$$

$$\frac{dE}{dK} = \frac{\hbar^2}{2m} (4K-3)$$

$$\frac{d^2 E}{d K^2} = \frac{2\hbar^2}{m}$$

Q. An intrinsic Semiconductor of band gap 1.25 eV has an electron concentration  $10^{10} \text{ cm}^{-3}$  at 300K. If the e<sup>-</sup> concentration at 200K is  $4 \times 10^N \text{ cm}^{-3}$ . Find N

$$\Rightarrow \frac{(n_i)_1}{(n_i)_2} = \frac{e^{-E_g/2k_B T_1}}{e^{-E_g/2k_B T_2}}$$

$$\frac{10^{10}}{(n_i)_2} = e^{\frac{E_g}{2k_B} \left( \frac{1}{T_2} - \frac{1}{T_1} \right)} = e^{\frac{1.25}{2k_B} \left( \frac{1}{200} - \frac{1}{300} \right)}$$

Value of N is 4


Q. The ratio of e<sup>-</sup> densities in the CB of Ge ( $E_g = 0.7 \text{ eV}$ ) and silicon ( $E_g = 1.14 \text{ eV}$ ) at 127°C is

$$\Rightarrow n_1 \alpha e^{-E_g/2KT}$$

$$\frac{n_1}{n_2} = \frac{e^{-\frac{E_{g1}}{2KT}}}{e^{-\frac{E_{g2}}{2KT}}} = e^{\frac{E_{g2} - E_{g1}}{2KT}} = 588$$
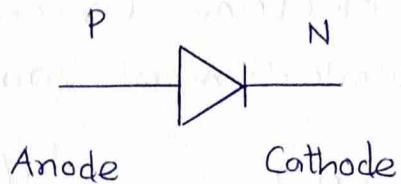
## p-n junction Diode

If doping Concentration increase depletion layer became decrease.



Diode equation is

$$I = I_s \left[ e^{\frac{qV}{nKT}} - 1 \right]$$

$e$  is electronic charge

$V$  is diode voltage

$\eta$  is ideality factor

$T$  is temperature

$$\eta = 1 \text{ (Ge)}$$



$$= 2 \text{ (Si)}$$

$I_s$  is reverse saturation current  
 $I$  is forward current

Required Voltage is

Knee voltage

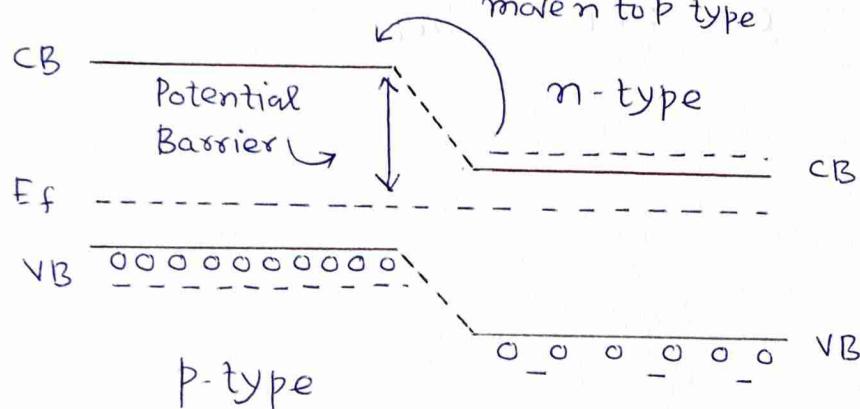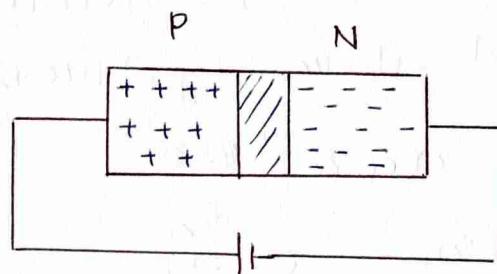By potential energy  $e^G$  move to p type



$$I = I_s \left[ e^{\frac{ev}{nKT}} - 1 \right]$$

$$I = I_s \exp\left(\frac{ev}{\eta KT}\right)$$

## Reverse Bias


Here Current is very low and

$$I = I_s \left[ e^{\frac{ev}{nKT}} - 1 \right]$$


$$V = 0$$


$$I = I_s e^0 = I_s$$

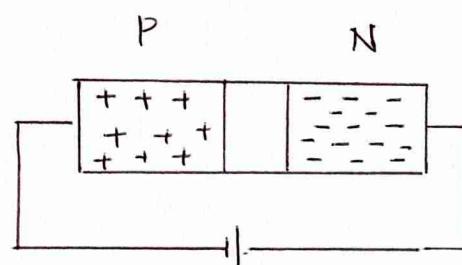$I_s$  is very low and tends to zero (mA unit)




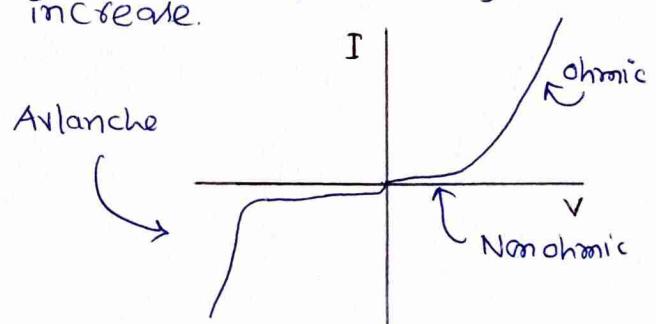with reverse voltage width of depletion layer increase.







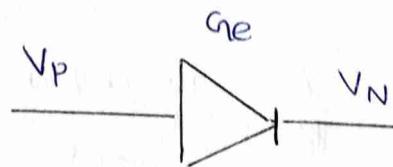


$$FB: V_p > V_N + 0.3$$

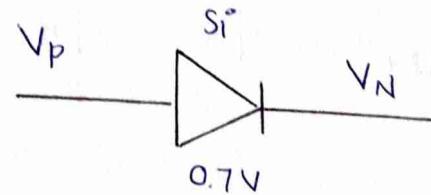

$$FB: V_p > V_N + 0.7$$

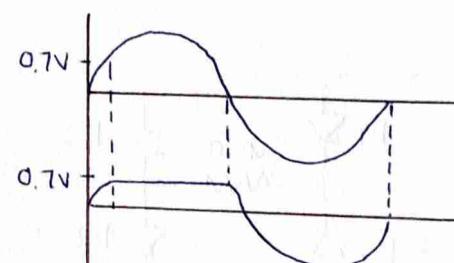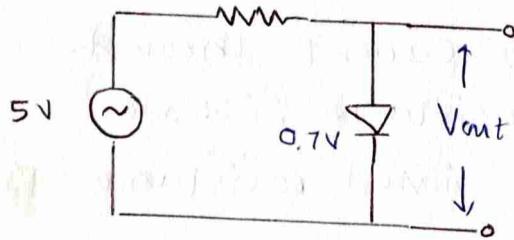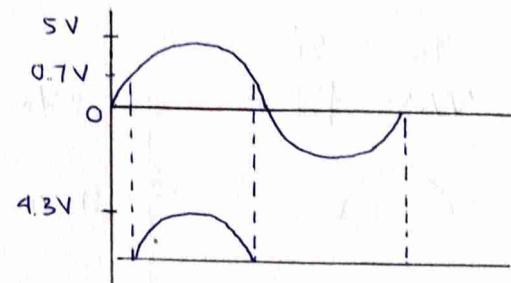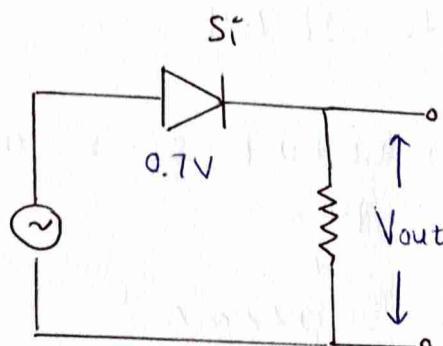

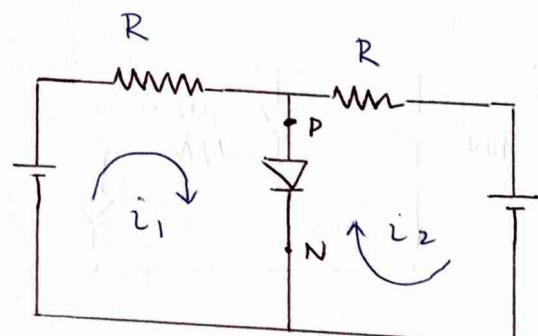First assume diode is in forward bias. Then if the current through diode is positive then our assumption is correct.



① Find the current in circuit

$$-5 + 20i_1 + 30(i_1 - i_2) = 0$$

$$50i_1 - 30i_2 = 5$$

$$20i_2 + 30(i_2 - i_1) = 0$$



$$i_2 = \frac{3}{5} i_1$$


$$i_1 = \frac{5}{32} A$$

$$i_2 = \frac{3}{32} A$$

So assumption is wrong

$$i = \frac{5}{50} A$$

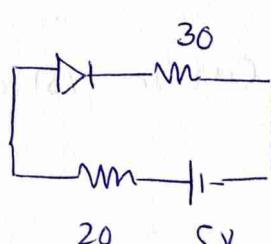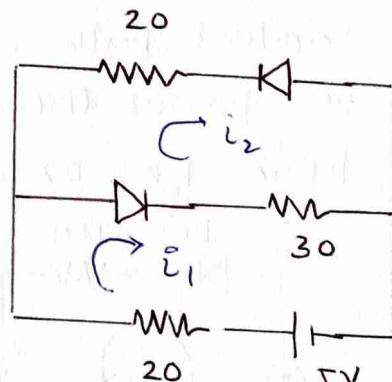


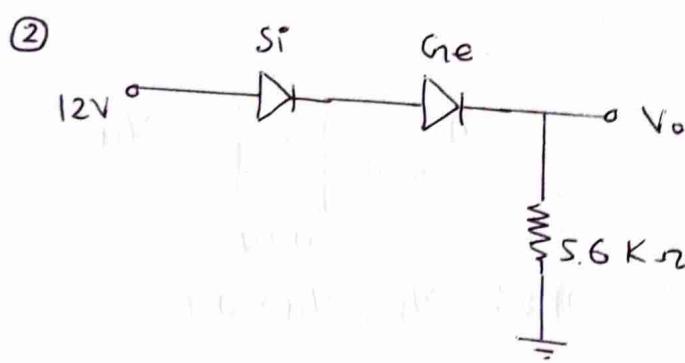

$$i_2 = \frac{V}{R} = \frac{12 - 0.7 - 0.3}{5.6}$$

$$V_o = iR = 12 - 0.7 - 0.3$$


$$V_o = 11 \text{ Volt}$$

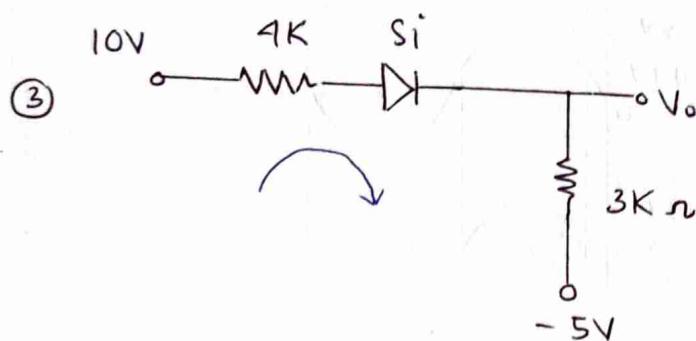


$$-10 + 9i + 0.7 + 3i - 5 = 0$$

$$i = \frac{14.3}{12}$$

$$i = 2.042 \text{ mA}$$

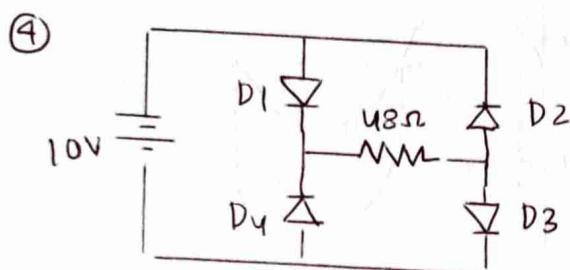


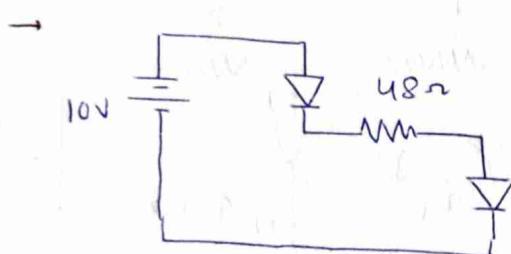Find the current through  
48Ω resistance Si diode,  
forward biased resistance = 1Ω




$$i = \frac{V}{R} = \frac{10}{48+1+1}$$

$$i = \frac{10}{50} = 0.2$$

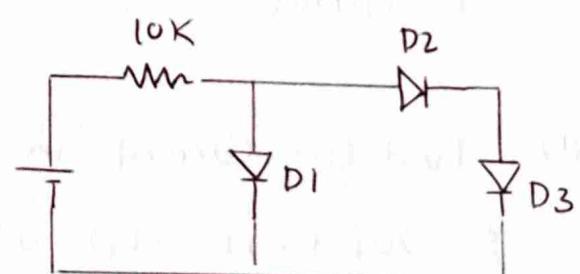

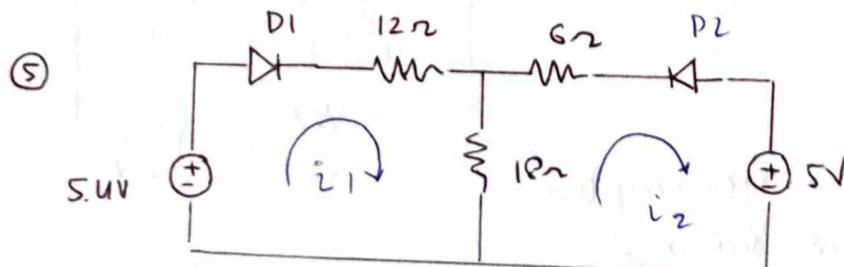④ As the current will follow  
shortest path so it will  
be passes through D1  
D1 in FB & D2, D3 in RB



Cut in Voltage 0.6V

$$-5.4 + 0.6 + 12i_1 + 18(i_1 - i_2) = 0$$


$$6i_2 - 0.6 + 5 + 10(i_2 - i_1) = 0$$

$$i_1 = 0.49 \text{ A}$$

$$i_2 = -0.55 \text{ A}$$

Both diodes are in forward Bias

⑥

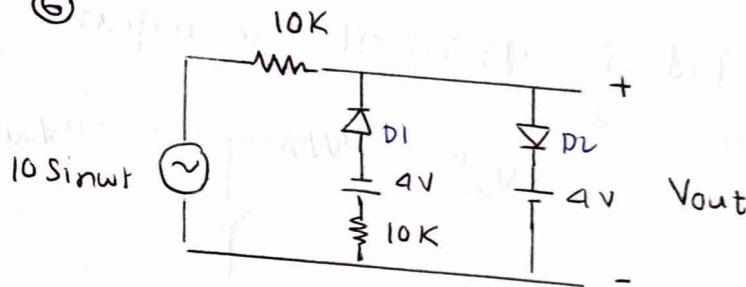

The max & min values of the output waveform

For Positive half cycle, D1 is reverse Bias

$$0 - 4 \text{ Volt}$$

D2 is reverse Bias

$$4 - 10 \text{ Volt}$$



D2 is forward Bias

$$V_{\min} = -7 \text{ Volt}$$

In negative half cycle D2 is reverse Bias

$$V_{\max} = 4 \text{ Volt}$$

⑦

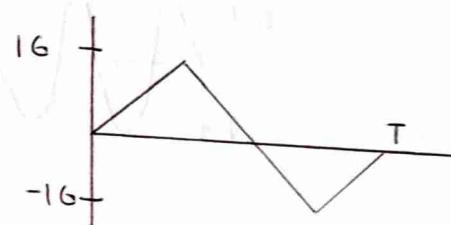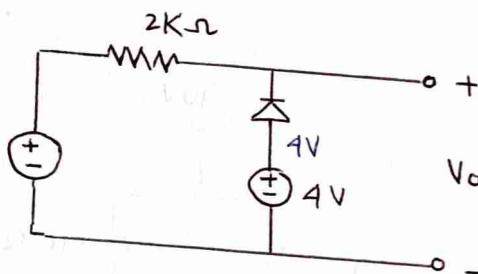

(+)  $\frac{1}{2}$  cycle


Forward

$0 - 4 \text{ V} \Rightarrow$  Diode is reverse Bias  $\Rightarrow V_{in} \neq V_{out} \Rightarrow V_{out} = 4 \text{ Volt}$

$V_i > 4 \text{ V} \Rightarrow$  Diode Reverse Bias  $\Rightarrow V_{in} = V_{out} = V_{in} = V_{out}$



(-)  $\frac{1}{2}$  cycle n term is zero volt.

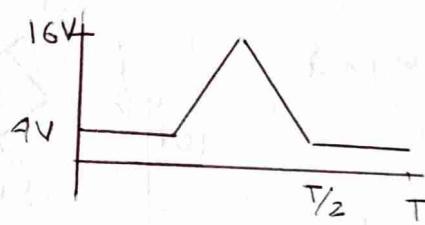Diode is always forward Bias  $V_{out} = 4 \text{ Volt}$





⑧

Determine the output waveform

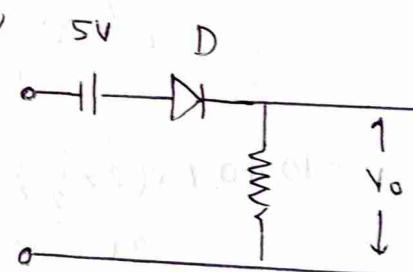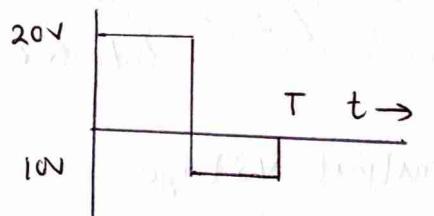

When  $V_i = 20 \text{ Volt}$  D is FB

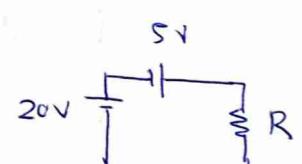
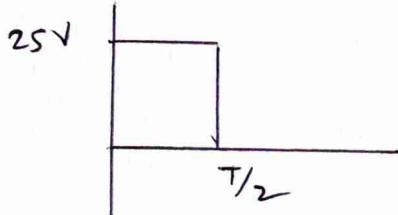


$$-25i + R = 0$$

$$i = \frac{R}{25} \cdot \frac{25}{R}$$


$$i = 25 \text{ Volt}$$

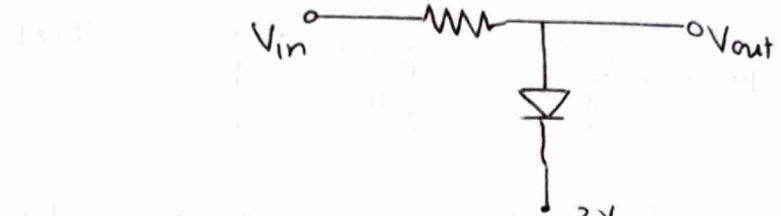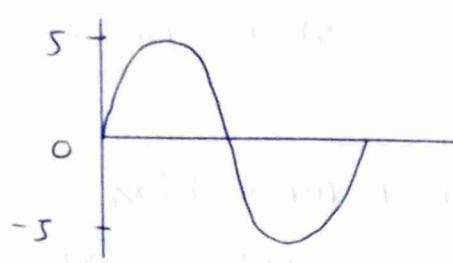⑨ A Sine wave of 5V amplitude is applied at the input of the circuit then  $V_{out} = ?$



when  $V_{in} = 5 \text{ Volt}$

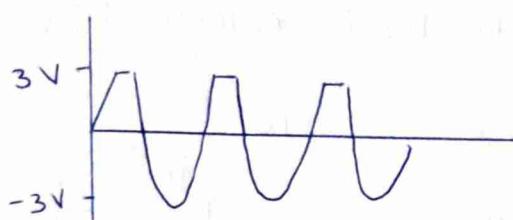
When 0-3 Volt Diode is reverse Bias,  $V_{in} = V_{out}$



⑩ The diode is

$$\Rightarrow V_a = \frac{10 \times 8}{10+8} = 8 \text{ Volt}$$
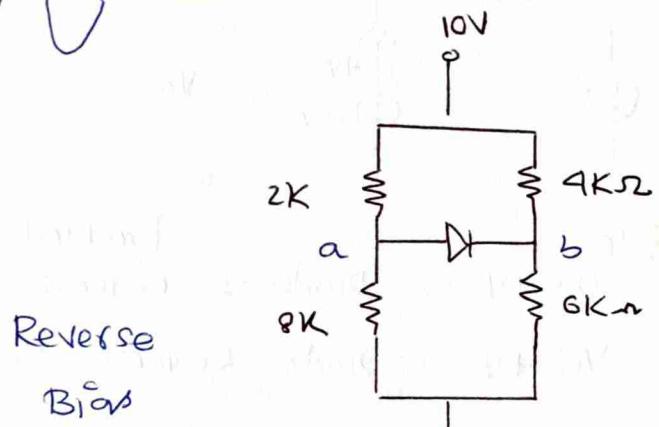
$$V_b = \frac{10 \times 6}{10} = 6 \text{ Volt}$$



⑪ The Value of  $V_o$  is equal to

$$-10i + 0.7 + 2\frac{i}{2} + 2i = 0$$


$$4i = 9.3$$

$$i = \frac{9.3}{4} \text{ A}$$

$$-10 + 0.7 + (2 \times \frac{i}{2}) + 2i = 0$$

$$3i = 9.3$$

$$i = 3.1 \text{ A}$$

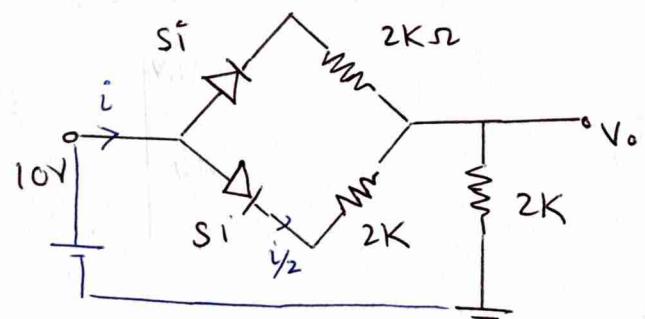


$$V_o = 2i \times \frac{9.3}{2} = 4.65$$

A.A: 6.2 Volt

output Voltage

$$V_o = 2i = 6.2 \text{ A}$$

## Rectifiers

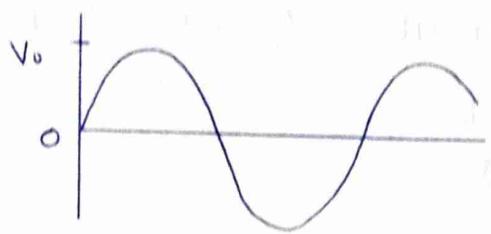

Voltage,  $V = V_0 \sin \omega t$

$$\text{and } T = \frac{2\pi}{\omega}$$

$$V_{avg} = 0$$


$$V_{rms} = V_0 / \sqrt{2}$$

$$\text{Average } \langle V \rangle = \frac{1}{T} \int_0^T V dt = \frac{1}{2\pi/\omega} \int_0^{2\pi/\omega} V_0 \sin \omega t dt$$

$$\langle V \rangle = \frac{V_0 \int_0^{2\pi/\omega} \sin \omega t dt}{2\pi/\omega} = 0$$

$$\langle V^2 \rangle = \frac{\int V^2 dt}{\int dt} = \frac{\int_0^{2\pi/\omega} V_0^2 \sin^2 \omega t dt}{\int_0^{2\pi/\omega} dt} = \frac{V_0^2 \cdot \frac{\pi}{\omega}}{2\pi/\omega} = \frac{V_0^2}{2}$$
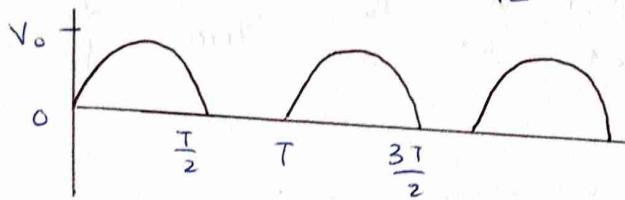
$$V_{rms} = \sqrt{\langle V^2 \rangle} = \frac{V_0}{\sqrt{2}}$$



$$V(t) = \begin{cases} V_0 \sin \omega t & 0 < t < \pi/\omega \\ 0 & \pi/\omega < t < 2\pi/\omega \end{cases}$$

Average of V,

$$\langle V \rangle = \frac{\int_0^{\pi/\omega} V_0 \sin \omega t dt + \int_{\pi/\omega}^{2\pi/\omega} 0 dt}{\frac{2\pi}{\omega}} = \frac{V_0 \omega}{2\pi} \times \frac{1}{\omega} \cos \omega t \Big|_0^{\pi/\omega}$$

$$= \frac{V_0}{2\pi} (1+1) = \frac{V_0}{\pi}$$


$$\langle V \rangle = \frac{V_0}{\pi}$$

$$\langle V^2 \rangle = \frac{\int_0^{\pi/\omega} V_0^2 \sin^2 \omega t dt + \int_{\pi/\omega}^{2\pi/\omega} 0 dt}{\frac{2\pi}{\omega}} = \frac{V_0^2 \omega}{2\pi} \cdot \frac{\pi}{2\omega} = \frac{V_0^2}{4}$$

$$V_{rms} = \sqrt{\langle V^2 \rangle} = \frac{V_0}{2}$$

$$V_{avg} = \frac{V_0}{\pi}$$

$$V_{rms} = \frac{V_0}{2}$$

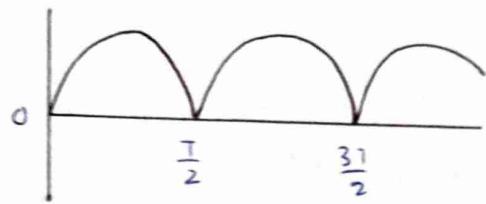

$$V(t) = \begin{cases} V_0 \sin \omega t & 0 < t < \pi/\omega \\ -V_0 \sin \omega t & \pi/\omega < t < 2\pi/\omega \end{cases}$$

$$\langle V^2 \rangle = \frac{\int_0^{\pi/\omega} V_0^2 \sin^2 \omega t dt + \int_{\pi/\omega}^{2\pi/\omega} V_0^2 \sin^2 \omega t dt}{\frac{2\pi}{\omega}}$$

$$\langle V \rangle = \frac{2V_0}{\pi}$$

$$= \frac{V_0^2 \omega}{2\pi} \left[ \frac{\pi}{2\omega} + \frac{1}{2} \int (1 - \cos 2\omega t) dt \right]$$

$$V_{avg} = \frac{2V_0}{\pi}$$





$$V_{rms} = \frac{V_0}{\sqrt{2}}$$

$$= \frac{V_0^2 \omega}{2\pi} \left[ \frac{\pi}{2\omega} + \frac{1}{2} \left[ t - \frac{\sin 2\omega t}{2\omega} \right]_{\pi/\omega}^{2\pi/\omega} \right]$$

$$= \frac{V_0^2 \omega}{2\pi} \left[ \frac{\pi}{2\omega} + \frac{1}{2} \left\{ \left( \frac{2\pi}{\omega} - \frac{\pi}{\omega} \right) - \frac{1}{2\omega} (\sin 4\pi - \sin 2\pi) \right\} \right]$$

$$= \frac{V_0^2 \omega}{2\pi} \left[ \frac{\pi}{2\omega} + \frac{\pi}{2\omega} \right] = \frac{V_0^2 \omega}{2\pi} \cdot \frac{\pi}{\omega} = \frac{V_0^2}{2} \Rightarrow V_{rms} = \frac{V_0}{\sqrt{2}}$$

## Half Wave Rectifiers

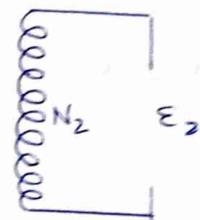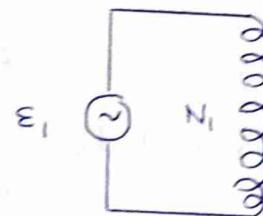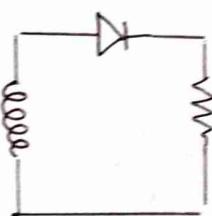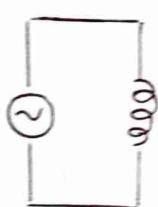

$$V_{DC} = \frac{E_0}{\pi} \quad V_{rms} = \frac{E_0}{2}$$

$$\frac{E_1}{E_2} = \frac{N_1}{N_2}$$

$$E_2 = \frac{N_2}{N_1} E_1$$

$E_2 > E_1 \Rightarrow$  step up

$E_2 < E_1 \Rightarrow$  step down

$$V_{rms} = \sqrt{V_{rms}^2 - V_{DC}^2}$$

$$= E_0 \sqrt{\frac{1}{4} - \frac{1}{\pi^2}} = 0.386 E_0$$



$$\text{Ripple factor, } \gamma = \frac{V_{rms}}{V_{DC}} = \frac{0.386 E_0}{E_0/\pi} = 1.21$$

$$\gamma = \frac{V_{DC}}{V_{rms}} = 40.57\%$$

Efficiency =  $\eta = \frac{V_{DC}}{V_{rms}} = \left(\frac{2}{\pi}\right)^2 = 40.6\%$

Form factor,  $F = \frac{V_{AC}}{V_{DC}} = \sqrt{\frac{2}{\pi}} = 1.57$

### Full wave Rectifier

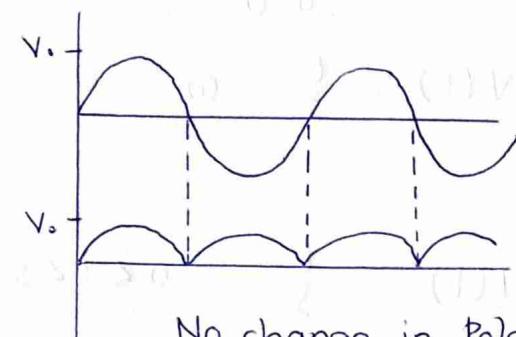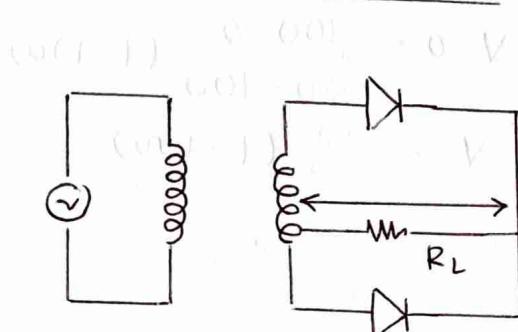

No change in Polarity

$$V(t) = \begin{cases} V_0 \sin \omega t & 0 < t < \pi/\omega \\ -V_0 \sin \omega t & \pi/\omega < t < 2\pi/\omega \end{cases}$$

$$V_{DC} = \frac{2V_0}{\pi}$$

$$V_{rms} = \frac{V_0}{\sqrt{2}}$$



$$V_{rms} = \sqrt{V_{rms}^2 - V_{DC}^2} = \sqrt{V_0^2 \left( \frac{1}{2} - \frac{4}{\pi^2} \right)} = 0.308V_0$$

$$\text{Ripple factor, } \gamma = \frac{V_{rms}}{V_{DC}} = \frac{0.308V_0}{\frac{2V_0}{\pi}} = 0.48$$

$$\text{Efficiency, } \eta = \frac{V_{DC}}{V_{rms}} = \left(\frac{2}{\pi}\right)^2 = 40.6\%$$

### Bridge Rectifier

1st HF	2nd HF
$D_1 \rightarrow FB$	$D_2 \rightarrow FB$
$D_2 \rightarrow RB$	$D_3 \rightarrow RB$
$D_3 \rightarrow FB$	$D_1 \rightarrow RB$
$D_4 \rightarrow RB$	$D_4 \rightarrow FB$

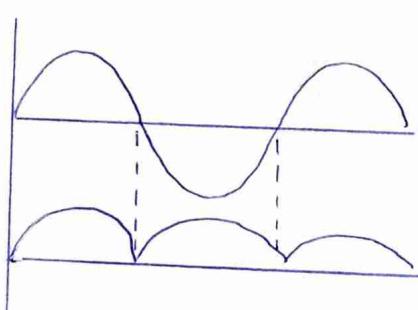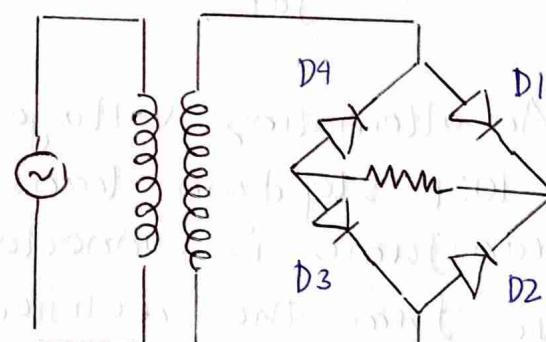

$$V_o = \begin{cases} V_0 \sin \omega t & 0 < t < \pi/\omega \\ -V_0 \sin \omega t & \pi/\omega < t < 2\pi/\omega \end{cases}$$

Due to PIV, it uses over FWR


① Consider a Sawtooth waveform which rises linearly from 0 to 10V. then decays to 0V. linearly to 0V. in 100 ns. The rms voltage is

$\Rightarrow$

$$V - 0 = \frac{10 - 0}{50 - 0} (t - 0)$$

$$V(t) = \frac{t}{5} - 0 \quad \textcircled{1}$$
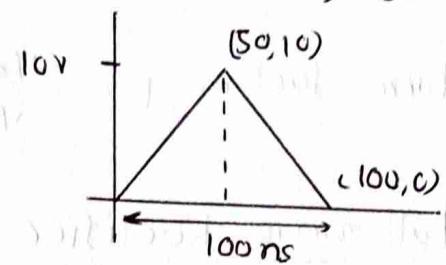
$$\begin{aligned} V(t) &= \frac{t}{5} & 0 < t < 50 \\ &= \frac{t}{5} + 20 & 50 < t < 100 \end{aligned}$$



$$V - 0 = \frac{100 - 0}{50 - 100} (t - 100)$$

$$V = -\frac{1}{5} (t - 100)$$

$$\begin{aligned} \langle V^2 \rangle &= \frac{1}{100} \left[ \int_0^{50} \frac{t^2}{25} dt + \int_{50}^{100} \left( \frac{t^2}{25} - 8t + 400 \right) dt \right] \\ &= \frac{1}{3 \times 25 \times 100} (50)^3 + \frac{1}{100} \left( \frac{1}{75} t^3 - 4t^2 + 400t \right) \Big|_{50}^{100} \\ &= 16.67 + \frac{1}{100} \times \frac{1}{75} \times 875000 - \frac{1}{25} (7500) + \frac{4}{1} \times 50 \\ &= 16.67 + 116.67 - 300 + 200 = 5.77^2 \text{ V} \end{aligned}$$


$$\langle V^2 \rangle = \frac{\int V^2 dt}{\int dt}, \quad V_{rms} = \sqrt{\langle V^2 \rangle} = 5.77 \times 10^{-3} \text{ Volt}$$

② An alternating voltage  $V = 50 \sin 30t$  is applied to a 10:1 stepdown transformer and secondary of this transformer is connected to the input of a hwr V<sub>DC</sub> form the rectifier is

$$\Rightarrow V_o = \frac{50}{10} = 5 \text{ Volt}$$

$$V_{DC} = \frac{V_o}{\pi} = \frac{5}{\pi} \text{ Volt}$$

(3)

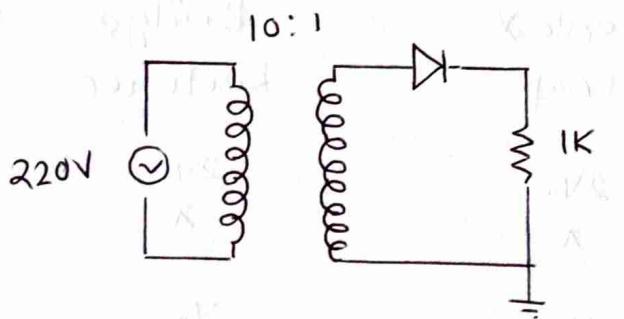


The peak secondary voltage and DC load voltage are respectively

$$V_{\text{peak}} = V\sqrt{2} = 220\sqrt{2} \text{ Volt}$$

For HWR

$$V_{\text{DC}} = \frac{V_p}{\pi} = \frac{31.1}{\pi} = 9.9 \text{ Volt}$$

(4)

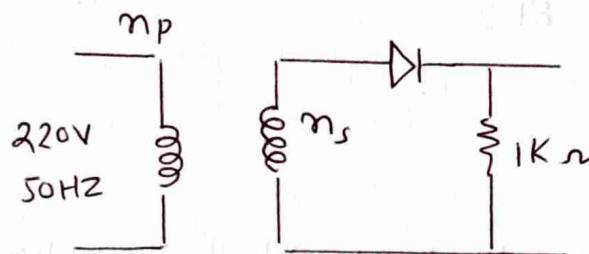


To develop a dc voltage of 10V, the ratio  $n_p:n_s$  is

$$\Rightarrow V_{\text{DC}} = \frac{V_m}{\pi} \quad V_p = 220\sqrt{2} = 311 \text{ V}$$

$$10 = \frac{V_m}{\pi} \quad \frac{n_p}{n_s} = \frac{311}{10\pi} = \frac{10}{1} \quad n_p:n_s = 10:1$$

$$V_m = 10\pi$$

(5)

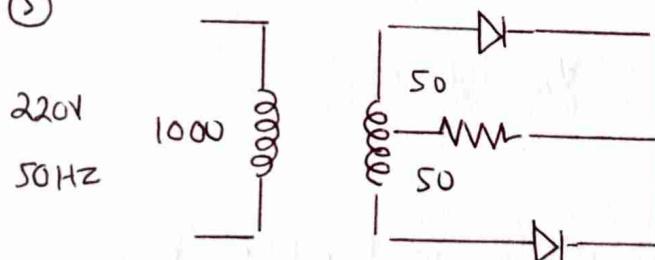

DC Voltage obtained from load is

$$\frac{V_1}{V_2} = \frac{N_1}{N_2} \Rightarrow \frac{1000}{V_2} = \frac{50+50}{220\sqrt{2}}$$

$$\Rightarrow V_2 = 31.1$$

$$V_{\text{DC}} = \frac{2V_m}{\pi} = \frac{2 \times 31.1}{\pi \times 2} = 10 \text{ V}$$

- (6) The Peak Value of AC Voltage across the secondary of the transformer in HWR without filter is  $9\sqrt{2}$  V. The max dc Voltage across the load

$$\Rightarrow V_{\text{DC}} = \frac{V_m}{\pi} = \frac{9\sqrt{2}}{\pi} = 4.02 \text{ Volt}$$

### Half Wave Rectifier

$$V_{DC}$$

$$\frac{V_o}{\pi}$$

$$V_{rms}/V_{DC}$$

$$\frac{2V_o}{\pi} \quad \frac{V_o}{2}$$

$$\gamma$$

$$1.21$$

$$\eta$$

$$40.6$$

### Central Tap

$$\frac{2V_o}{\pi}$$

$$\frac{V_o}{\sqrt{2}}$$

### Bridge Rectifier

$$\frac{2V_o}{\pi}$$


$$\frac{V_o}{\sqrt{2}}$$

$$0.482$$

$$81.2$$
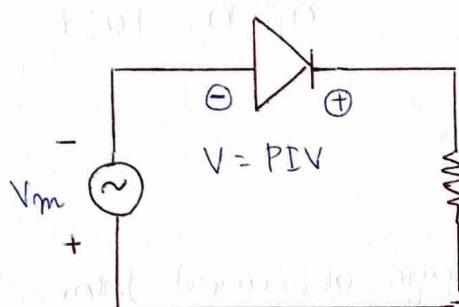
### peak Inverse Voltage

Maximum reverse voltage that should be applied across a diode so that it doesn't reach the breakdown region.




Diode is in off state Voltage across diode is PIV

$$V_m - V = 0 \Rightarrow V = V_m = \text{PIV}$$

$$V_m \leq \text{PIV}$$

HWR:

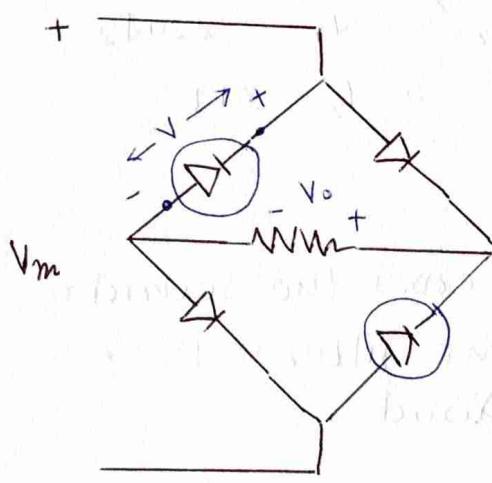


As both the diode in Forward bias

$$\text{we have } V_m = V_o \quad \textcircled{1}$$

$$+V - V_o = 0$$
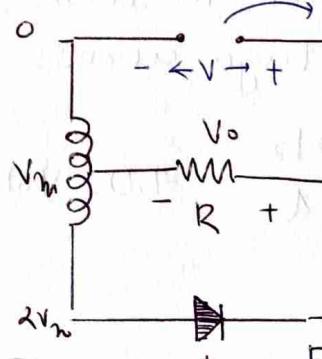
$$V_o = V = \text{PIV} \Rightarrow \text{PIV} = V_m$$



$$-V + V_o + V_m = 0$$

$$V = 2V_m$$

$$\text{PIV} = 2V_m \Rightarrow V_m = \frac{\text{PIV}}{2}$$

As diode is off

$$V = \text{PIV}$$


Bridge Rectifier

# Bipolar Junction Transistor

They are basically two types -


NPN

N	P	N
---	---	---

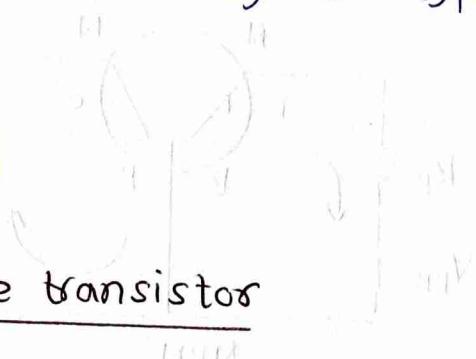

PNP

P	N	P
---	---	---

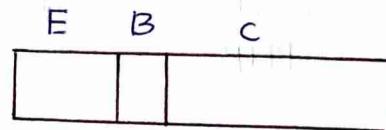

## ① NPN type transistor

Width of

Collector  $\Rightarrow$  Maximum

Base  $\Rightarrow$  Minimum

Emitter  $\Rightarrow$  Moderate

Doping of

Emitter  $\Rightarrow$  Maximum

Base  $\Rightarrow$  Minimum



Collector  $\Rightarrow$  Moderate.

Biassing:



EB Junction is forward Bias

BC Junction is Reverse Bias

## ② Common Emitter (CE) Configuration

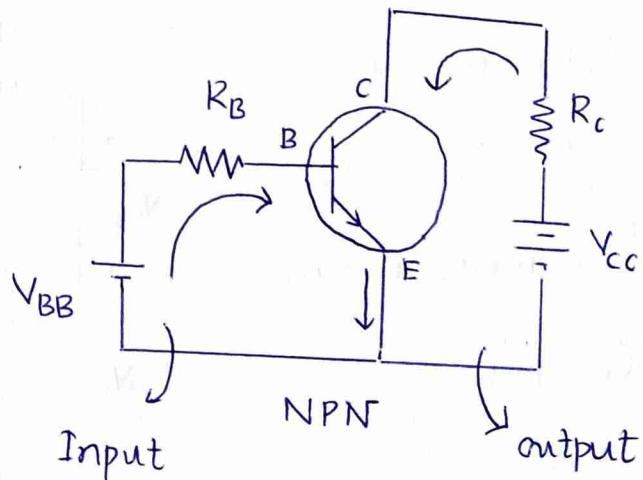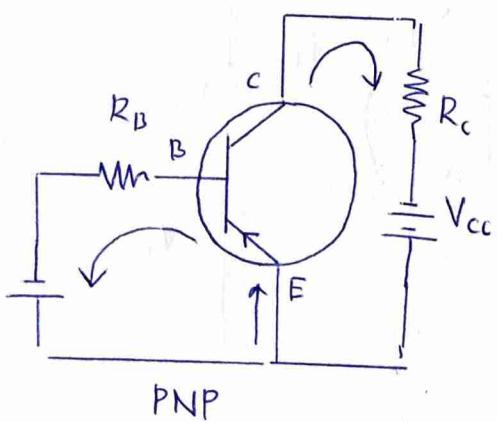

### ③ Common Base Configuration

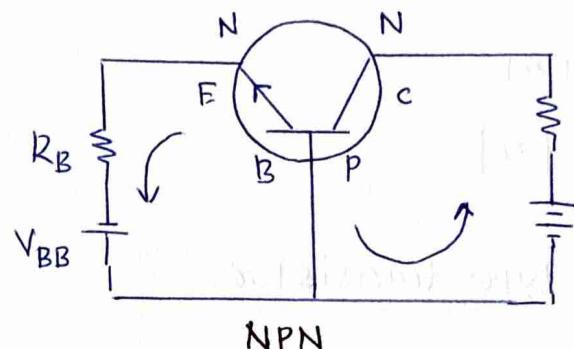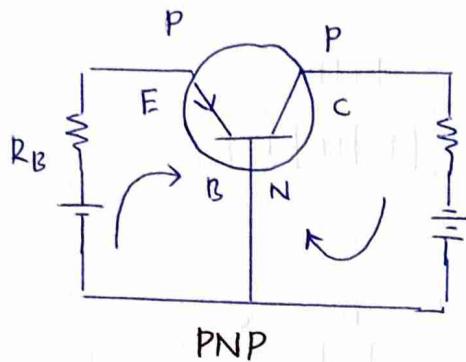

$$I_E = I_B + I_C$$

$I_E$  is input current

$I_C$  is output current

$V_{EB}$  is input voltage

$V_{CB}$  is output voltage  
(For CB Mode)

$I_B$  is input current

$I_C$  is output current

$V_{CB}$  is output voltage

$V_{EB}$  is input voltage  
(For CE Mode)

$$\frac{I_C}{I_E} = \alpha \quad (\text{Current gain})$$

$$\frac{I_C}{I_B} = \beta$$

Now  $I_E = I_B + I_C$

$$\frac{I_C}{\alpha} = \frac{I_C}{\beta} + 1 \Rightarrow \frac{1}{\alpha} = \frac{1+\beta}{\beta} \Rightarrow \alpha = \frac{\beta}{1+\beta} \Rightarrow \beta = \frac{\alpha}{1-\alpha}$$


### ④ Equation of Circuit

$$-V_{BB} + i_B R_B + 0.7 = 0$$

$$\frac{V_{BB} - 0.7}{R_B} = i_B \quad \text{--- ①}$$

Eqn of input circuit

$$i_C = \beta i_B$$

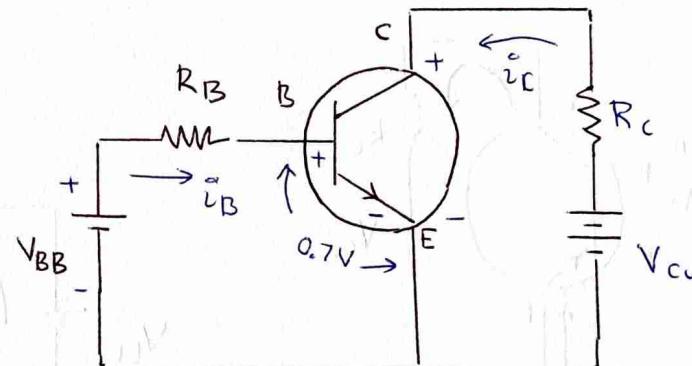

$$-V_{CC} + i_C R_C + V_{CE} = 0$$

$$V_{CE} = V_{CC} - i_C R_C$$

## ⑤ Circuit Analysis


CKt:01

$$-V_{BB} + i_B R_B + V_{BE} = 0$$

$$\text{or } i_B = \frac{V_{BB} - V_{BE}}{R_B}$$

$$\text{Now } i_c = \beta i_B$$

$$V_{CE} = V_C - V_E = V_C$$

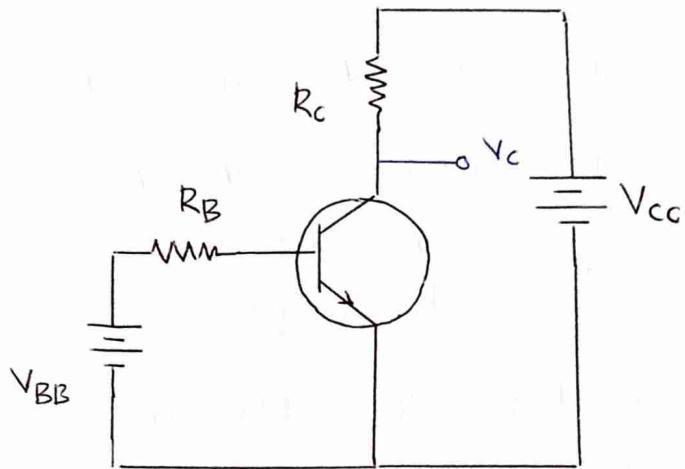


$$i_E = i_c + i_B = \beta i_B + i_B = (1+\beta) i_B \Rightarrow i_E \approx \beta i_B = i_c$$

CKt:02

$$i_B = \frac{V_{CC} - V_{BE}}{R_B}$$

$$i_c = \beta i_B \Rightarrow V_{CE} = V_{CC} - i_c R_C$$
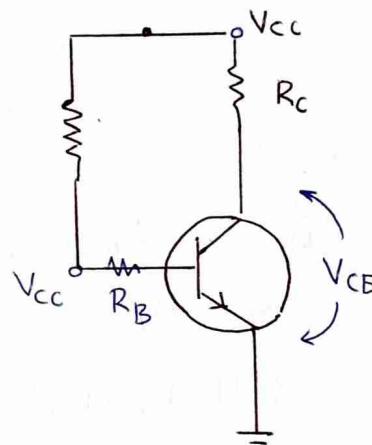
$$\text{As } -V_{CC} + i_c R_C + V_{CC} = 0$$



CKt:03

$$-V_{BB} + i_B R_B + V_{BE} + i_E R_E = 0$$

$$i_B R_B + i_E R_E = V_{BB} - V_{BE}$$


$$i_B R_B + (1+\beta) i_B R_E = V_{BB} - V_{BE}$$

$$i_B [R_B + (1+\beta) R_E] = V_{BB} - V_{BE}$$

$$i_B = \frac{V_{BB} - V_{BE}}{R_B + (1+\beta) R_E}$$

$$\text{As } i_E = (1+\beta) i_B \text{ and } i_c = \beta i_B$$
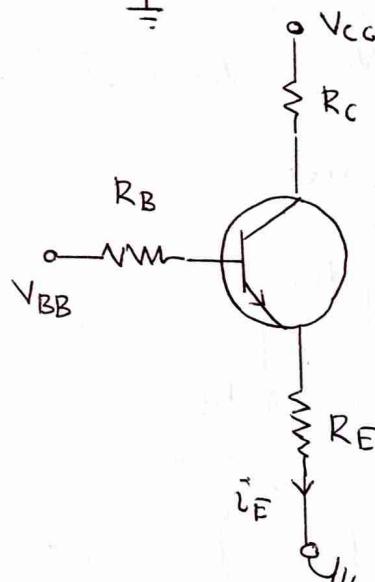
$$\text{Also } -V_{CC} + i_c R_C + i_E R_E + V_{CE} = 0$$



$$i_c = \beta i_B$$

$$i_E = (1+\beta) i_B$$

### CKT on


$$-V_{CC} + i_B R_B + V_{CE} + i_E R_E = 0$$

$$i_B R_B + (1+\beta) R_E = V_{CC} - V_{CE}$$

$$i_B = \frac{V_{CC} - V_{CE}}{R_B + (1+\beta) R_E}$$

$$i_C = \beta i_B \quad i_E = (1+\beta) i_B$$

$$V_{CE} = V_{CC} - i_C R_C - i_E R_E$$

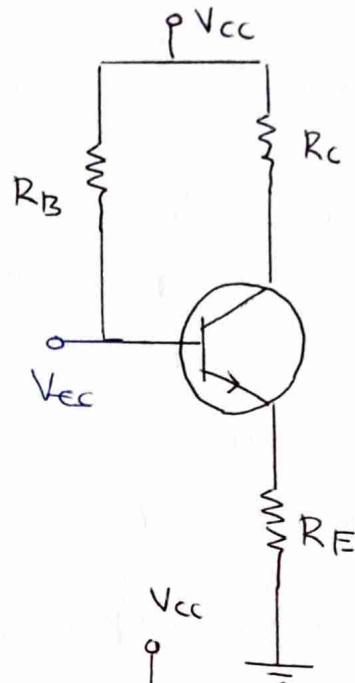


### CKT OS:


$$-V_{CC} + (i_C + i_B) R_C + i_B R_B + V_{BE} = 0$$

$$i_B = \frac{V_{CC} - V_{BE}}{(1+\beta) R_C + R_B}$$

$$V_{CE} = V_{CC} - (i_C + i_B) R_C$$

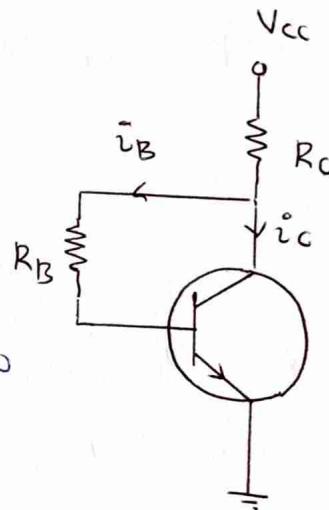


### CKT OS:

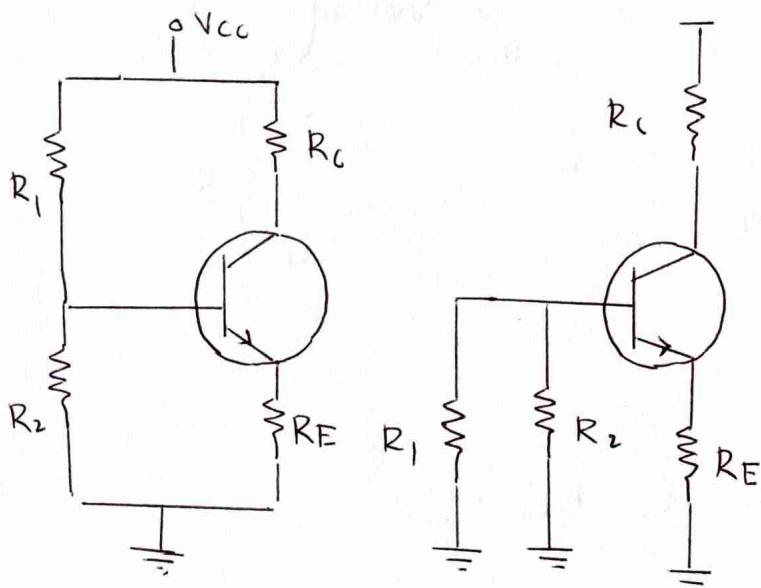

$$V_{th} = \frac{V_{CC} R_2}{R_1 + R_2}$$

$$R_{th} = \frac{R_1 R_2}{R_1 + R_2}$$

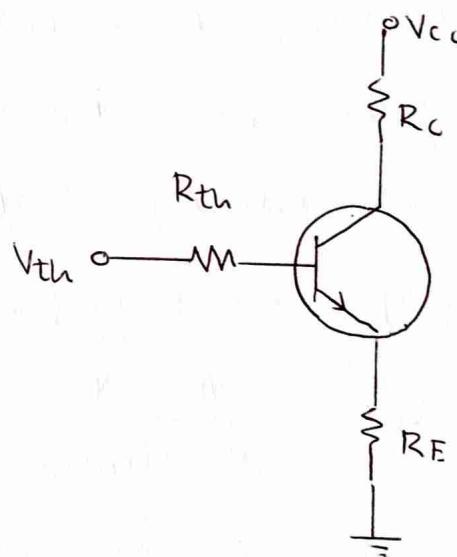


$$-V_{th} + i_B R_{th} + V_{BE} + i_E R_E = 0$$

$$i_B R_{th} + (1+\beta) i_B R_E = V_{th} - V_{BE}$$

$$i_B = \frac{V_{th} - V_{BE}}{R_{th} + (1+\beta) R_E}$$

## ⑥ Common Emitter Configuration

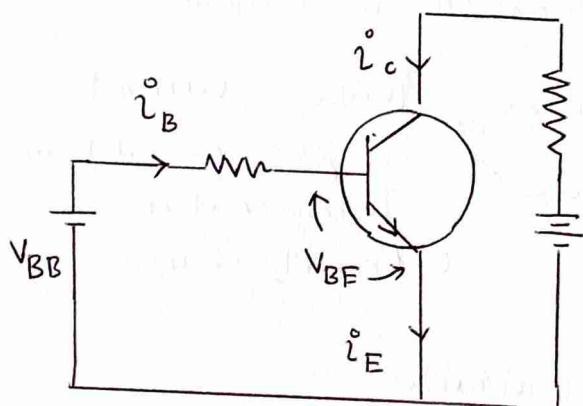

output current  $i_c$


output voltage  $V_{CE}$

$$V_{CE} = V_{CB} + V_{BE}$$

If  $V_{CE} \uparrow \Rightarrow V_{CB} \uparrow$

$V_{BB}$  remain constant

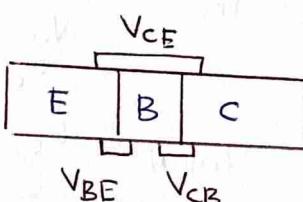As  $V_{CB}$  increase (Reverse Bias), base width became decrease and the depletion layer increases so base current  $i_B$  became decrease.




$V_{BE}$  is almost constant

$$V_{CE} = V_{CB} + V_{BE}$$

## ⑦ Input characteristics

Plot  $I_B$  vs  $V_{BB}$  by taking

$V_{CE}$  as a constant.

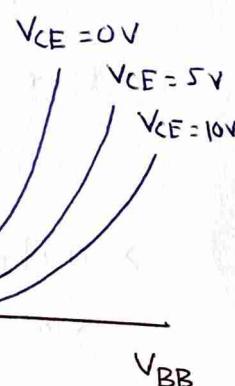

As depletion layer increase the amount of recombination increase so base current became decrease

## ⑧ Output characteristics

Plot  $i_c$  v/s  $V_{CE}$

taking  $i_B$  constant

$$i_c = \beta i_B \text{ (Almost Constant)}$$


$$i_c = \beta i_B + i_{CBO} \quad \text{Due to minority carrier (Leakage current)}$$

$$i_E = i_c + i_B$$

$$\Rightarrow i_c = \alpha (i_c + i_B) + i_{CBO}$$

$$\Rightarrow i_c = \frac{\alpha}{1-\alpha} i_B + \frac{1}{1-\alpha} i_{CBO}$$
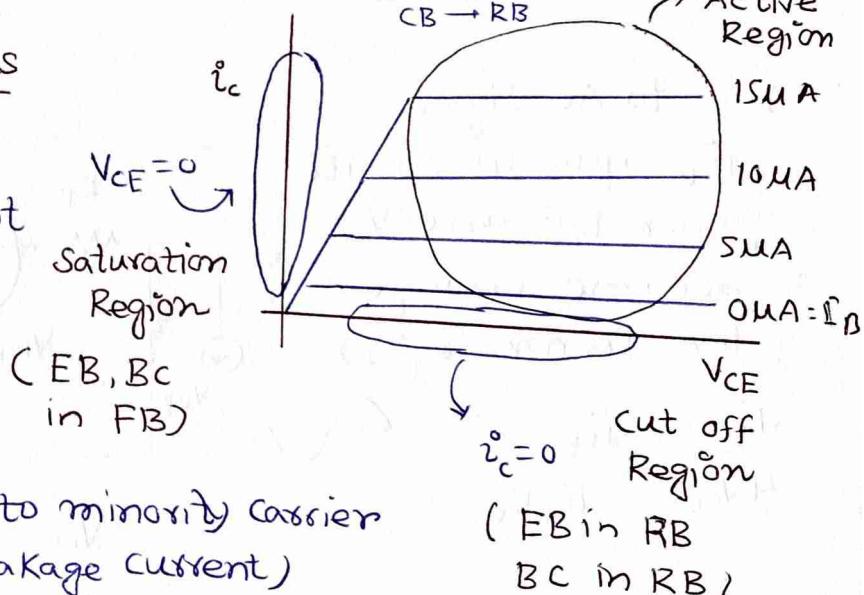
$$\Rightarrow i_c = \beta i_B + (1+\beta) i_{CBO}$$



$$\text{Here } i_{EO} = (1+\beta) i_{CBO}$$

$i_{EO}$  is leakage current in common emitter configuration

## ⑨ Stabilization In Transistors

The process of making an operating point independent (less dependent) of  $B$  and temperature is known as stabilization.

$$\dot{i}_E = \alpha \dot{i}_C + \dot{i}_{CBO}$$

$$\dot{i}_C = B \dot{i}_B + \dot{i}_{CEO}$$

Leakage current is generated from Temperature.  
(Minority charge)

$$\dot{i}_{CEO} = (1+B) \dot{i}_{CBO}$$

After  $\Delta T \rightarrow 10^\circ\text{C}$ ,  $\dot{i}_{CBO}$  became almost double

$V_{BE}$  decrease  $2.5\text{ mV}$  per  $^\circ\text{C}$  temperature increase.


> output characteristics in configuration is

$$\dot{i}_B = \frac{V_{BB} - V_{BE}}{R_B}$$

$$\dot{i}_C = B \dot{i}_B \Rightarrow \Delta \dot{i}_C = B \Delta \dot{i}_B$$

$$V_{CE} = V_{CC} - \dot{i}_C R_C$$
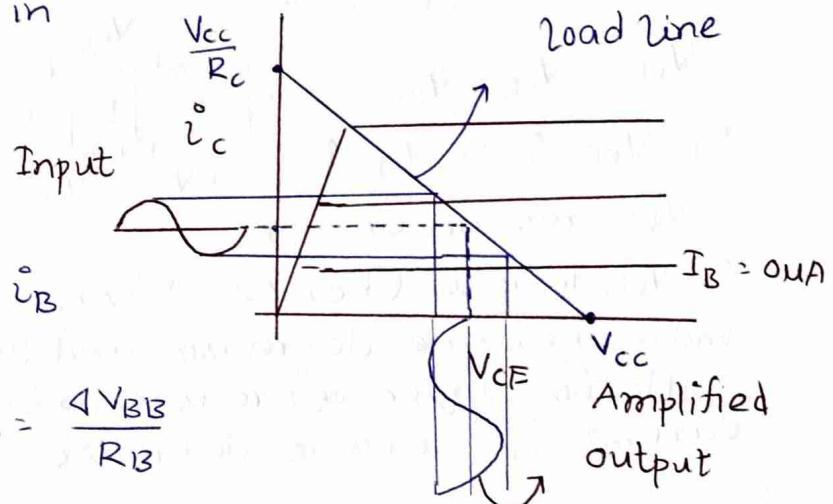
$$\Delta V_{CE} = - \Delta \dot{i}_C R_C$$




Due to AC Signal

$\Delta \dot{i}_B$  appears so  $\Delta \dot{i}_C$  generated and  $V_{CE}$  became change (from previous eq's)

$$\Delta \dot{i}_C = B \Delta \dot{i}_B$$
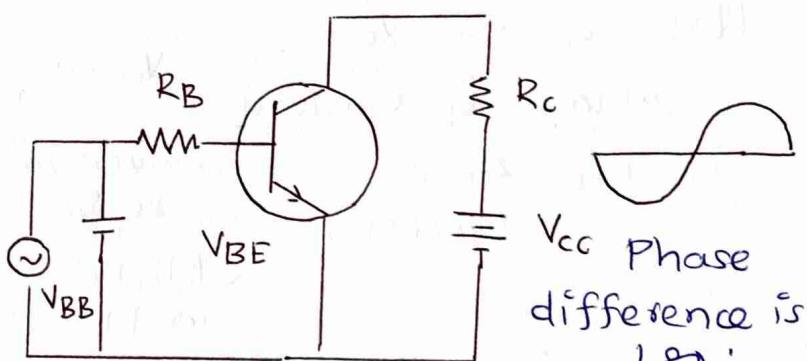
$$\Delta V_{CE} = - \Delta \dot{i}_C R_C$$



$$V_{CE} = V_{CC} - \dot{i}_C R_C$$

$$\dot{i}_C = 0, \quad V_{CE} = V_{CC}$$


$$V_{CE} = 0, \quad \dot{i}_C = \frac{V_{CC}}{R_C}$$

Load line

>  $(I_c, V_{CE})$  is operating point and we have to choose it very carefully. For amplification this point should be lies in active region

$$V_{CE} = V_{CC} - i_c R_C$$


Question

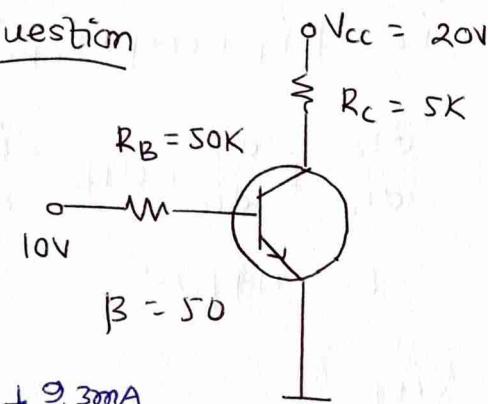

Find the Q-point

$$V_{CC} = i_c R_C + V_{CE}$$

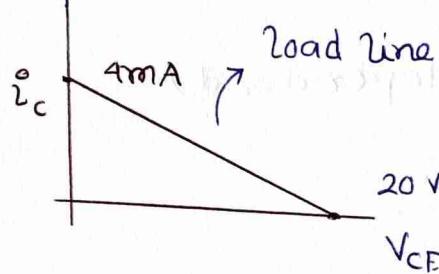
$$\begin{aligned} V_{CE} &= V_{CC} - i_c R_C \\ &= 20 - i_c \times 5k \end{aligned}$$



$$\bar{i}_B = \frac{10 - 0.7}{50} = 0.18 \text{ mA}$$

$$\begin{aligned} \bar{i}_c &= \beta \bar{i}_B = 9.3 \text{ mA} > (\bar{i}_c)_{\max} \\ &\text{(Unsaturated Region)} \end{aligned}$$

Question

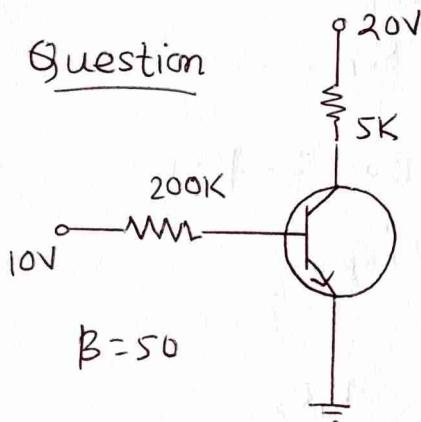


$$V_{CE} = V_{CC} - i_c R_C$$

$$= 20 - i_c \times 5k$$

$$\bar{i}_B = \frac{10 - 0.7}{200} = 0.0465 \text{ mA}$$

$$\bar{i}_c = \beta \bar{i}_B = 2.33 \text{ mA}$$
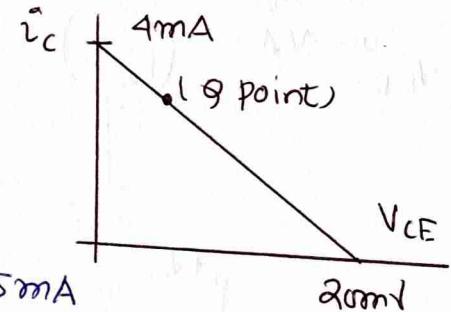
$$\begin{aligned} V_{CE} &= 20 - i_c \times 5k \\ &= 8.375 \text{ V} \end{aligned}$$




Stability Factor:

$$S = \left( \frac{d \bar{i}_c}{d \bar{i}_{cBO}} \right)_{V_{BE}, \beta}$$

$$S = \left( \frac{d \bar{i}_c}{d \beta} \right)_{\bar{i}_c, V_{BE}}$$

$$S = \left( \frac{d \bar{i}_c}{d V_{BE}} \right)_{\beta, \bar{i}_{cBO}}$$

①

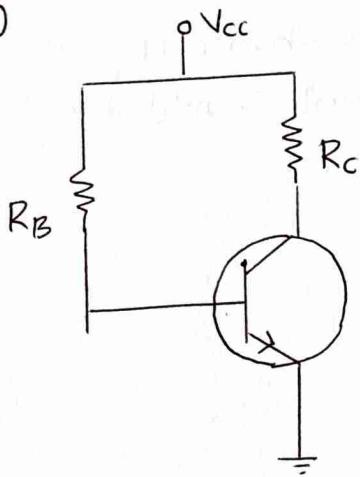

$$V_{CC} - i_B R_B - V_{BE} = 0$$

$$\dot{i}_B = \frac{V_{CC} - V_{BE}}{R_B}$$

$$\dot{i}_B = \frac{V_{CC}}{R_B}$$

$$\dot{i}_c = \beta \dot{i}_B + (1+\beta) \dot{i}_{CB0}$$

$$\dot{i}_c = \beta \dot{i}_B = \beta \frac{V_{CC}}{R_B}$$


$$\frac{d\dot{i}_c}{d\dot{i}_c} = \beta \frac{d\dot{i}_B}{d\dot{i}_c} + (1+\beta) \frac{d\dot{i}_{CB0}}{d\dot{i}_c}$$

$$1 = (1+\beta) \frac{1}{S}$$

$$\text{stability, } S = \left( \frac{d\dot{i}_c}{d\dot{i}_{CB0}} \right)_{\beta, V_{BE}} \Rightarrow Y_S = \left( \frac{1}{1+\beta} \right)$$

$$S = (1+\beta) \quad (\text{But is also } \beta \text{ dependent})$$

②

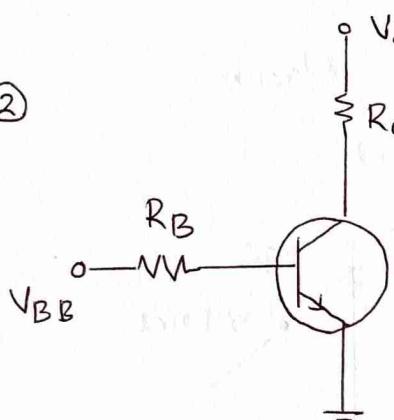


$$V_{BB} - i_B R_B - V_{BE} = 0$$

$$\dot{i}_B = \frac{V_{BB} - V_{BE}}{R_B} \approx \frac{V_{BB}}{R_B}$$

$$\dot{i}_c = \beta \dot{i}_B + (1+\beta) \dot{i}_{CB0} \quad S = \beta + 1$$

$$\dot{i}_c = \beta \cdot \frac{V_{BB}}{R_B} + (1+\beta) \dot{i}_{CB0}$$

③

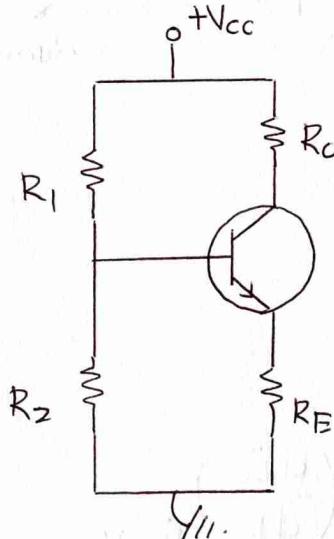

$$V_{th} = \frac{V_{CC} R_2}{R_1 + R_2}$$

$$R_{th} = \frac{R_1 R_2}{R_1 + R_2}$$

~~$$\dot{i}_B = \frac{V_{th} - V_{BE}}{R_{th} + (1+\beta) R_E}$$~~

But  $\dot{i}_B$   
should not  
written in  
form of  $\beta$

~~$$\dot{i}_c = \beta \dot{i}_B + (1+\beta) \dot{i}_{CB0}$$~~

$$= \beta \left[ \frac{V_{th} - V_{BE}}{R_{th} + (1+\beta) R_E} \right] + (1+\beta) \dot{i}_{CB0}$$

That's why the  
process is wrong

Stability,  $S = (1+\beta)$

Also,  $\dot{i}_c = \beta \left( \frac{V_{th} - V_{BE} - \dot{i}_E R_E}{R_{th}} \right) + (1+\beta) \dot{i}_{cB0}$

$$\dot{i}_c = \beta \left( \frac{V_{th} - V_{BE} - (\dot{i}_c + \dot{i}_B) R_E}{R_{th}} \right) + (1+\beta) \dot{i}_{cB0}$$

$$1 = \beta \left( -\frac{R_E}{R_{th}} \right) + (1+\beta) \frac{1}{S} \Rightarrow S = \left( \frac{1+\beta}{1+\beta} \frac{R_E}{R_{th}} \right)$$

so,  $S = \frac{(1+\beta) R_{th}}{R_{th} + \beta R_E}$   $R_I \sim R_{th}$  (Very less)  
 $R_{th} \ll \beta R_E$

$$S = \frac{(1+\beta)}{\beta} \frac{R_{th}}{R_E}$$

$$S = (1 + \frac{1}{\beta}) \frac{R_{th}}{R_E}$$

### ③ Collector to Base Bias

$$V_{cc} - \dot{i}_B R_B - V_{BE} = 0$$

$$\dot{i}_B = \frac{V_{cc} - V_{BE} - \dot{i}_c R_c}{R_c + R_B}$$


$$\dot{i}_c = \beta \left( \frac{V_{cc} - V_{BE} - \dot{i}_c R_c}{R_c + R_B} \right) + (1+\beta) \dot{i}_{cB0}$$

$$\frac{d\dot{i}_c}{d\dot{i}_c} = -\frac{\beta R_c}{R_c + R_B} + (1+\beta) \frac{d\dot{i}_{cB0}}{d\dot{i}_c}$$

$$1 + \frac{\beta R_c}{R_c + R_B} = (1+\beta) \frac{1}{S}$$

$$\frac{1}{S} = \frac{1}{(1+\beta)} + \frac{\beta R_c}{(\beta+1)(R_B + R_c)}$$
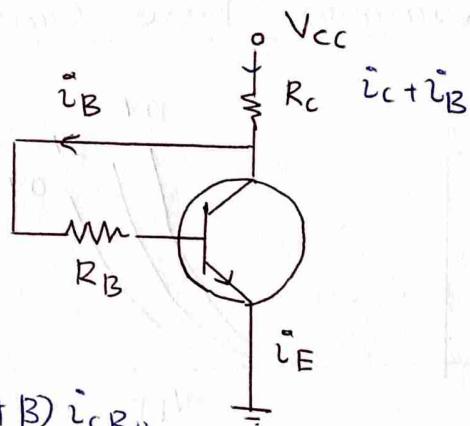
$$\frac{1}{S} = \frac{R_B + R_c + \beta R_c}{(1+\beta)(R_B + R_c)}$$



$$S = \frac{(\beta+1)(R_B + R_c)}{(\beta+1)(R_c + R_B)}$$

$$S = \frac{(\beta+1)R_B}{(\beta+1)R_c + R_B}$$

(  $R_B \gg R_c$  )

$$S = \frac{(\beta+1)R_c}{(\beta+1)R_c} = 1$$

#### ④ Emitter Bias

$$\hat{i}_B = \frac{V_{CC} - V_{BE} - i_E R_E}{R_B}$$


$$\hat{i}_B = \frac{V_{CC} - i_C R_E - V_{BE}}{R_B + R_E}$$

$$\hat{i}_C = \beta \hat{i}_B + (1 + \beta) \hat{i}_{CB0}$$

$$S = \frac{(1 + \beta)(R_B + R_E)}{R_B + (\beta + 1)R_E}$$

$$R_B \gg R_E$$


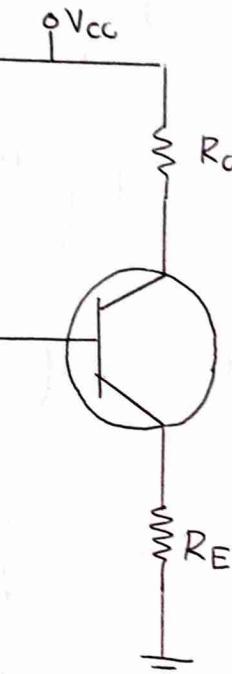
$$S = \frac{(1 + \beta) R_B}{R_B + (1 + \beta) R_E}$$



$$R_E \gg R_B$$

$$S = \frac{(1 + \beta) R_E}{(1 + \beta) R_E + R_B} = 1$$

#### ⑤ Common Base Configuration

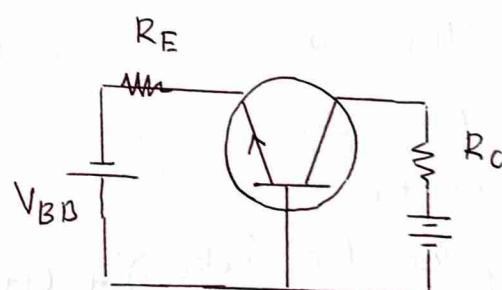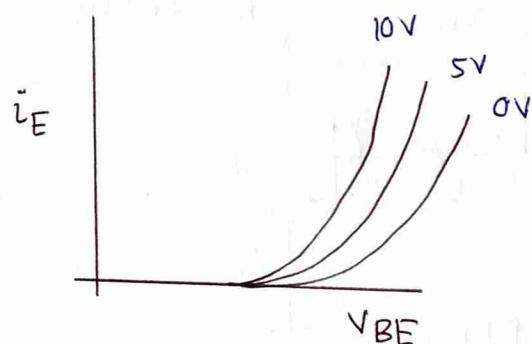

( $V_{CB}$  as Constant)  
Reverse Bias



Base region is narrowed

with increase Reverse Bias


less current is needed for  
forward Bias

Early Effect

① For a BJT under Saturation Condition

$$\Rightarrow i_c < \beta i_B$$

where  $i_B$  from  
Circuit diagram

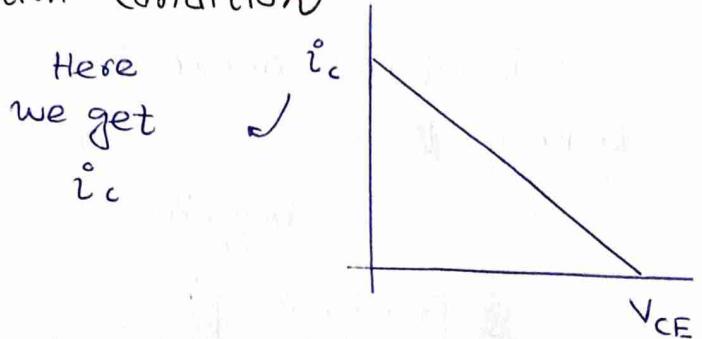


② In a phase shift oscillator, the frequency determining elements are


$$\Rightarrow f = \frac{1}{2\pi\sqrt{6} RC} \quad \text{both } R \text{ and } C$$

③ In a phase shift oscillator  $R = 1M\Omega$ ,  $C = 68 \mu F$   
At what frequency does the circuit oscillates
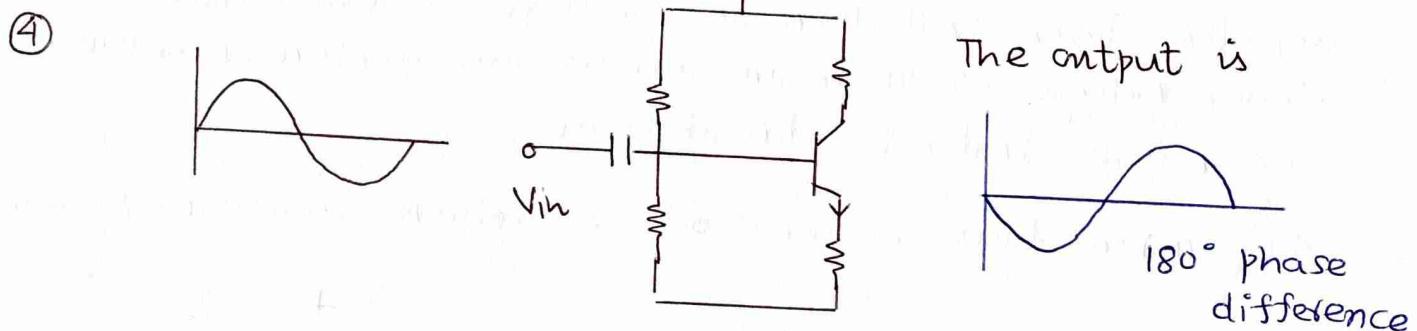
$$\Rightarrow f = \frac{1}{2\pi\sqrt{6} RC} = \frac{1}{2\pi\sqrt{6} \times 10^6 \times 68 \times 10^{-12}} = 954 \text{ Hz}$$



The output is

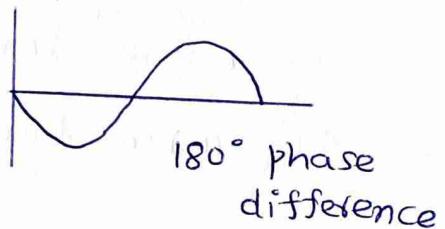



⑤ In a phase shift oscillator the capacitance of each capacitor is  $5 \mu F$ . The value of  $R$  so that a frequency of  $800 \text{ Hz}$  is produced

$$\Rightarrow f = \frac{1}{2\pi\sqrt{6} RC} = 800$$

$$\frac{1}{R} \times \frac{1}{5} \times 10^{-12} = 800 \times 2\pi\sqrt{6} \Rightarrow R = 16.25 \text{ k}\Omega$$

## Breakdown

It always occurs in  
Reverse Bias.

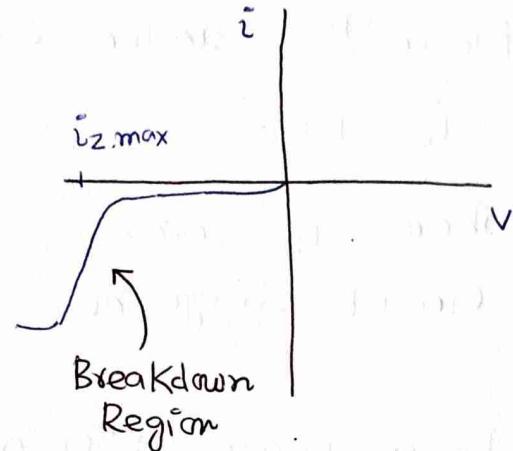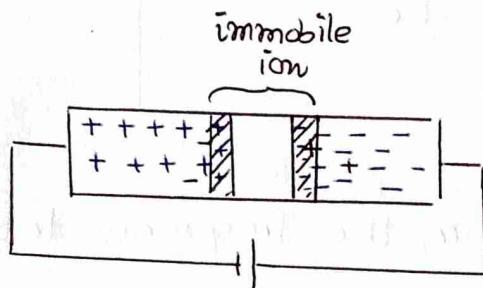

## Zener Diode

By KE,  $e^-$  will strike at depletion region and knock out the electrons.  $\Rightarrow$  Avalanche Breakdown.

Further strike  
That's why current will be  
increase very fast.

- > If we increase break<sub>c</sub> impurity (doping) width of the depletion layer will decrease so that we can control Zener voltage. So there are no such difference between Zener and Avalanche Breakdown
- > At Forward Bias, Zener diode will behaves like normal diode.

> Voltage across A and B is  $V_{th}$



if  $V_{th} > V_z \Rightarrow$  Zener is on  $\Rightarrow V_o = V_z$

$V_{th} < V_z \Rightarrow$  Zener is off  $\Rightarrow V_o = V_{th}$

> How to get  $V_{th}$ :


Thevenin Voltage
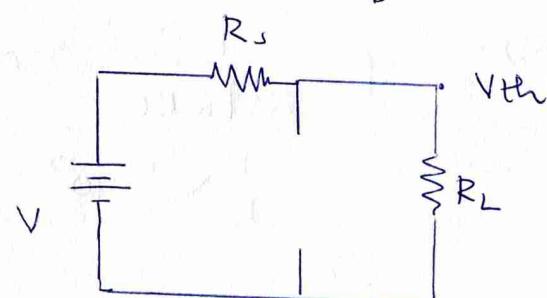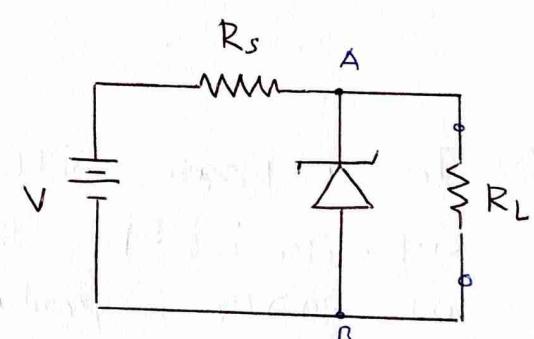
$$V_{th} = \left( \frac{VR_L}{R_s + R_L} \right)$$



① Is the diode ON or OFF

⇒

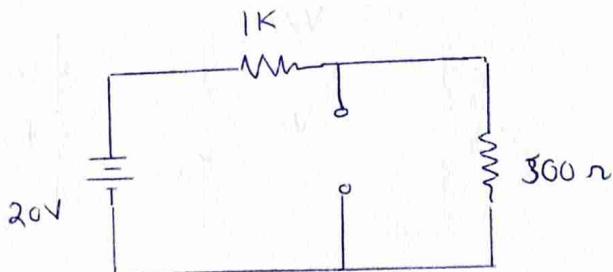

$$V_{th} = \frac{20 \times 300}{1500} = 6.67 \text{ Volt}$$

$$V_z = 15 \text{ V}$$

$$V_z > V_{th}$$

Zener diode is off.

So output voltage,  $V_o = V_{th} = 6.67 \text{ volt}$

②


check the zener diode

⇒

$$V_{th} = \frac{2 \times 20}{3} = 13.33 \text{ Volt}$$

$$V_z = 10 \text{ V} \text{ so } V_{th} > V_z$$

Diode is ON.

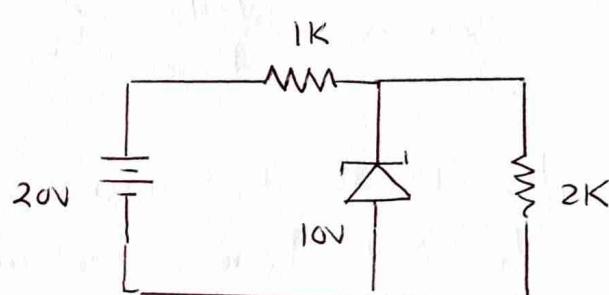

$$\text{so } V_{out} = V_z = 10 \text{ Volt}$$

③  $V, R_s$  is Given:

Minimum Voltage to make ON  
of the Zener diode


$$V_{th} > V_z (\text{ON})$$

$$\text{Minimum } V_{th} = V_z$$

$$\frac{VR_L}{R_L + R_s} = V_z$$

∴

we get  $R_{L,\min}$

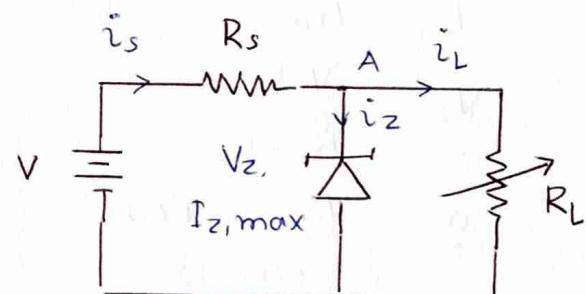

As the diode is ON, Voltage at point A is  $V_z$

$$i_s = \frac{V - V_z}{R_s} \text{ is constant}$$

$$i_s = i_z + i_L$$

As  $R_L \uparrow, i_L \downarrow, i_z \uparrow$  as  $i_s$  is constant

But  $i_z$  has a maximum value

$$i_s = i_{L,\min} + i_{z,\max}$$

$$\text{we get } R_{L,\max}$$


$$i_s = \frac{V_z}{R_{L,\max}} + i_{z,\max}$$

#### ④ Range of $R_s$

As the diode is ON

$$V_{th} = V_z$$
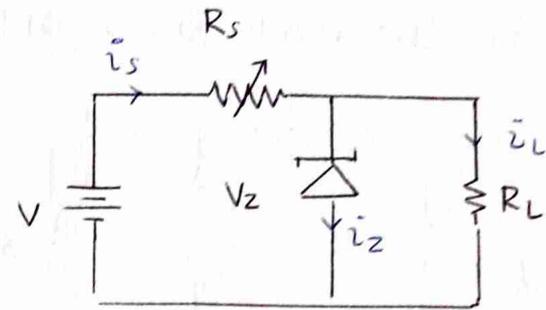
$$\frac{VR_L}{R_L + R_s} = V_z \Rightarrow R_s \text{ max}$$



$$\dot{i}_s = \frac{V - V_z}{R_s} \quad \dot{i}_L = \frac{V_z}{R_L} = \text{constant}$$

$$\dot{i}_s = \dot{i}_z + \dot{i}_L \Rightarrow \dot{i}_L = \dot{i}_s - \dot{i}_z$$

$\dot{i}_s, \dot{i}_z$  maximum

$\dot{i}_z, \dot{i}_s$  minimum

$$\dot{i}_L = \frac{V - V_z}{R_L} - \dot{i}_{z,\text{max}}$$

$R_s \downarrow, \dot{i}_s \uparrow$


$$\dot{i}_{z,\text{max}} = \frac{V - V_z}{R_{s,\text{min}}} - \dot{i}_L$$

125 Ω

$$\textcircled{5} \quad R_s = 125 \Omega, R_L = 470 \Omega,$$

$$V_z = 9V, I_{z,\text{max}} = 65 \text{ mA}$$

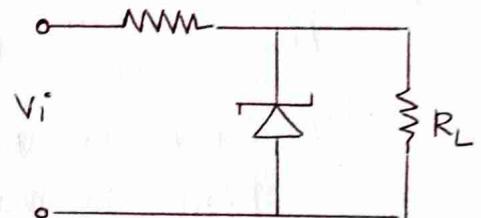Find  $V_{i,\text{max}}$  and  $V_{i,\text{min}}$



$$\Rightarrow V_z = V_{th}$$

$$V_z = \frac{V_i R_L}{R_L + R_s}$$

$$g = \frac{V_{i,\text{min}} \times 470}{470 + 125}$$

$$V_{i,\text{min}} = 11.4 \text{ Volt}$$

$$\dot{i}_L = \dot{i}_s - \dot{i}_z = \frac{V_z}{R_L}$$

$$\frac{V_{\text{max}} - V_z}{R_s} - (65 \times 10^{-3}) = \frac{9}{470}$$

$$\frac{V_{\text{max}} - 9}{125} = 0.084 \Rightarrow V_{\text{max}} = 10.5$$


⑥ The ratio of max to min Power dissipated will be

⇒ At 5V, Diode off

$$V = \frac{5 \times 1000}{1000 + 500} - \frac{10}{3} = 3.33 \text{ Volt}$$

$$P = \frac{V^2}{R_L} = \frac{(3.33)^2}{1000} \text{ watt (Min)}$$

500 Ω

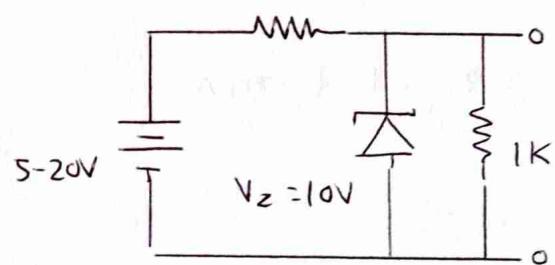

To ON the diode


$$10 = \frac{V \times 1000}{15000}$$

$$V = 15 \text{ Volt}$$

$$P = \frac{10^2}{1000} = 0.1 \text{ watt}$$

(Maximum)


- ①
- 
- Find the value  $V_o$
- $$-4 + 2i_1 + 2(i_1 - i_2) = 0$$
- $$4i_1 - 2i_2 = 4$$
- $$2i_1 - i_2 = 2 \quad \text{--- ①}$$
- $$2i_2 - 2 + 2(i_2 - i_1) = 0$$
- $$4i_2 - 2i_1 = 2 \quad \text{--- ②}$$
- $$2i_1 = 2 + i_2 = 2 + \frac{4}{3} = \frac{10}{3}$$
- $$i_1 = \frac{5}{3} \text{ A}$$
- $$2i_2 = 4 \Rightarrow i_2 = \frac{4}{3} \text{ A}$$
- Current through the diode
- $$i = (i_1 - i_2) = \frac{1}{3} \text{ A}$$
- Voltage across the resistance  $V_o = 2i = \frac{2}{3} \text{ volt}$
- ②
- 
- Voltage across diode is 0.6 Volt.
- Find the values of  $V_1$  and  $V_2$
- $\Rightarrow$  As diode  $D_1$  is in reverse bias,  $V_1 = 6 \text{ volt}$
- Now voltage across  $D_2$
- $$V_2 = 6 - 0.6 = 5.4 \text{ volt}$$
- $$V_1 = 6 \text{ volt}, V_2 = 5.4 \text{ volt}$$
- ③
- 
- Find the current across Diode
- $\Rightarrow$  By Node analysis
- $$\frac{V_a - 25}{10} + \frac{V_a - 0}{15} + \frac{V_a - 20}{4} = 0$$
- $$6V_a - 150 + 4V_a + 15V_a - 300 = 0$$
- $$25V_a = 450 \Rightarrow V_a = 18 \text{ Volt}$$
- Current diode
- $$i_d = \frac{20 - 18}{4} = 0.5 \text{ A}$$
- ④ A particular LED emits light of  $\lambda = 5490 \text{ Å}$ . The energy band gap of semiconductor material
- $\Rightarrow \Delta E = \frac{hc}{\lambda} = \frac{6.63 \times 10^{-34} \times 3 \times 10^8}{5490 \times 10^{-10}} = 2.26 \text{ eV.}$

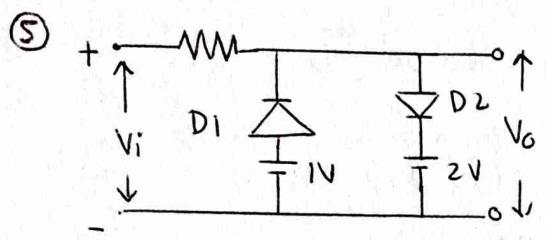

Voltage drop = 0.7V.

if  $V_o = Vi$  then

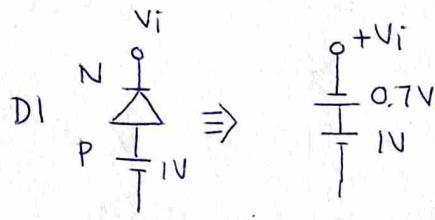- $\Rightarrow$  Input Voltage is equal to output voltage if both the diodes are in reverse bias.




D1 will be in Forward Bias

$$\text{if } V_p - V_N > 0.7 \quad V_i \leq 3 \text{ Volt}$$

$| - V_N > 0.7 \quad \text{For Reverse Bias}$

$$| - V_i > 0.7 \quad V_i > 0.3 \text{ Volt}$$

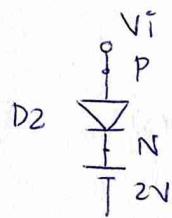

D2 will be in Forward Bias

$$V_p - V_N > 0.7$$

$$V_p - 2 > 0.7 \Rightarrow V_p > 2.7 \text{ Volt}$$

$$0.3 < V_i < 2.7$$

For Reverse Bias  $V_p < 2.7 \text{ Volt}$

- (6) Check D1, D2 are in Forward Bias or not

(Given  $V_f = 0.6 \text{ Volt}$ )

$\Rightarrow$

$$-5.4 + 0.6 + 12i_1 + 18(i_1 - i_2) = 0$$

$$30i_1 - 18i_2 = 4.8$$


$$5i_1 - 3i_2 = 0.8 \quad \textcircled{1}$$

$$40i_1 - 24i_2 = 6.4$$

$$-18i_1 + 24i_2 = -4.4$$

$$22i_1 = 2$$
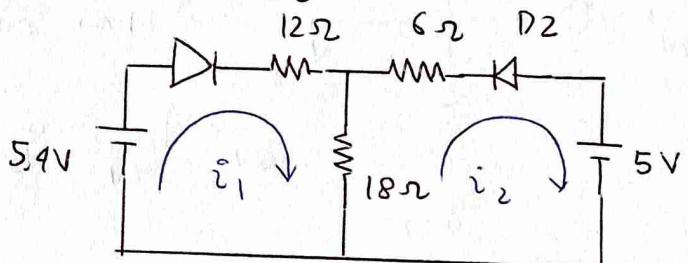
$$i_1 = 0.09 \text{ A} \quad i_2 = -0.09 \text{ A}$$



$$6i_2 - 0.6 + 5 + 18(i_2 - i_1) = 0$$


$$-18i_1 + 24i_2 = -4.4 \quad \textcircled{2}$$

$$i_1 = \frac{1}{11} \quad i_2 = \frac{1}{3}(5i_1 - 0.8)$$

$$= \frac{1}{3}\left(\frac{5}{11} - 0.8\right) = -0.09 \text{ A}$$

Both D1 and D2 is in Forward Bias.

⑦ Draw the transfer characteristic

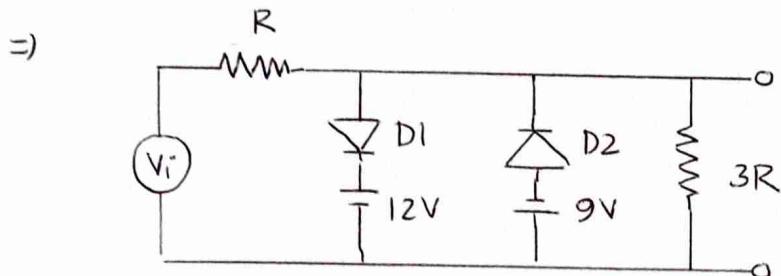

$$\begin{array}{lll} \text{D1} & \begin{array}{c} V_p \\ \text{---} \\ 12V \end{array} & V_p - V_N > 0 \\ & \text{---} \\ & V_N & V_p > V_N \\ & \text{---} \\ & V_{p_1} > 12 \text{ Volt} & \begin{array}{c} V_N \\ \text{---} \\ 9V \end{array} \\ & (\text{Forward Bias}) & V_p > 9V \end{array}$$

$V_i \leq 12 \text{ Volt (RB)}$

For Forward Bias


$$\begin{array}{l} V_p - V_N > 0 \\ -9 - V_N > 0 \\ V_i \leq -9 \\ V_i > -9 \text{ V (RB)} \end{array}$$

$$D1, D2 \Rightarrow FB \Rightarrow V_o = -9V$$

$$D1 FB, D2 RB \Rightarrow V_o = -12V$$

$$D1 RB, D2 FB \Rightarrow V_o = -9V$$

$$D1, D2 RB \Rightarrow V_o = V_i$$

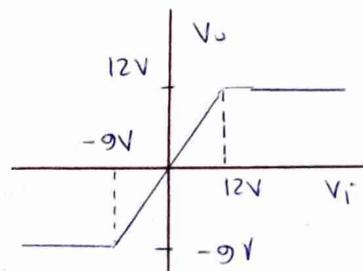

⑧ Find the Current through diode

$\Rightarrow$

$$-10 + 4i_1 + 4(i_1 - i_2) = 0$$

$$8i_1 - 4i_2 = 10$$

$$4i_1 - 2i_2 = 5 \quad \text{---} \textcircled{1}$$


$$4i_1 - 2i_2 = 5$$

$$\underline{-4i_1 + 5i_2 = -2}$$

$$3i_2 = 3$$

$$i_2 = 3/3 = 1$$

$$i_2 = 1$$

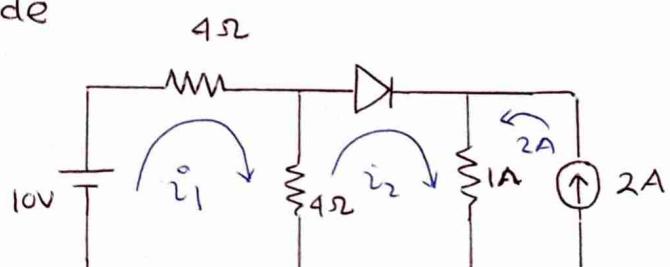

$$1(i_2 + 2) + 4(i_2 - i_1) = 0$$

$$5i_2 - 4i_1 = -2$$

$$3i_2 - 2i_1 = -1 \quad \text{---} \textcircled{11}$$

$$4i_1 = 5 + 2i_2 = 5 + \frac{3}{2} = \frac{13}{2}$$

$$i_1 = 13/8$$

Current through diode is 1A.

- ① In the circuit, the input voltage  $V_i$  is 2V,  $V_{cc} = 16V$ ,  $R_2 = 2K\Omega$  and  $R_L = 10K\Omega$ . The value of  $R_1$  required to deliver 10mW of power across  $R_L$  is


CSIR-2016

⇒ By KCL

$$\frac{0-V_i}{R_2} = \frac{V_i-V_o}{R_1} = \frac{V_o-0}{R_L}$$

$$P_L = \frac{V_o^2}{R_L} = 10mW \Rightarrow V_o = 10 \text{ Volt}$$

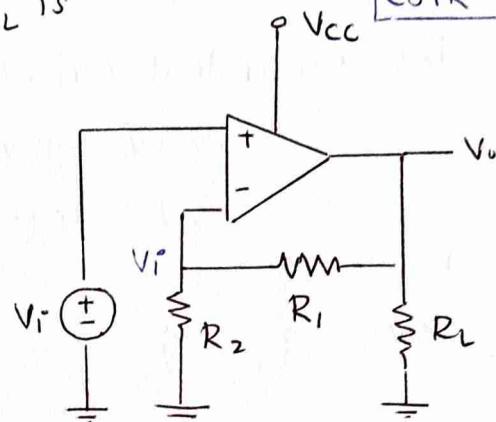
$$\frac{0-2}{2} = \frac{2-10}{R_1} \Rightarrow R_1 = 8K\Omega$$



- ② Consider the circuit.  $\beta = 100$ . Find the Q point

GATE-2012

⇒

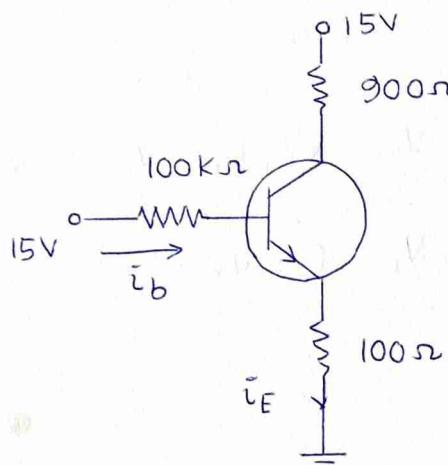


$$i_c = \beta i_b = 14.3 \text{ mA}$$

$$-15 + 100i_b + 0.7 + 100i_E = 0$$

$$100i_b + 0.1i_E = 14.3$$

$$i_b = \frac{14.3}{100} \text{ mA}$$

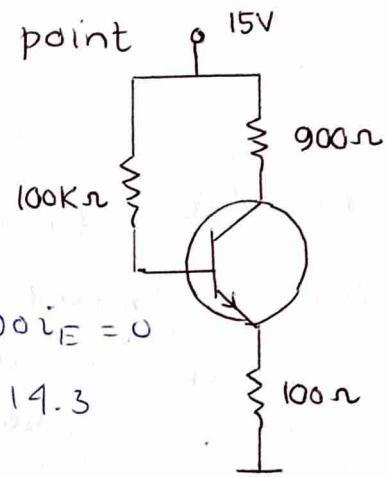

$$V_{CE} = V_{cc} - i_c(R_{ct} + R_E)$$

$$= 15 - (900 + 100) \times 13 \times 10^{-3} = 2 \text{ V}$$

$$i_c = \frac{V_{cc}}{R_c + R_E} = \frac{15}{1000} = 15 \text{ mA}$$

Q point. (2, 13mA)

- ③ Current passing through the diode

$$-24 + 12i_1 + 6(i_1 - i_d) = 0$$

$$18i_1 - 6i_d = 24$$

$$3i_1 - i_d = 4 \quad \textcircled{1}$$

$$-2i_d + 6i_1 = 8$$

$$0.7 + 3.3i_d + 6(i_d - i_1) = 0$$


$$9.3i_d - 6i_1 = -0.7 \quad \textcircled{11}$$

$$9.3i_d - 6i_1 = -0.7$$

$$-2i_d + 6i_1 = 8$$

$$7.3i_d = 7.3 \Rightarrow i_d = 1 \text{ mA}$$

GATE-2012

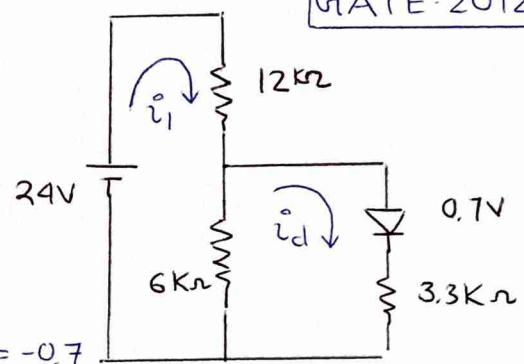


④

In the following circuit,  $\beta = 100$ ,  $V_{BE} = 0.7V$  what will be the collector voltage.  $V_{CC} = 15V$ ,  $R_1 = 100K\Omega$ ,  $R_2 = 50K\Omega$ ,  $R_C = 4.7K\Omega$ ,  $R_E = 3.3K\Omega$

JAM 2023

=)

The equivalent circuit

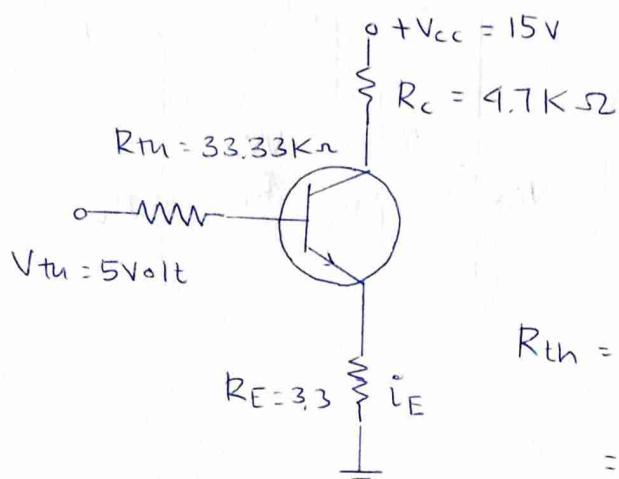

$$R_{th} = \frac{V_{CC} R_2}{R_1 + R_2}$$

$$= \frac{15 \times 50}{150} = 5 K\Omega \text{ Volt}$$

$$R_{th} = \frac{R_1 R_2}{R_1 + R_2} = \frac{100 \times 50}{150} = 33.33 K\Omega$$

$$-V_{th} + i_b R_{th} + V_{BE} + i_E R_E = 0$$

$$-5 + 33.3 i_b + 0.7 + i_b 101 \times 3.3 = 0$$

$$i_b = \frac{5 - 0.7}{366.6} = \frac{4.3}{366.6} A$$

$$V_{CC} - i_c R_C = V_C - i_E R_E$$

$$V_C = 8.9 \text{ Volt}$$

